

Introduction

※Use a pair of scissors to cut out parts with the frame, be careful not to tear off by hand





Prepare for experiment

※Please check the flap of the box regarding the items inside

Preparation A: Prepare vinyl leads

○As shown below, Cut the vinyl leads.
※Make 3 of the same thing, please keep extra vinyl leads in case of loss or breakage.


○Pinch and pull the vinyl of vinyl leads

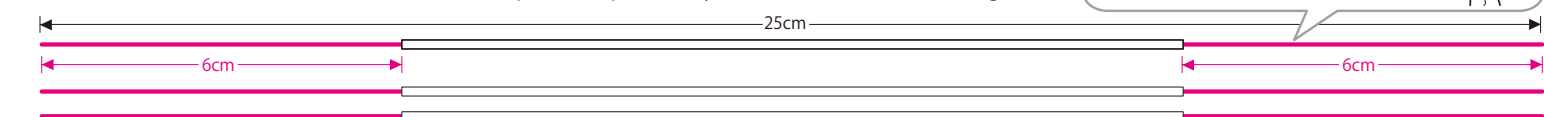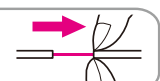

○Pass the vinyl stripped leads through the hole in the plug twice, twist firmly so that leads do not come loose

Note

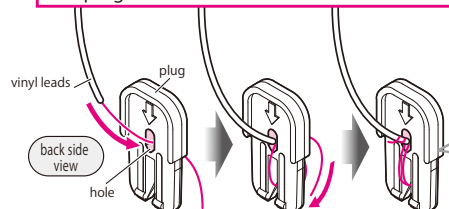○When attaching the plug to leads of motor or socket, pass the leads through the holes of plug once and then twist it!





Note

※Make sure the vinyl of the leads do not come out




※As shown in the figure, prepare leads.

1 Vinyl leads (Plug on one side)

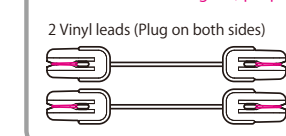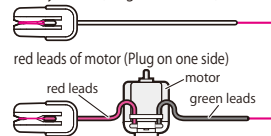


Plug, How to use parallel plug and dry battery box

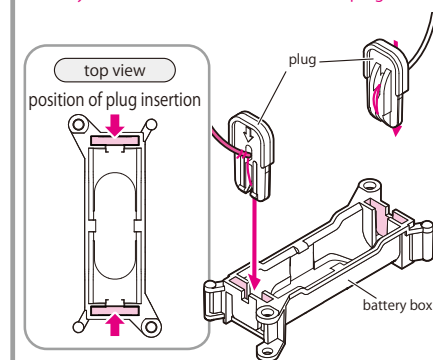
○Insert plug into the dry battery box
※Pay attention to the orientation of the plug



dry batteries connected in series

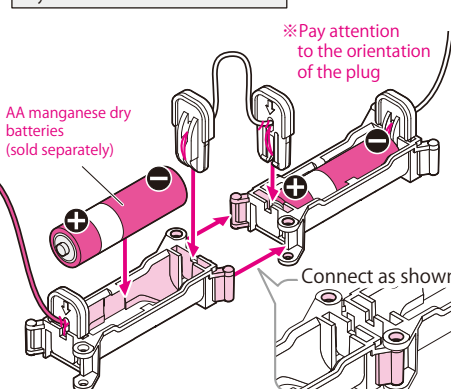

dry batteries connected in parallel

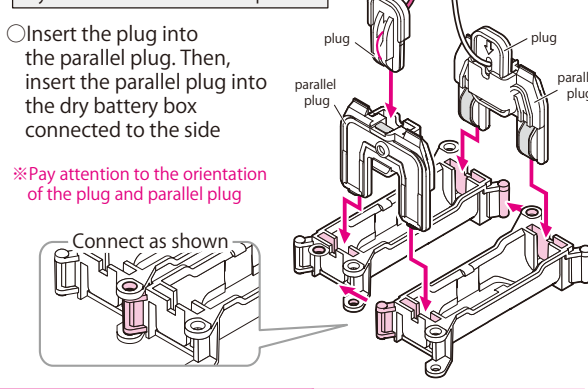


Be careful of short circuit

※Insert the parallel plug only after removing the dry batteries

Preparation C: Attach the propeller to the motor



○Put the gear (small) to the gear holder and insert the motor axis into the gear

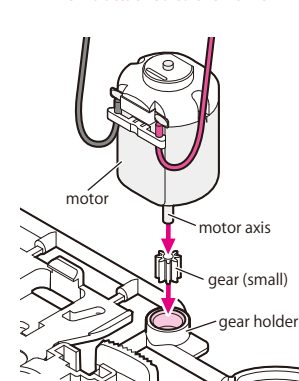※Use the gear holder which is attached to the frame



○Attach the motor to the motor cover

※Fit firmly

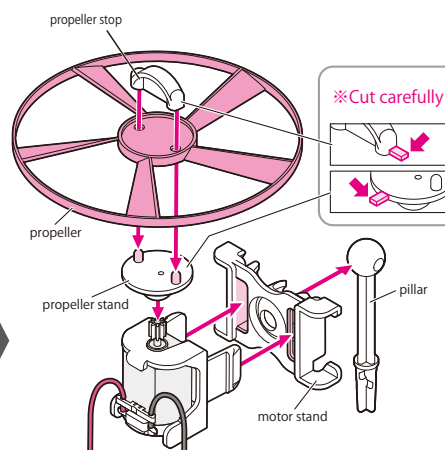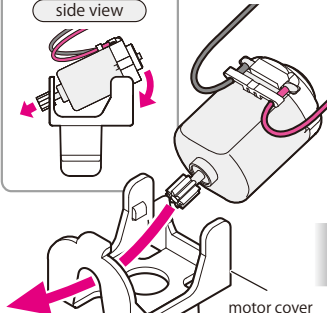


Let's try! How to represent the circuit

○If you use symbols to represent a circuit diagram, it is easy to understand how they are connected

★Draw a circuit diagram using symbols below!

circuit symbols

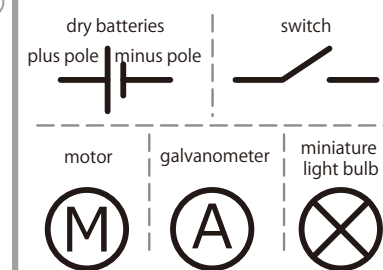

Experiment 1

Let's check the connection between direction of the dry batteries and the direction of the current

★Let's predict the direction of the motor after changing the direction of dry batteries

Prediction

Same, turn opposite

Change the direction of dry batteries

Result


★Let's predict the direction of the current after changing the direction of dry batteries

Prediction

Same, turn opposite

check with the galvanometer

Result

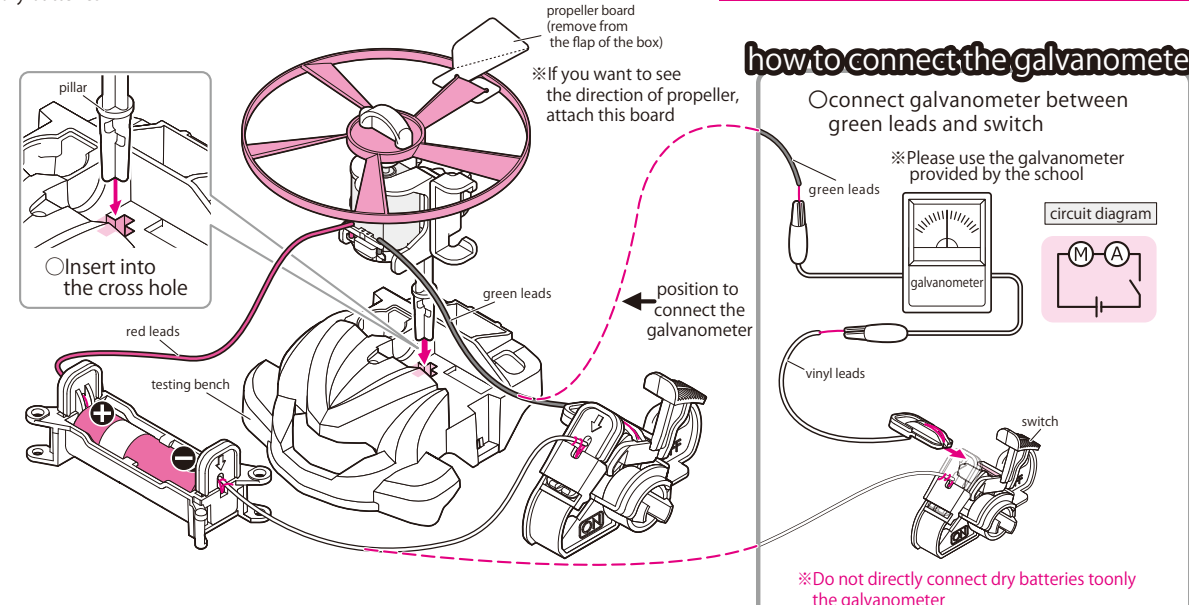

Experiment 2

Let's check the strength of the current if you change connection of dry batteries

★Let's predict the speed of motor with parallel/series connection compared to the speed of motor with 1 dry battery

Prediction

Series same, turn faster

Parallel same, turn faster

Change the connection of dry batteries

Result

Series

Parallel

★Let's predict the strength of current with parallel/series connection compared to the speed of motor with 1 dry battery

Prediction

Series same, stronger


Parallel same, stronger

check with the galvanometer

Result

Series

Parallel

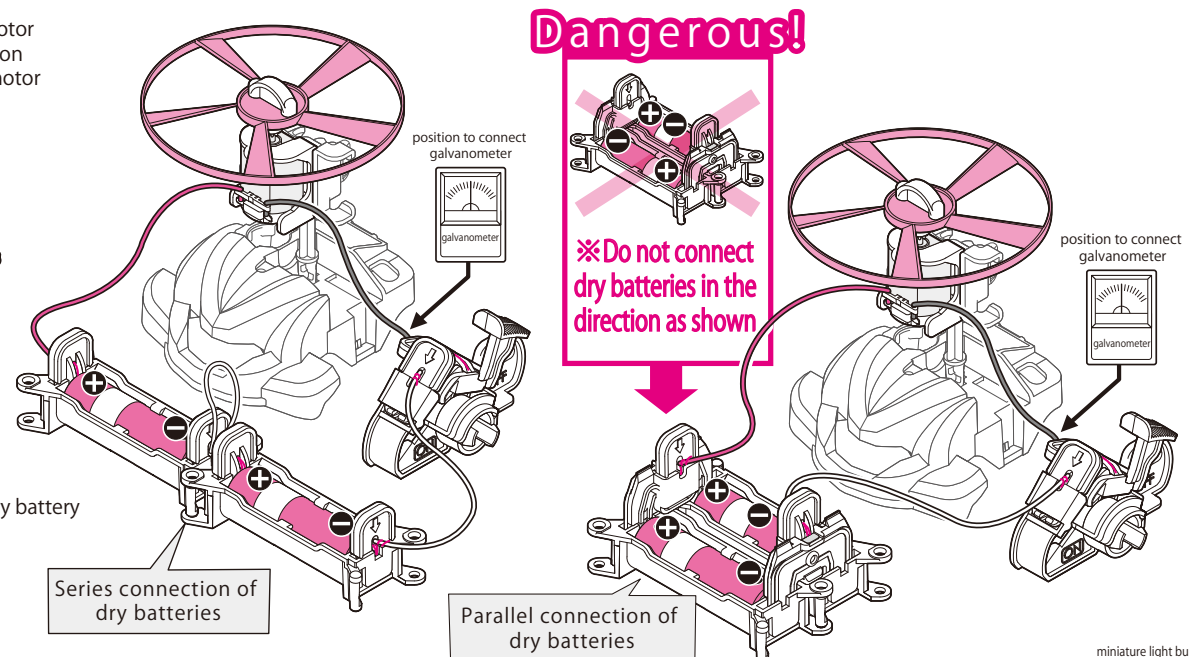


Dangerous!

※Do not connect dry batteries in the direction as shown

Let's try!

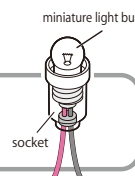★Let's compare the brightness when you change the motor to miniature light bulb
※Keep the miniature light bulb firmly in the socket



Let's try! Let's check how to connect batteries and check how to fly the propeller.


○Change the direction of dry batteries so that wind comes down

※If the dry batteries are weak, it may not fly.

★Let's check how the propellers with parallel or series connection fly compared to the ones with 1 dry battery

Dangerous!

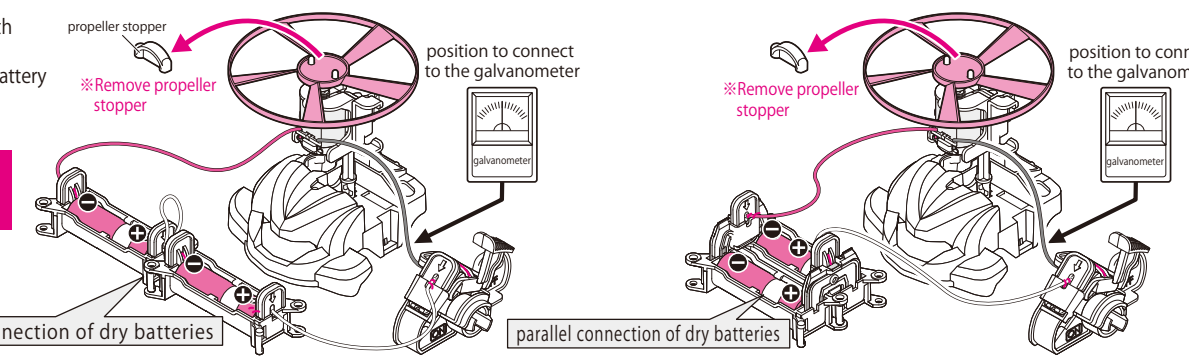Keep your face away from the direction in which propeller fly up




Preparation D: Assemble motor car

- Please use manganese dry batteries for this experiment
- After use, be sure to remove dry batteries

STEP 1


○Combine testing bench and the car body and install tires

※Cut carefully

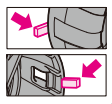

Preparation before assembly


○Remove propeller stand and motor stand

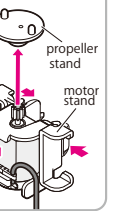

STEP 2


○Attach the dry batteries box and switch to the car body

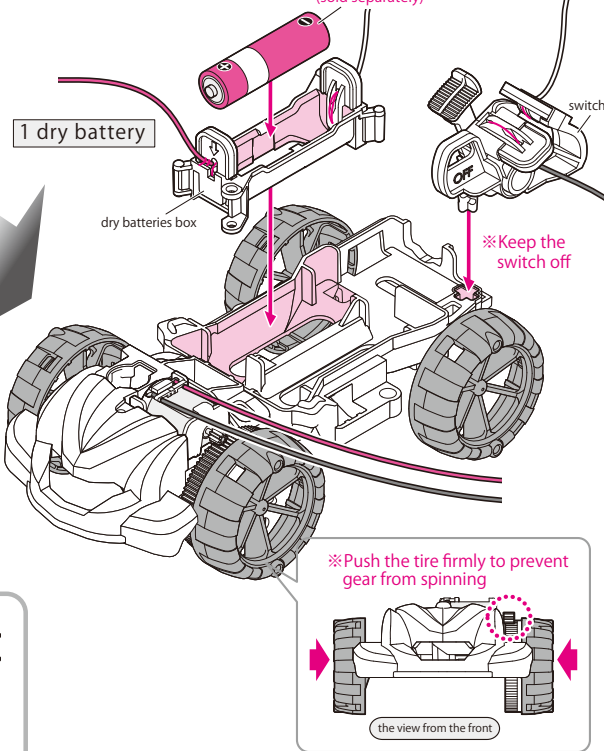AA manganese dry batteries (sold separately)



How to assemble testing bench and car body

○Insert the tip of car body into the hole of testing bench and rotate it

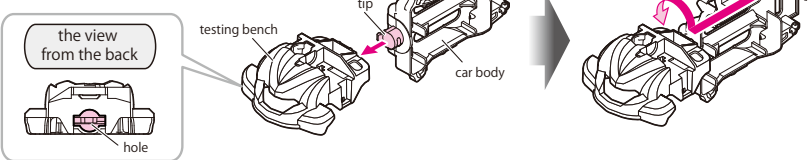

Experiment 3
Let's check the strength of the current using motor car

If the motor does not turn, check the connection

★ Let's predict and compare the speed of motor car with parallel/series, to the speed of motor car with 1 dry battery

Prediction

| | |
|----------|------------------|
| Series | same, run faster |
| Parallel | same, run faster |

Compare the speed

Result

| | |
|----------|--|
| Series | |
| Parallel | |

★ Let's predict and compare the strength of the current of motor, to the strength of the current of motor car with 1 dry battery

Prediction



| | |
|----------|----------------|
| Series | same, stronger |
| Parallel | same, stronger |

check with the galvanometer

Result

| | |
|----------|--|
| Series | |
| Parallel | |


Dangerous!

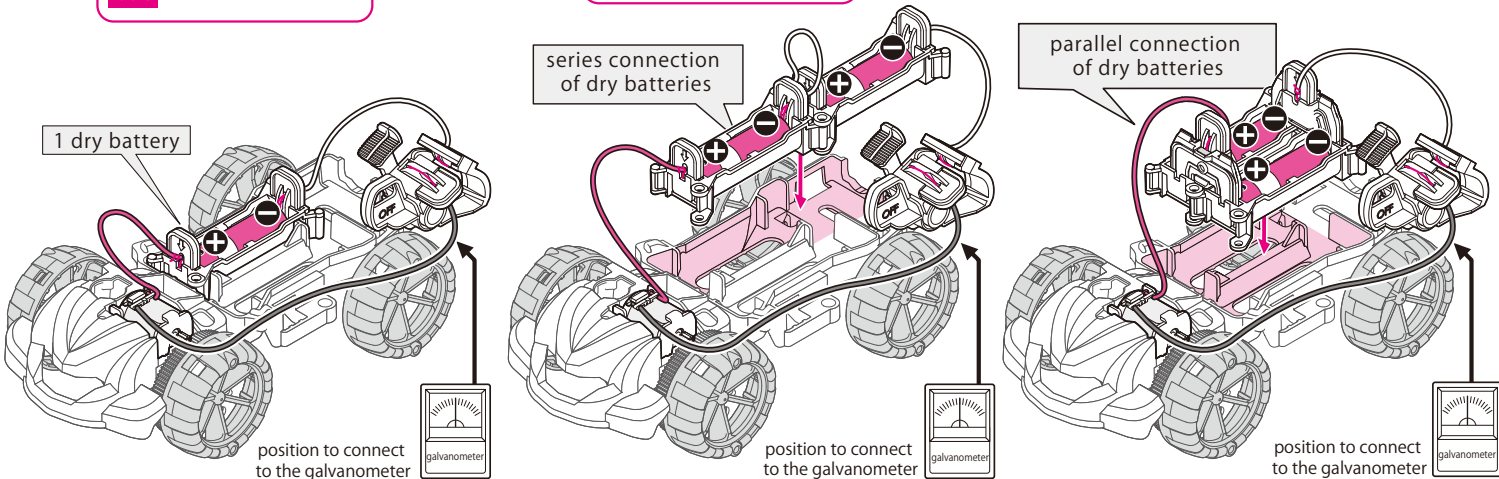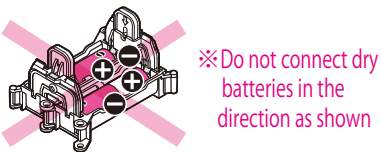

Let's try! Let's run a motor car with miniature light bulb

○Attach the socket (miniature light bulb) and car body cover by connecting the dry batteries in series

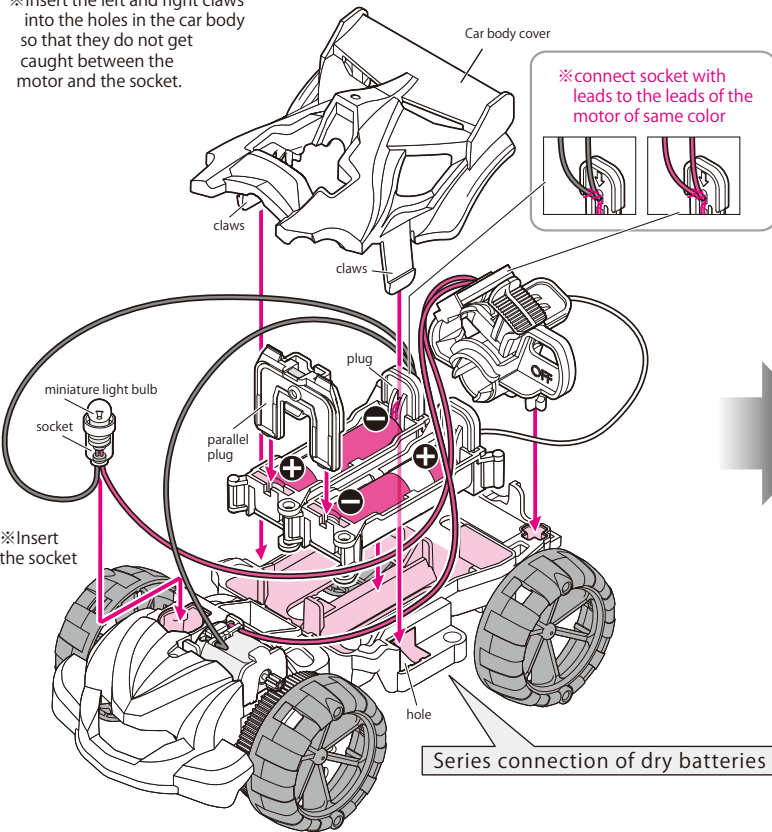※Insert the left and right claws into the holes in the car body so that they do not get caught between the motor and the socket.




motor car with miniature light bulb

※If the motor does not turn, or miniature light bulb does not light up, please check the connection

- Note
- When you run the motor car, please do so in a safe and wide place
 - If the motor car hits the wall and stops, change direction immediately or off the switch

Let's try! Let's run a propeller car

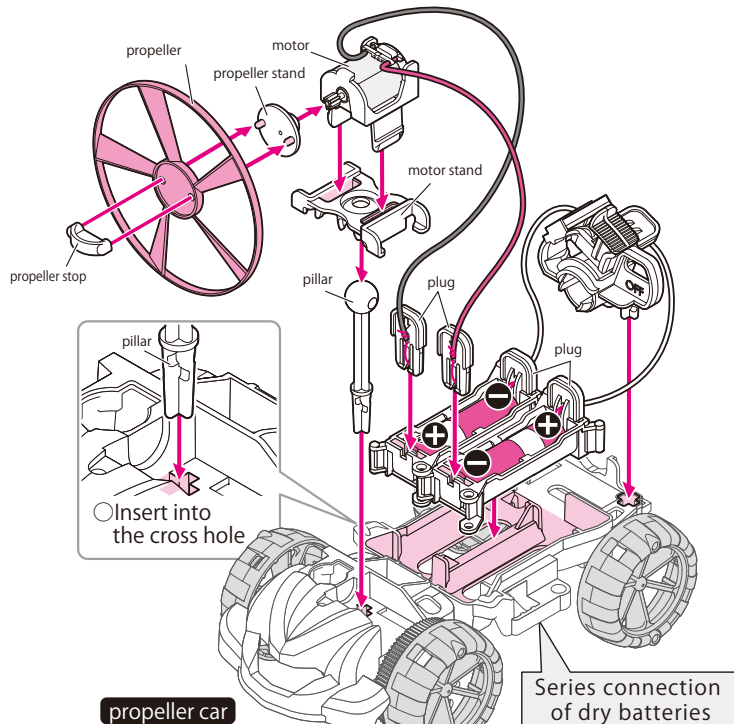○Remove motor and socket (miniature light bulb), assemble while paying attention to the orientation of the batteries and how to connect the wires.



Let's try! Let's explore the use of solar power!

★ Connect the solar cell to the motor, change the direction of the shining light, and then observe how the motor turns

★ Cast different shadows on the solar panel, and observe how the motor turns


★ Connect to galvanometer and observe the strength of the flowing electric current.

※Do not connect the solar cell directly to the galvanometer on its own

★ Replace the motor with the mini light bulb, and observe the brightness

Let's try! Let's run a solar car

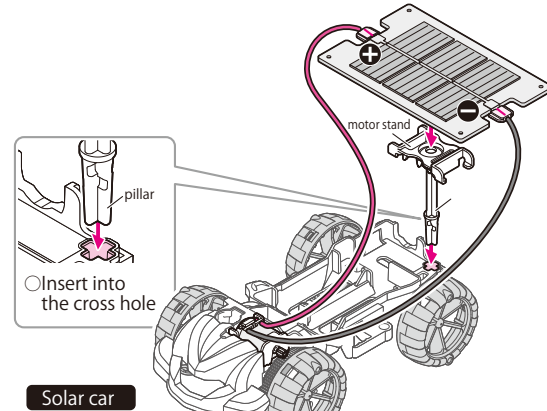○Pay attention to how the wires are connected and arrange



How to attach solar cell

○Connect the wires to the cap attached with the solar cell



○Attach a rubber band to the motor stand and insert the solar cell

