
Paper Craft Grumpy Ghost!

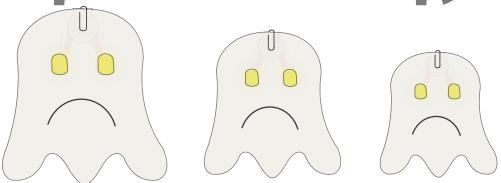

YOU WILL NEED:

TIME: 5-10 MINUTES



Paper & Vellum (Colorful **Construction Paper** or Card Stock.)



Scissors or **Exacto Knife**



Copper **Tape**



LEDs



Glue, or Adhesive Tape (To attach back layer)






1 Paper **Battery** Clip

Make an adorable Halloween Friend with glowing LED eyes from conductive tape and paper with Brown Dog Gadgets Conductive Tape Kit.


CUT GRUMPY GHOST

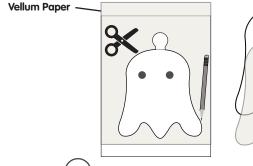Cut grumpy ghost template. Tape the white construction paper and translucent vellum together. Next cut out the ghost shape from both pieces of paper at the same time.




INSERT LED's

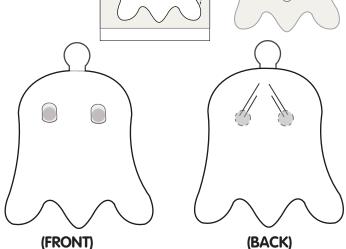Cut a tiny slit in the paper. Place your LEDs where the dots are on the white paper. Stick both legs through the slit.





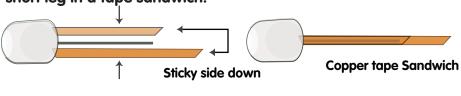On the back of the white constructive paper. add copper tape diangionally from the LEDs towards the center of the ghost . Secure the short leg in a tape sandwich.







Long LED legs on Battery

4 ATTACH BATTERY

Battery:
Place a battery at the end of the tape below
the tab (+ side up). Place long LED legs on top
of the battery. Fold the tab to cover the battery.
Your LED should light up!

Decorate:


Add the vellum sheet over the ghost. Draw a mouth with a black sharpie .

If your LEDs do not light up

- •Make sure tape is touching the battery on each side
- Make sure one piece of tape is not touching both sides of the battery
- Try flipping the battery over (+ side down)


If only one LED lights up

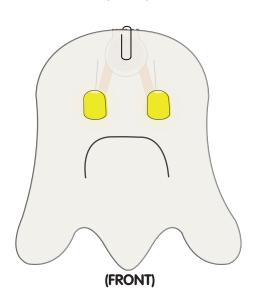- •Make sure both LEDS have a good connection
- •Flip the battery over. If the other LED now lights up, the long leg is on the wrong side



(BACK)

USE THIS TEMPLATE

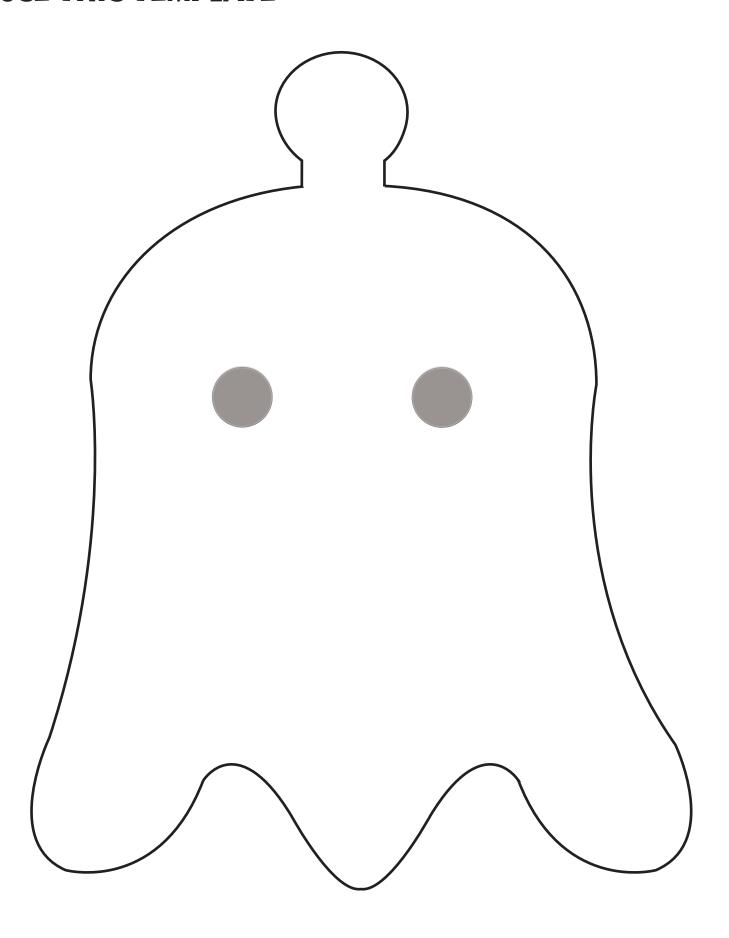

Please visit www.BrownDogGadgets.com for more great ideas & info.