

YOU WILL NEED: \_\_\_\_\_\_\_TIME: 20-30 MINUTES



or Card Stock.)





Scissors or Exacto Knife



Copper Tape



1 LED



Glue, or Adhesive Tape



1 Battery




1 Paper Clip

Make an adorable Dinosaur Friend with a glowing LED eye from conductive tape and paper with Brown Dog Gadgets Conductive Tape Kit.


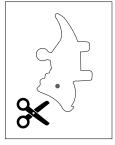
## **CUT OUT TRICER ATOPS**


Cut out the dino template and trace on colored paper. Then cut the shapes you traced.






2 INSERT LED's

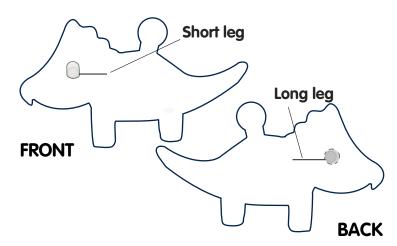Cut a tiny slit in the paper for the eye. Stick the longer leg through the slit, so there is one leg on each side of the paper.



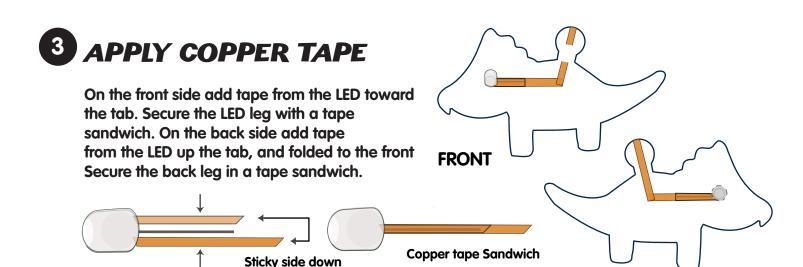

**BACK** 

**FRONT** 

## 4 ATTACH BATTERY & DECORATE

## **Battery**

Place a battery at the end of the tape below the tab (+ side up). Fold the tab to cover the battery. Your LED should light up!

If your LED does not light up

- •Make sure tape is touching the battery on each side
- Make sure one piece of tape is not touching both sides of the battery
- •Try flipping the battery over (+ side down)

## **Decorate:**

Add spikes and a belly to your Triceratops. Use template to trace on color paper and cut. Tape or glue the pieces onto the back your Triceratops.

