

# CONTENTS

## 11. Relay

1

Introduction	3
Identifying the Relay Terminals	5
<b>Experiment 23: Continuity Test of Relay</b>	<b>6</b>
Schematic Representation	8
Connecting a Relay on a Breadboard	8
<b>Experiment 24: Alternate Switching of LEDs Using a Relay</b>	<b>10</b>
Bump Switch	13
<b>Experiment 25: Burglar Alarm</b>	<b>14</b>
<b>Experiment 26: Relay as an Oscillator</b>	<b>18</b>
Momentary Push Button Switch	18
Applications	30

## 12. Diode

33

Introduction	35
<b>Experiment 27: To Learn How a Diode Works</b>	<b>37</b>
History of Diodes	39
Formation of Diode	39
Forward Biasing	43
Reverse Biasing	44
Types of Diodes	45
<b>Experiment 28: Low Resistance Path Using a Diode</b>	<b>48</b>
<b>Experiment 29: Protecting a Circuit Using a Diode</b>	<b>50</b>

## 13. Logic Gates

55

Introduction	57
Gate Types	58
NOT Gate	58
OR Gate	60
AND Gate	61
NOR Gate	62
NAND Gate	63



Experiment 30: OR Gate Using Diodes	65
Experiment 31: AND Gate Using Diodes	70
Experiment 32: NOR Gate Using Diodes	74
Experiment 33: NAND Gate Using Diodes	78
Rectification	87

## 14. Zener Diode 93

Introduction	94
Experiment 34: To Learn How a Zener Diode Works	96
Experiment 35: Zener Diode as Voltage Regulator	100
V-I Characteristic Curve	107

## 15. DC Motor 109

Introduction	111
DC Motors	111
Experiment 36: DC Motor as Generator	112
Experiment 37: Surgery of DC Motor	114
Experiment 38: Controlling Speed of DC Motor	120
Motor specification	122
Motor selection	122
Current capacity	123

## 16. Transistors 125

Introduction	127
Advantages	130
Physical Construction	130
Types	130
Identification of Legs	132
Experiment 39: Identifying the Type of BJT Transistor Using a Multimeter	133
Experiment 40: Measuring the Gain of a Transistor	135
Schematic symbol	137
Basics of NPN and PNP Transistor	138



## 17. Transistor Experiments 142

<b>Experiment 41:</b> B-E Junction as Diode	143
<b>Experiment 42:</b> Transistor as Amplifier and Switch	145
<b>Experiment 43:</b> Touch Activated Switch Using a Transistor	158
<b>Experiment 44:</b> Darlington Pair	160
Calculating Base and Collector Current in a Darlington Pair	162
Effective Transistor	163
Working of a BJT Transistor in Different Operating Regions Through Mathematics	164
<b>Experiment 45:</b> Automatic Night Lamp	167
<b>Experiment 46:</b> Transistor as Blinker (LED Flasher)	170
Esaki (Tunnel) Diode	172
<b>Experiment 47:</b> Alternate Blinking of LEDs using Transistors	174
<b>Experiment 48:</b> OR Gate Using Transistors	176
<b>Experiment 49:</b> AND Gate Using Transistors	182
<b>Experiment 50:</b> NOR Gate Using Transistors	190
<b>Experiment 51:</b> NAND Gate Using Transistors	197
<b>Experiment 52:</b> Transistor as an Inverter (NOT Gate)	204
<b>Experiment 53:</b> H-Bridge	208

## 18. Signals 213

---

Introduction	215
Types of Signals	216
Digital Signal	218
Analog Signal	221
Converting a Binary Number into a Decimal Number	222
Need of Digital Signals	223
Pulse	223
Wave	224
AC Sine Wave	224
Pulsed DC Wave	225
AC Square Wave	225
AC Triangle Wave	226



Complex Sine Wave	226
DC Ramp Wave	226
Voice	227
Different Wave Generated on CRO	227
Difference between Electrical and Electronics	228
Active and Passive Components in Electronics	228