



Mand Labs
step by step



Electronic Series, KIT-1



Experiment:

Kirchhoff's Voltage Law




Mand Labs

step by step



Circuit Diagram

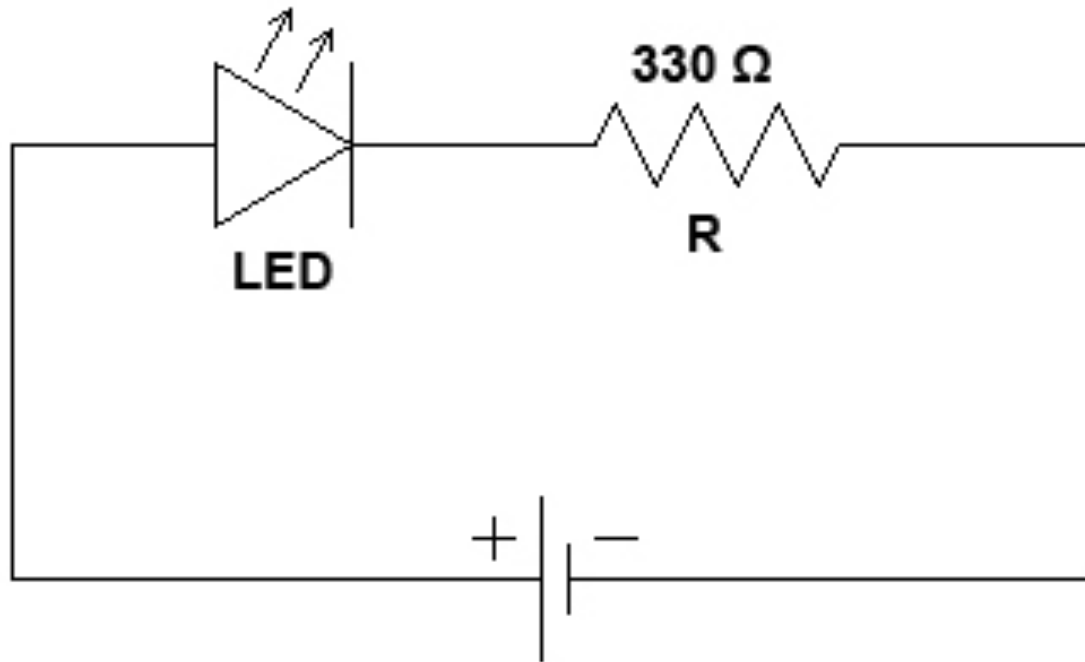

Mand Labs
step by step



Materials Required


- i. Breadboard - 1
- ii. LED - 1
- iii. Resistor: $330\ \Omega$ - 1
Colour Code: 330 Ω - Orange Orange Brown Gold
- iv. 9 V Battery - 1
- v. Connecting Wire Pieces






Step No. 1

Take a breadboard.

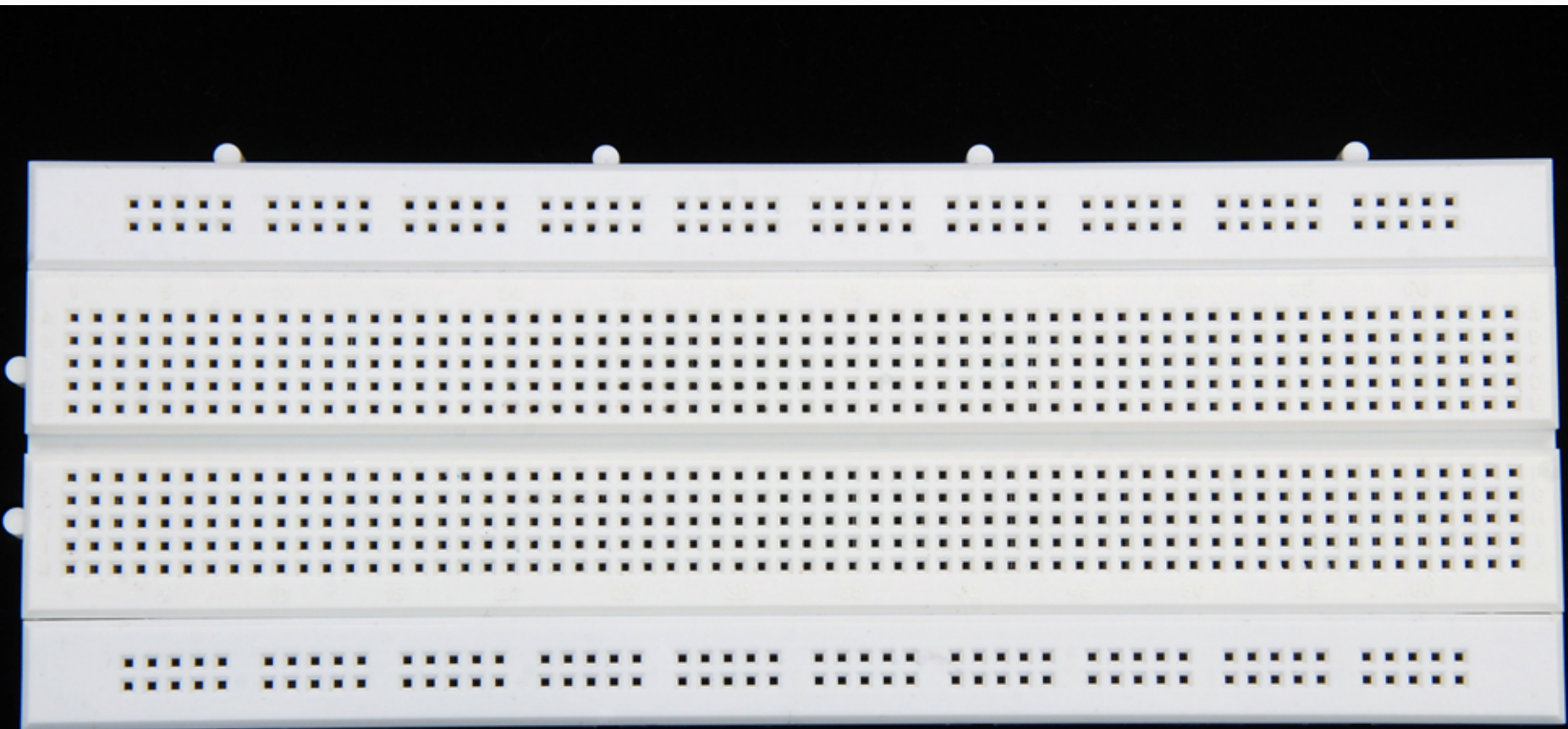


Step No. 2

Connect a 9 V battery on the breadboard.

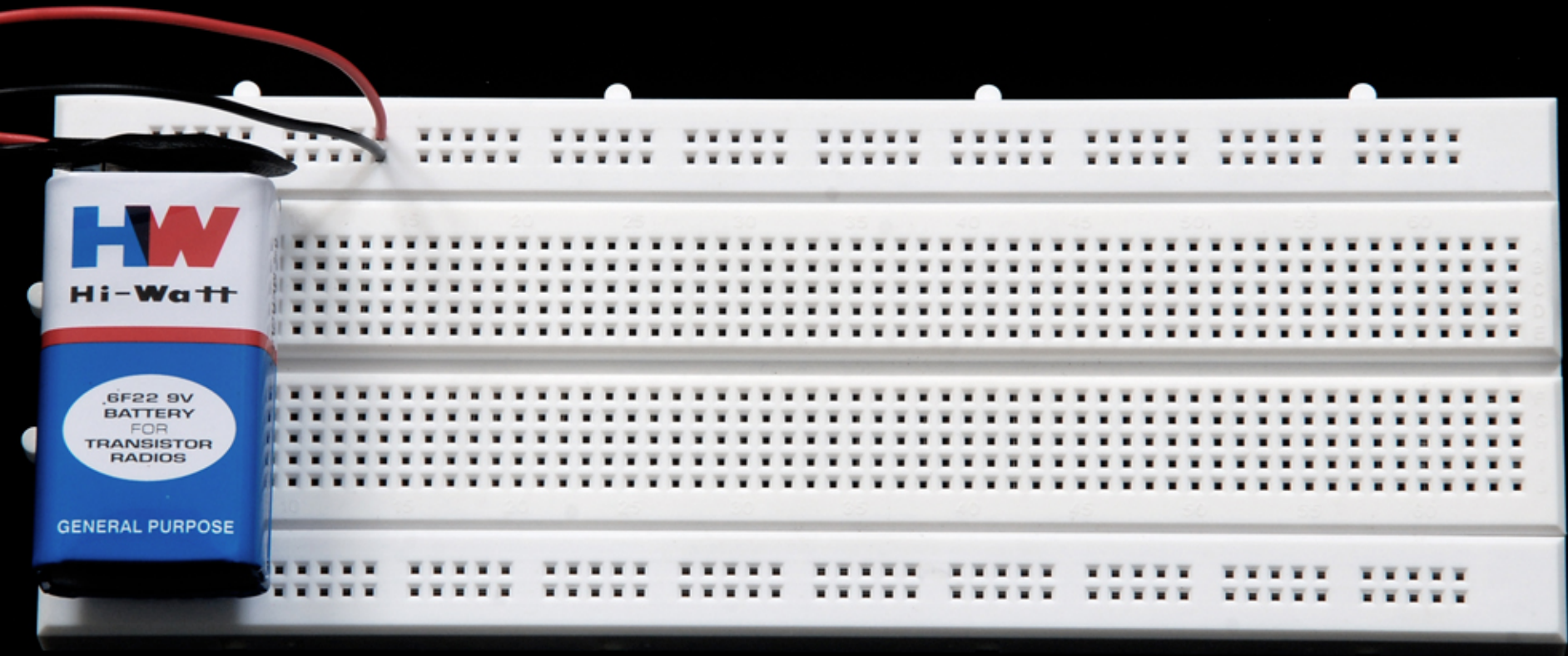


Step No. 3

Connect an LED on the breadboard.

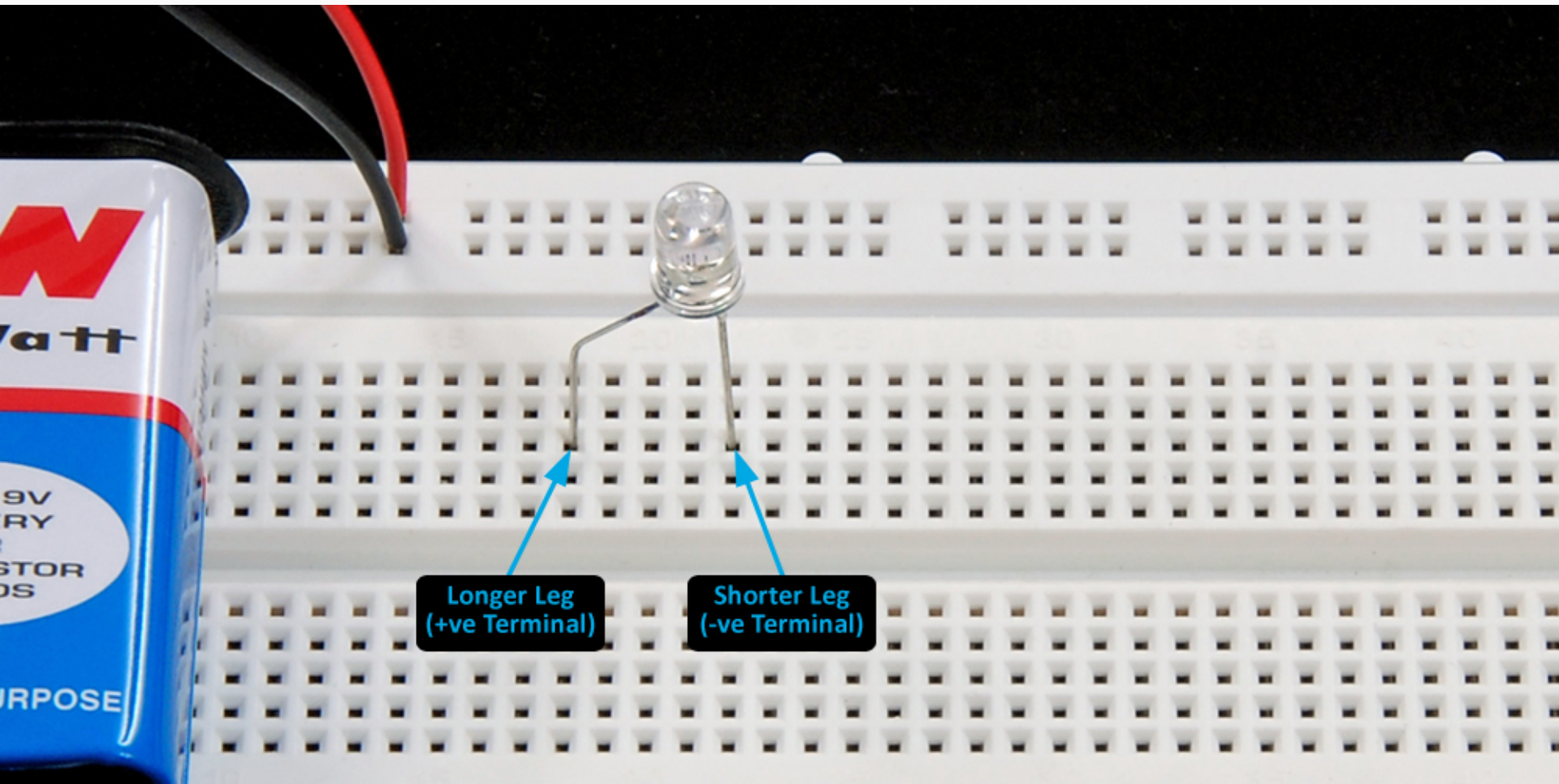


Step No. 4

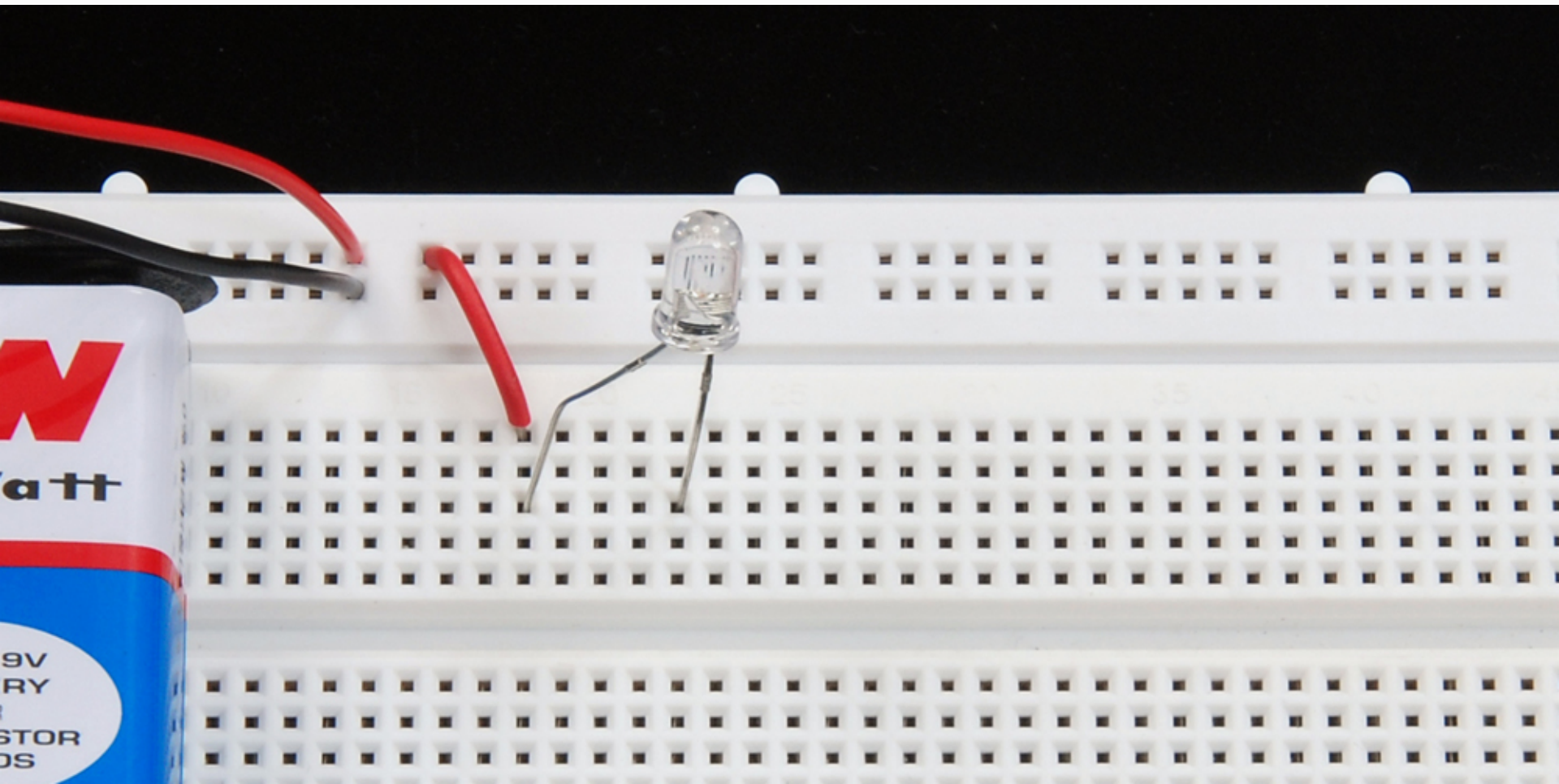Connect the positive terminal of the LED to Vcc (positive terminal of the battery) with a connecting wire (red).




Step No. 5

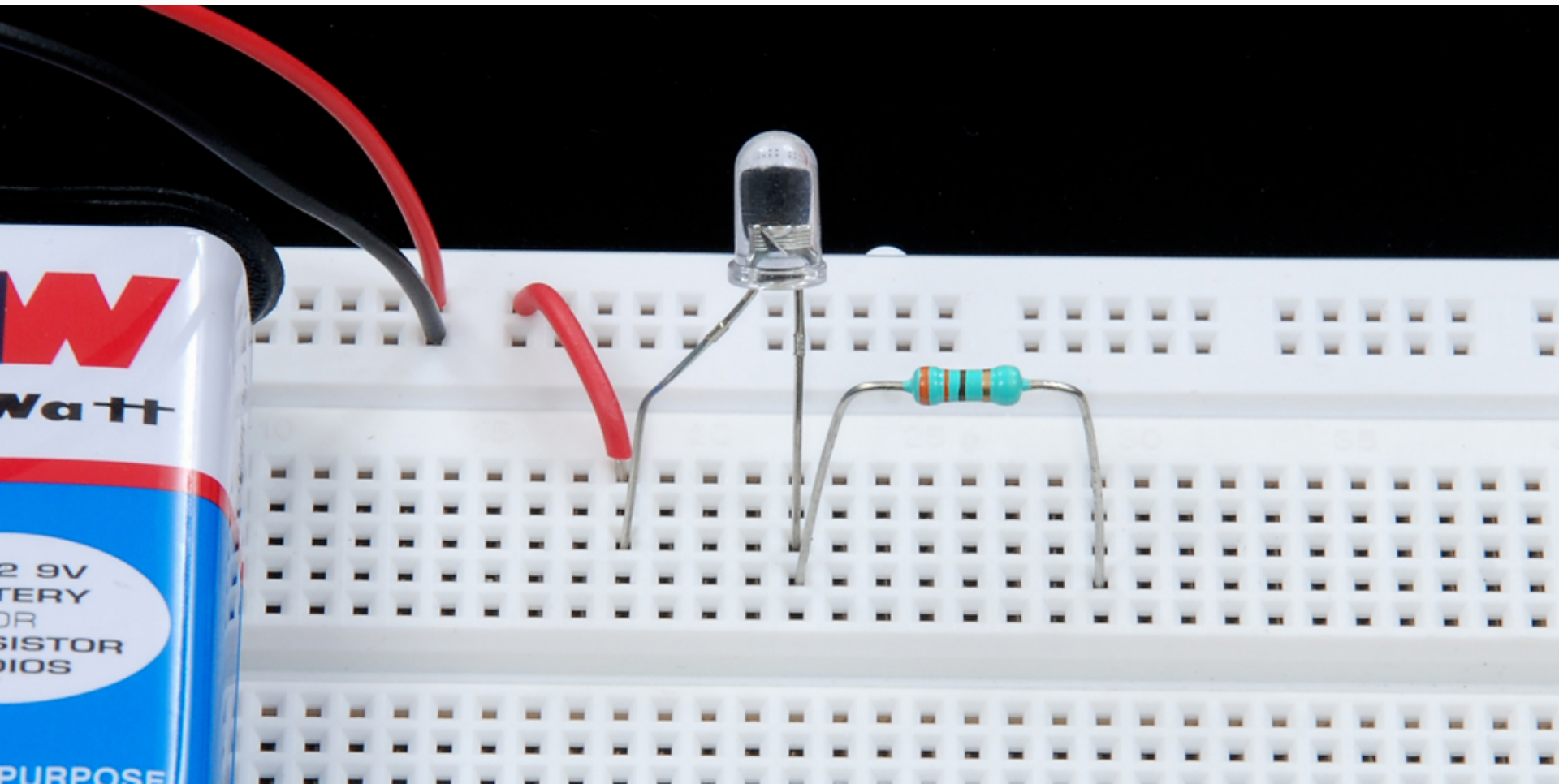Connect one leg of a 330 Ω resistor to the negative terminal of the LED. Connect the other leg of the resistor to any different column of the breadboard.




Step No. 6

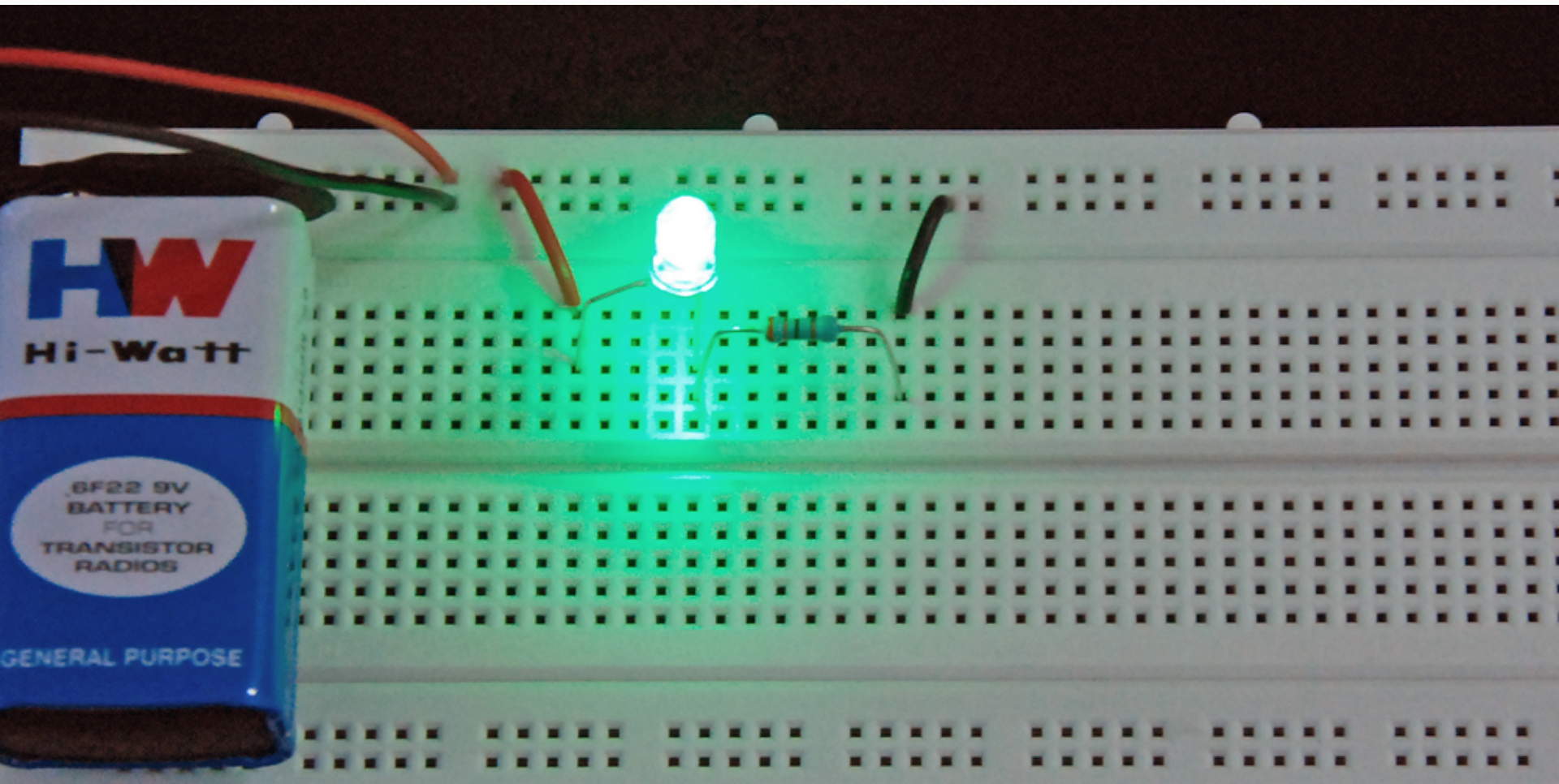Connect the other leg of the resistor to ground (negative terminal of the battery).



Complete Circuit

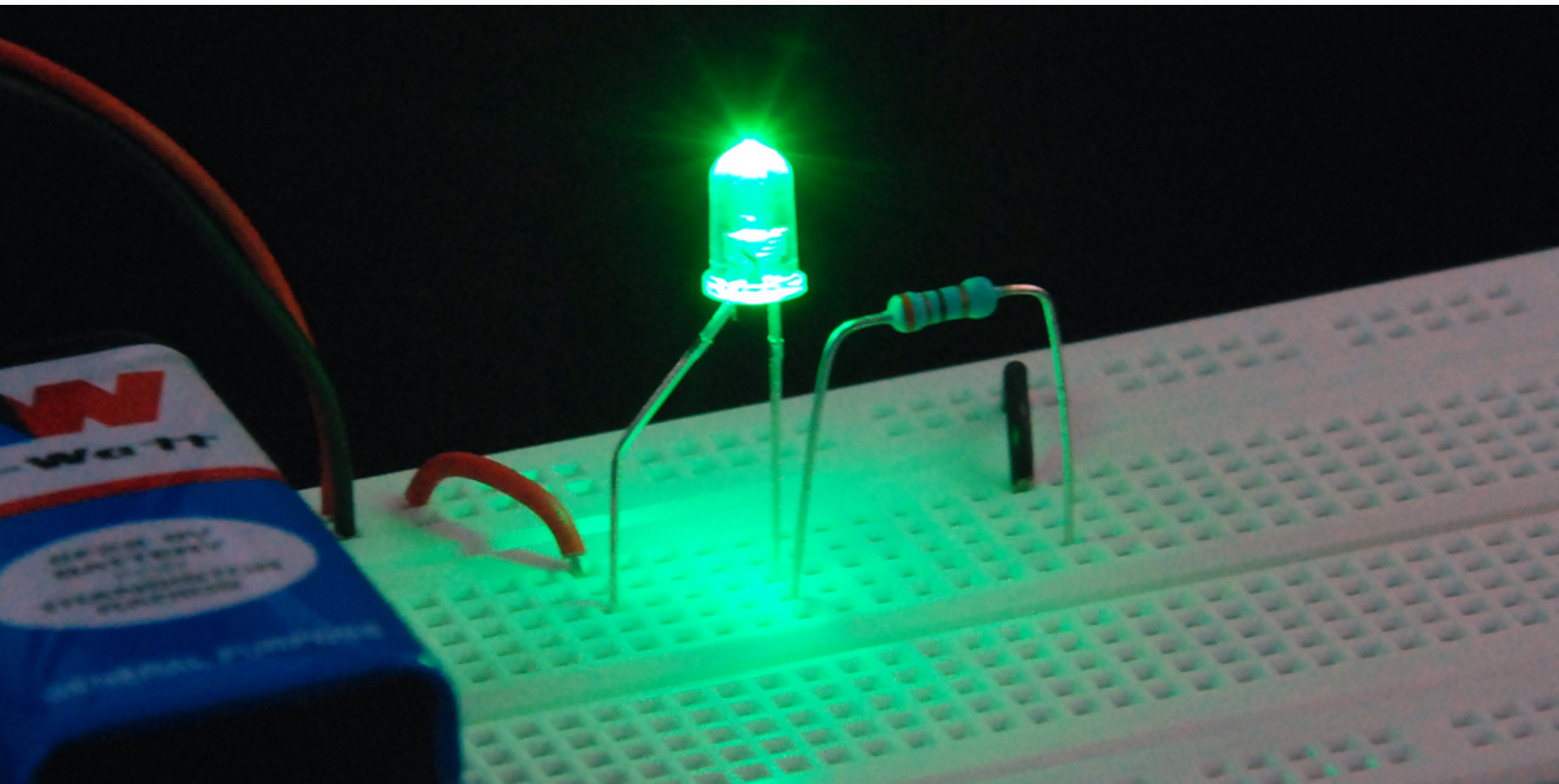The LED glows. Hence, the circuit is complete. Now we will measure the voltages across the LED and the resistor.




Step No. 7

Now take out the multimeter and rotate its dial to 20 V DC.




Step No. 8

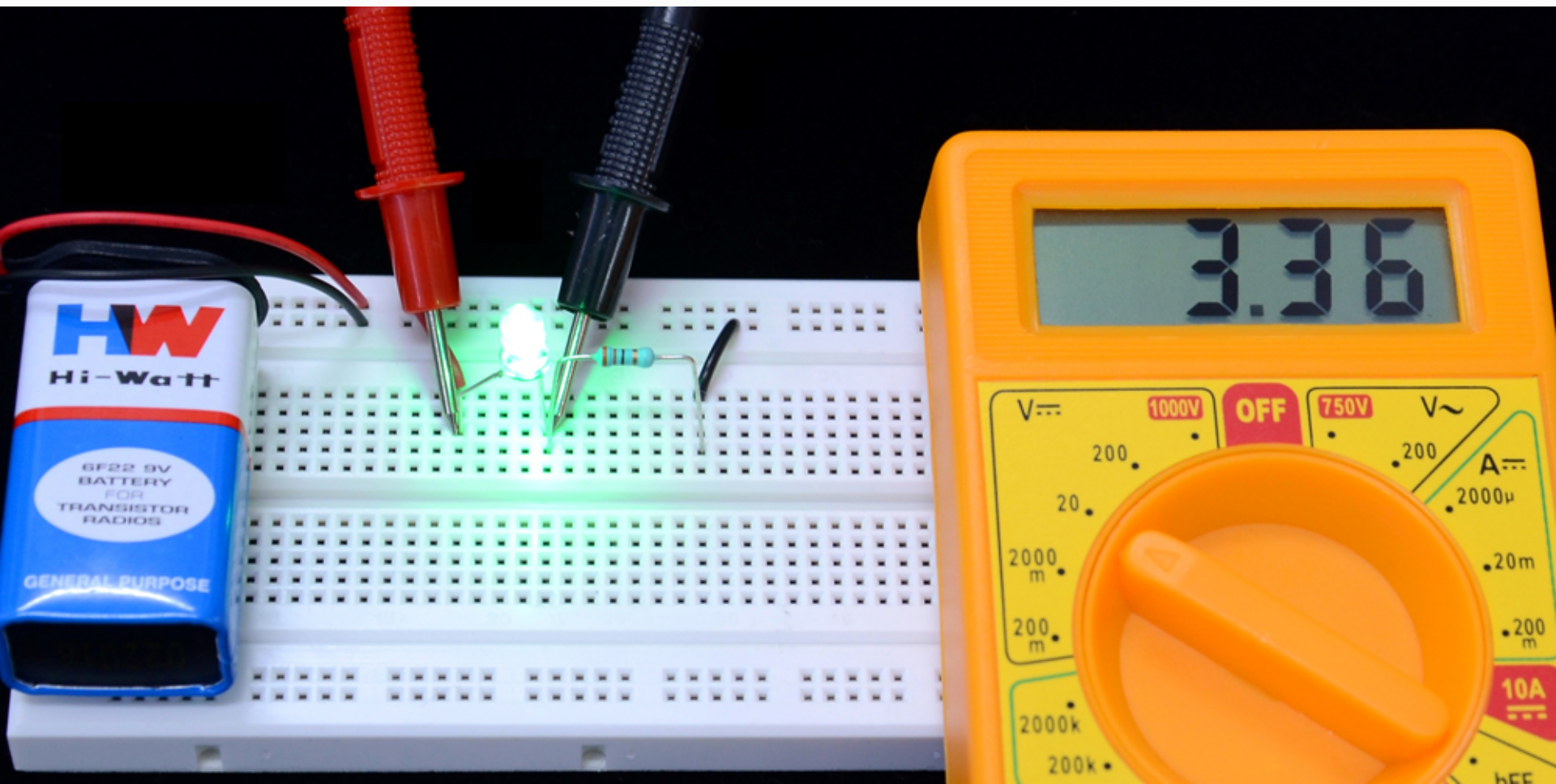To measure voltage across the LED, connect the red and black probes to the positive and negative terminals of the LED, respectively. Let us call this voltage V_1 . So, $V_1 = 3.36 \text{ V}$.



Step No. 9

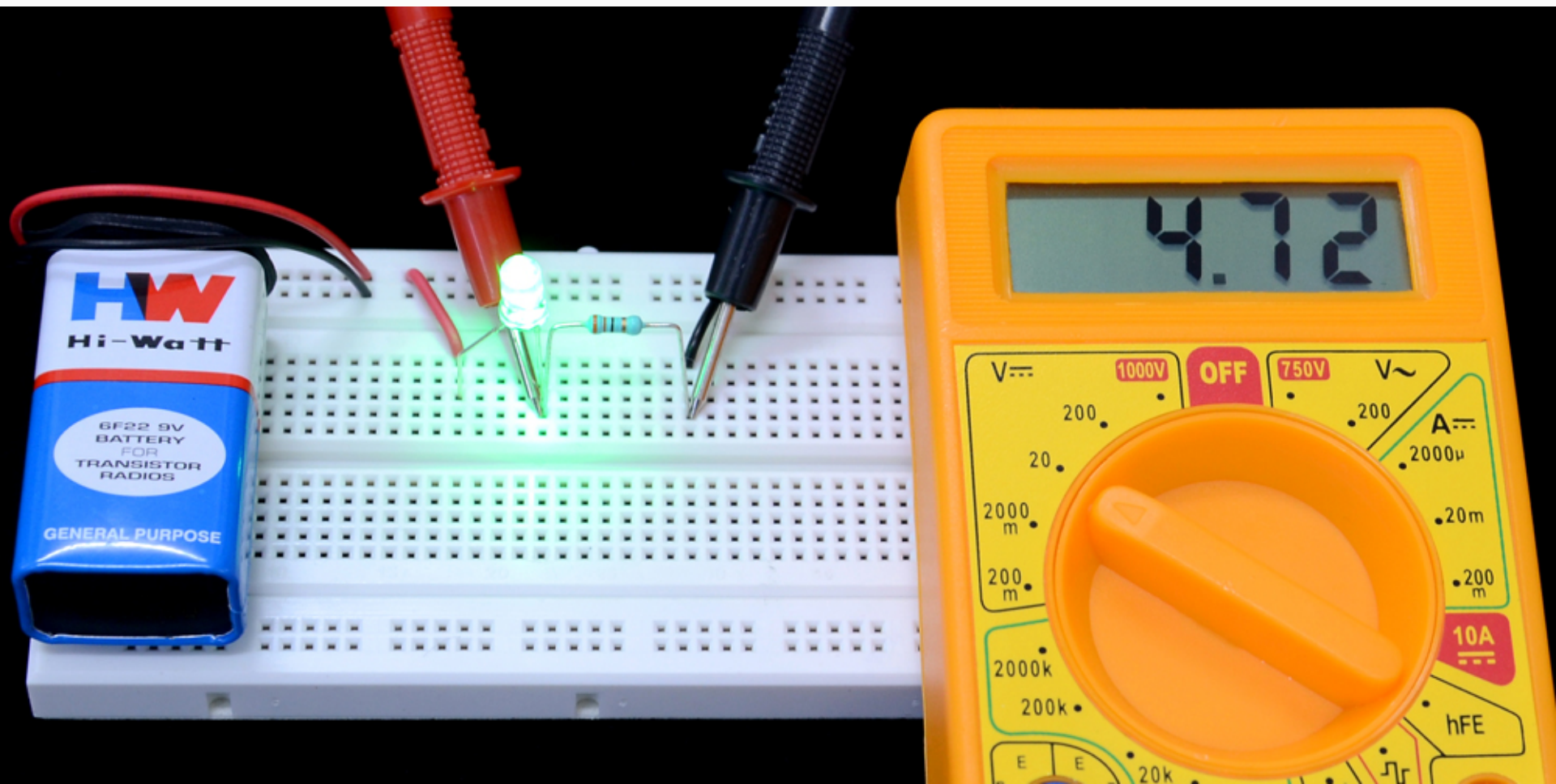Similarly, measure the voltage across the resistor. Connect the red & black probes to the left and right legs of the resistor, respectively. Let us call this voltage V_2 . So, $V_2 = 4.72 \text{ V}$.



Observation

Voltage drop across the LED, $V_1 = 3.36 \text{ V}$

Voltage drop across the resistor, $V_2 = 4.72 \text{ V}$

Note: Your readings may differ.

$$\begin{aligned}\text{Sum of voltage drops} &= V_1 + V_2 = 3.36 + 4.72 \\ &= 9.6 \text{ V} \\ &\cong \text{Battery Voltage (9 V)} \\ &\cong V_{cc}\end{aligned}$$

Result

On adding the individual voltages across all components, we will find that the total voltage supplied by the battery (source) is divided among the LED and the resistor connected in series, i.e.,

$$V_{cc} = V_1 + V_2$$

This establishes Kirchhoff's Voltage Law (KVL) which states that the total voltage drop (sum of voltage drops) in a loop is zero.

$$\text{i.e., } V_{cc} - V_1 - V_2 = 0$$



Troubleshooting Tips

- Ensure that the battery voltage is more than 6 volt.
- Ensure that the wires of the battery connector are properly inserted into the breadboard. The red wire should be inserted into the first row, and the black wire into the second row of the breadboard.
- Ensure that the LED is in working state using a multimeter.
- Ensure that the positive terminal (longer leg) of the LED is connected to Vcc, not the other way around.
- Ensure that the stripped ends of the connecting wires should be long enough to fit inside the holes of the breadboard completely.
- Ensure that there are no loose connections.




Activity

We can also extend the law for multiple components connected in series. To verify this, we will connect multiple LEDs in series in the next experiment, Series combination of LEDs.

Note: Disconnect (remove) all the components from the breadboard to build series combination of LEDs.

Circuit Diagram

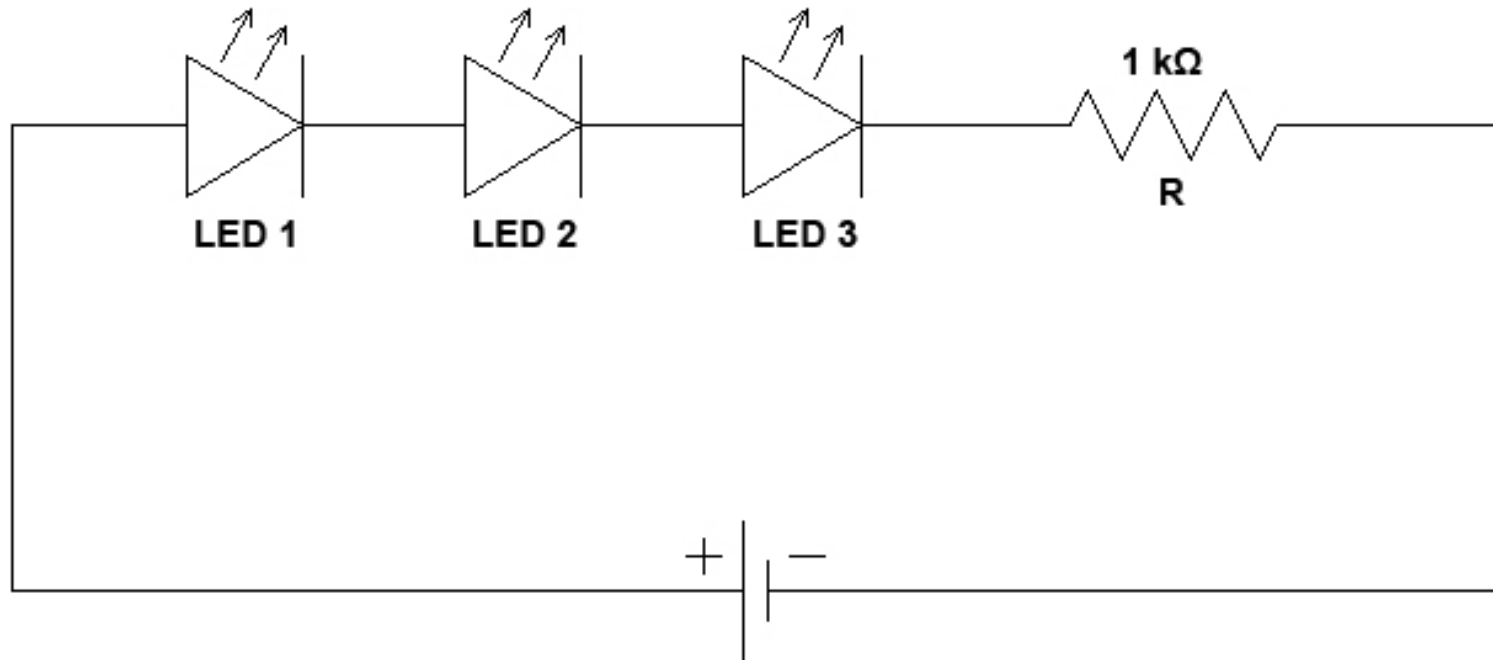

Mand Labs
step by step




Materials Required

- i. Breadboard - 1
- ii. LED - 3
- iii. Resistor: 1 k Ω - 1
Colour Code: 1 k Ω - Brown Black Red Gold
- iv. 9 V Battery - 1
- v. Connecting Wire Pieces




Step No. 10

Take a breadboard.

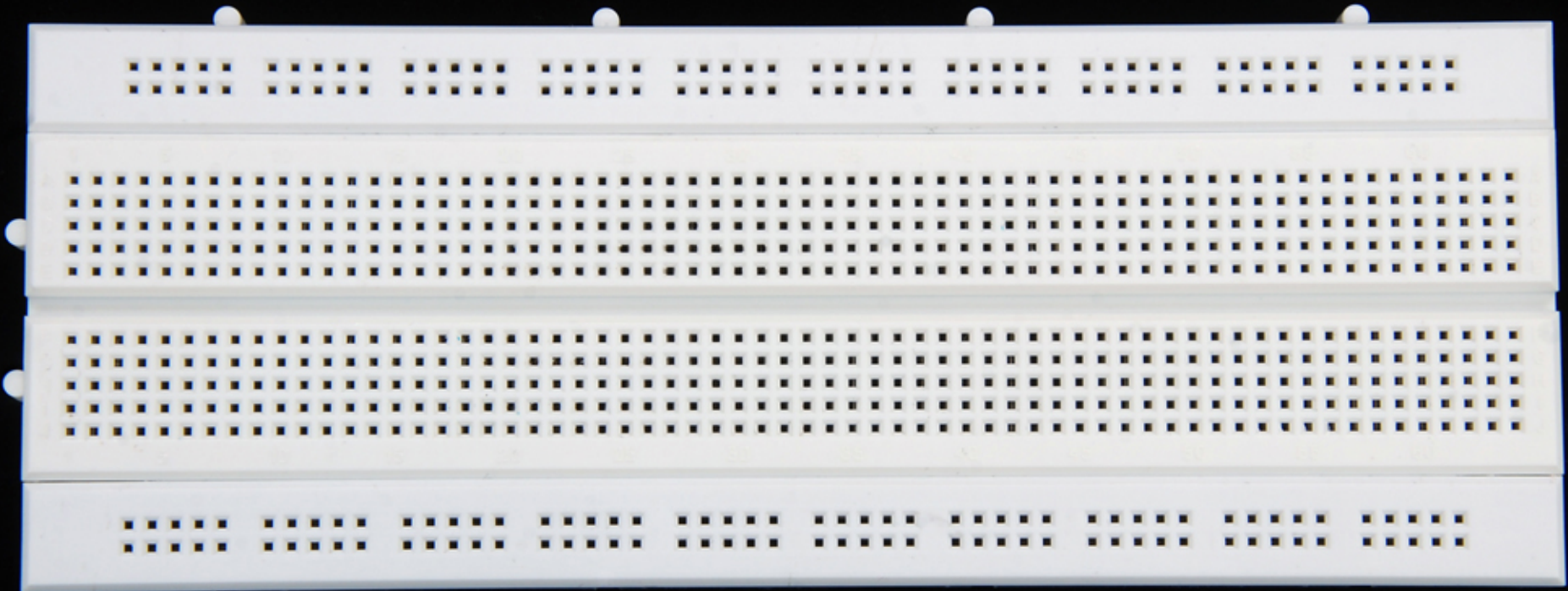


Step No. 11

Connect a 9 V battery on the breadboard.

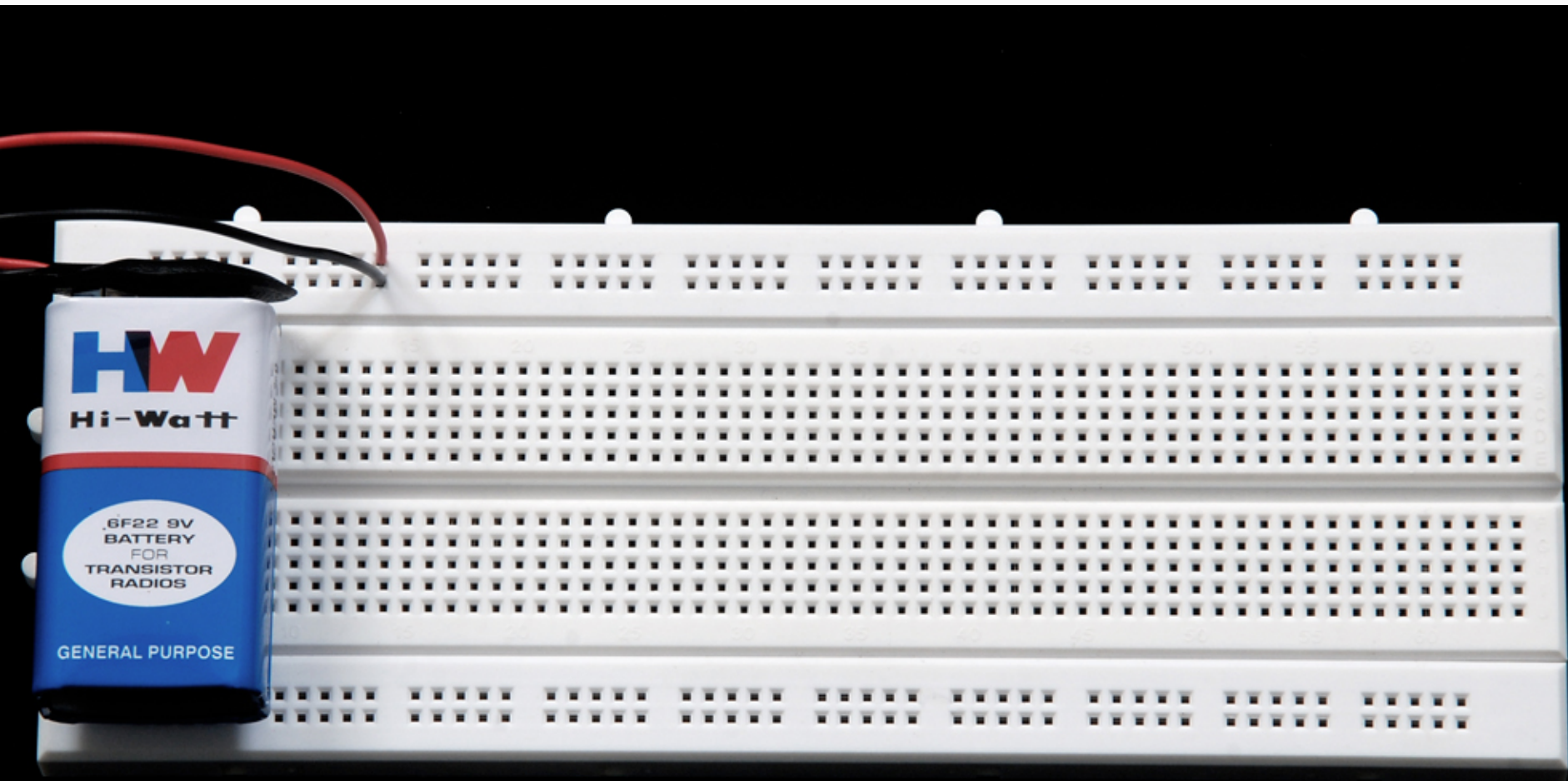


Step No. 12

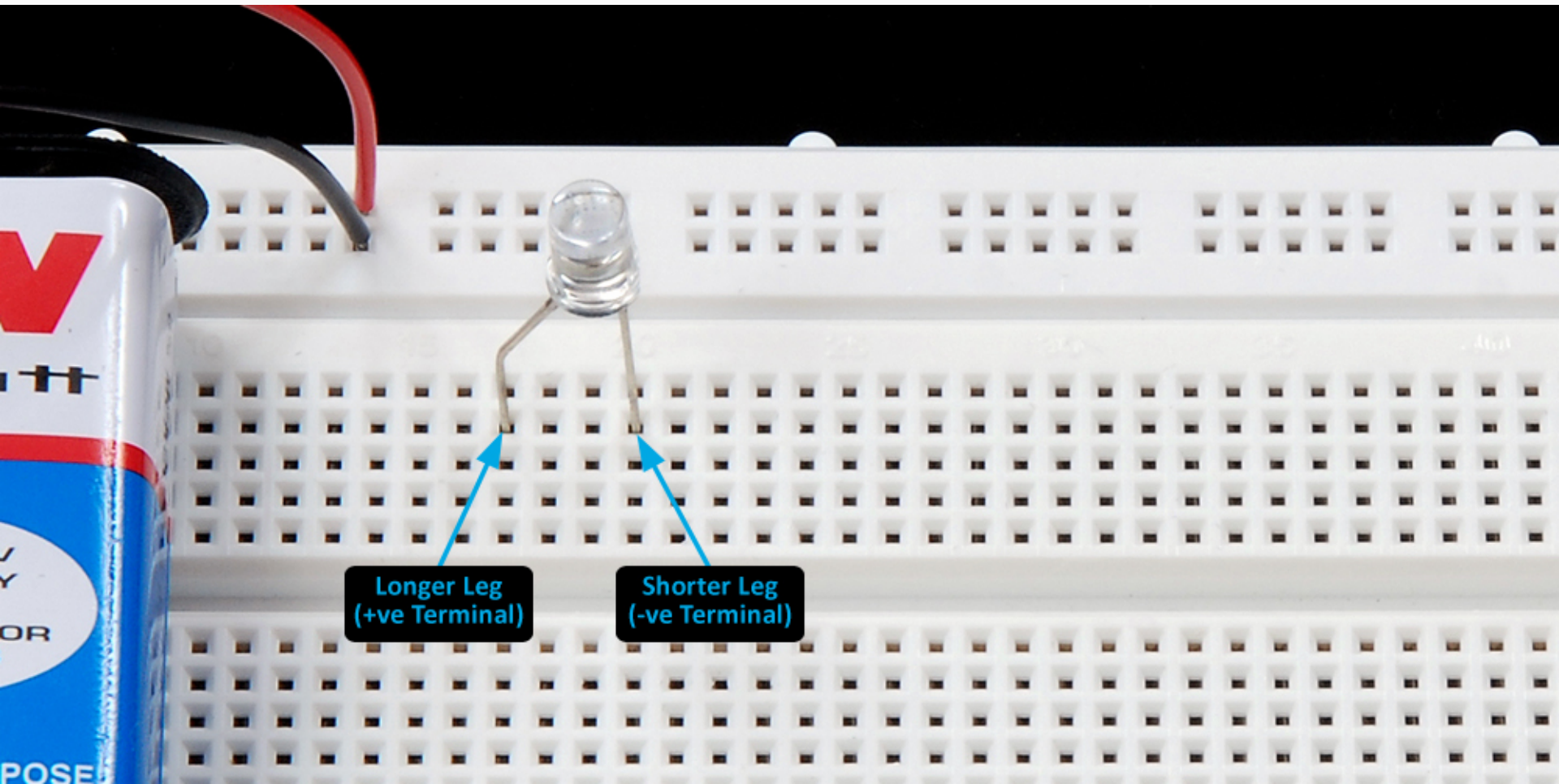Connect an LED on the breadboard. Let us assume that this is LED₁.




Step No. 13

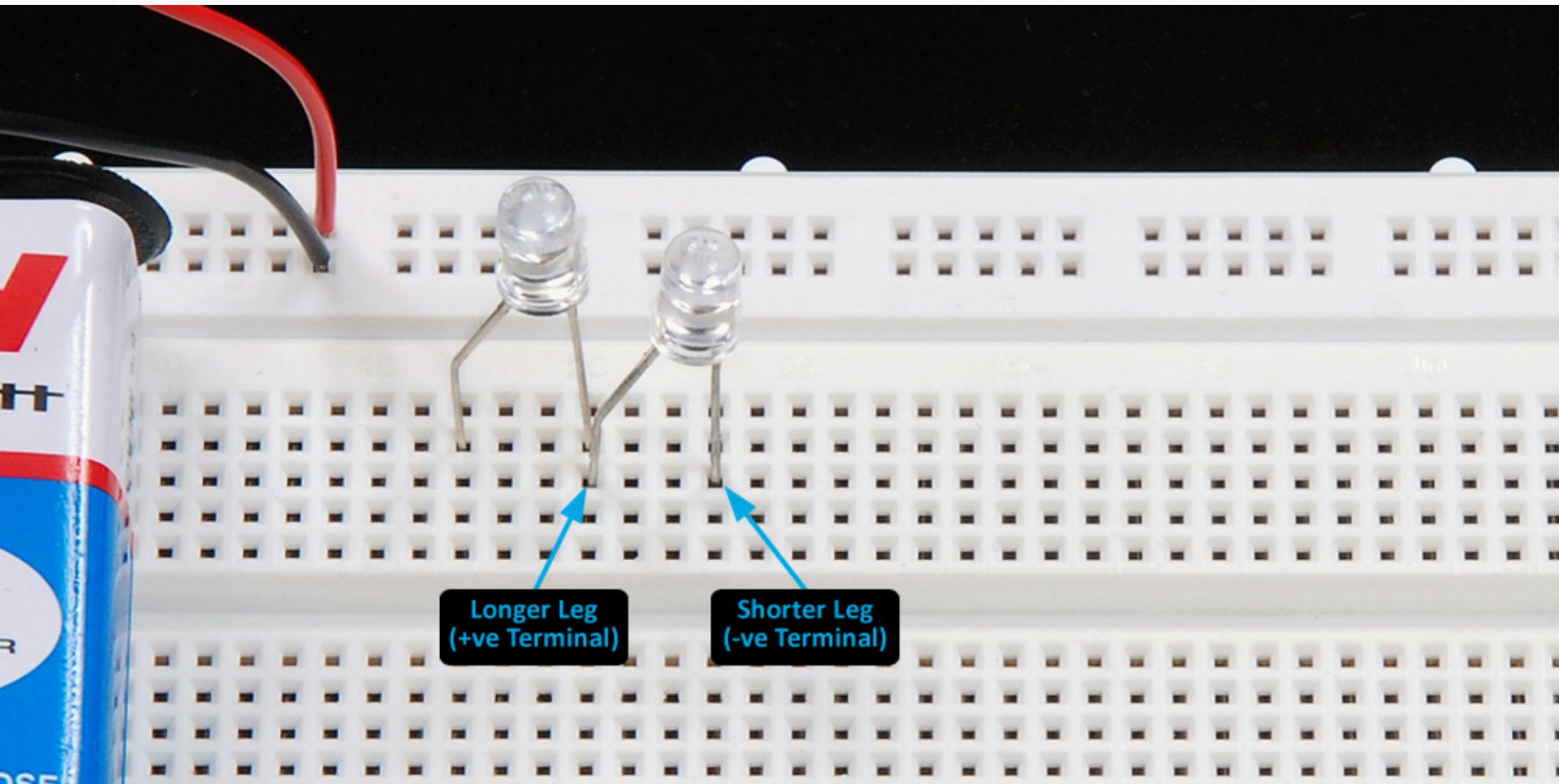To combine two LEDs in series, connect the positive terminal of LED₂ to the negative terminal of LED₁. Connect the negative terminal of LED₂ to any different column of the breadboard.




Step No. 14

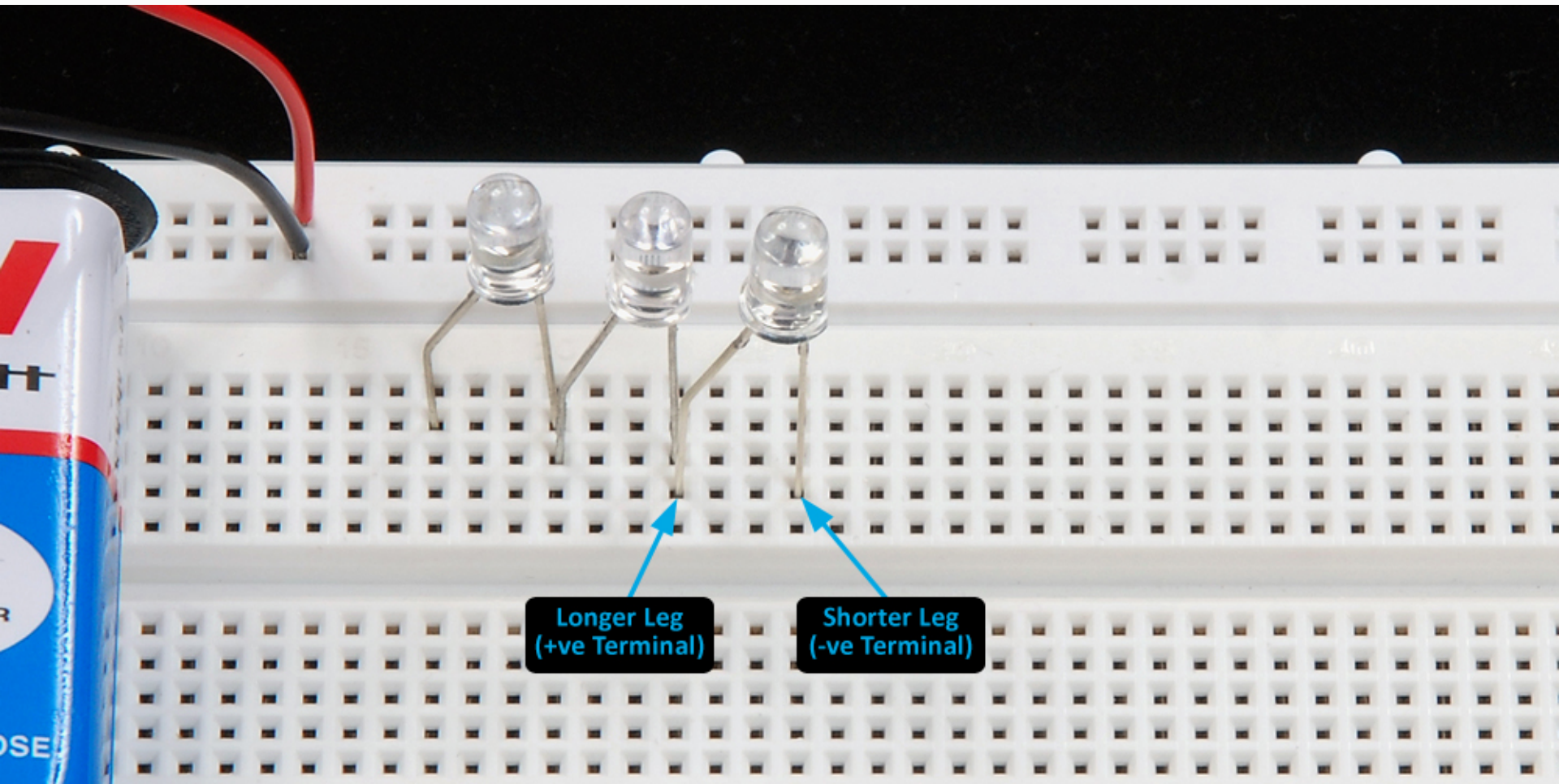Similarly, connect the positive terminal of LED₃ to the negative terminal of LED₂. Connect the negative terminal of LED₃ to any different column of the breadboard.




Step No. 15

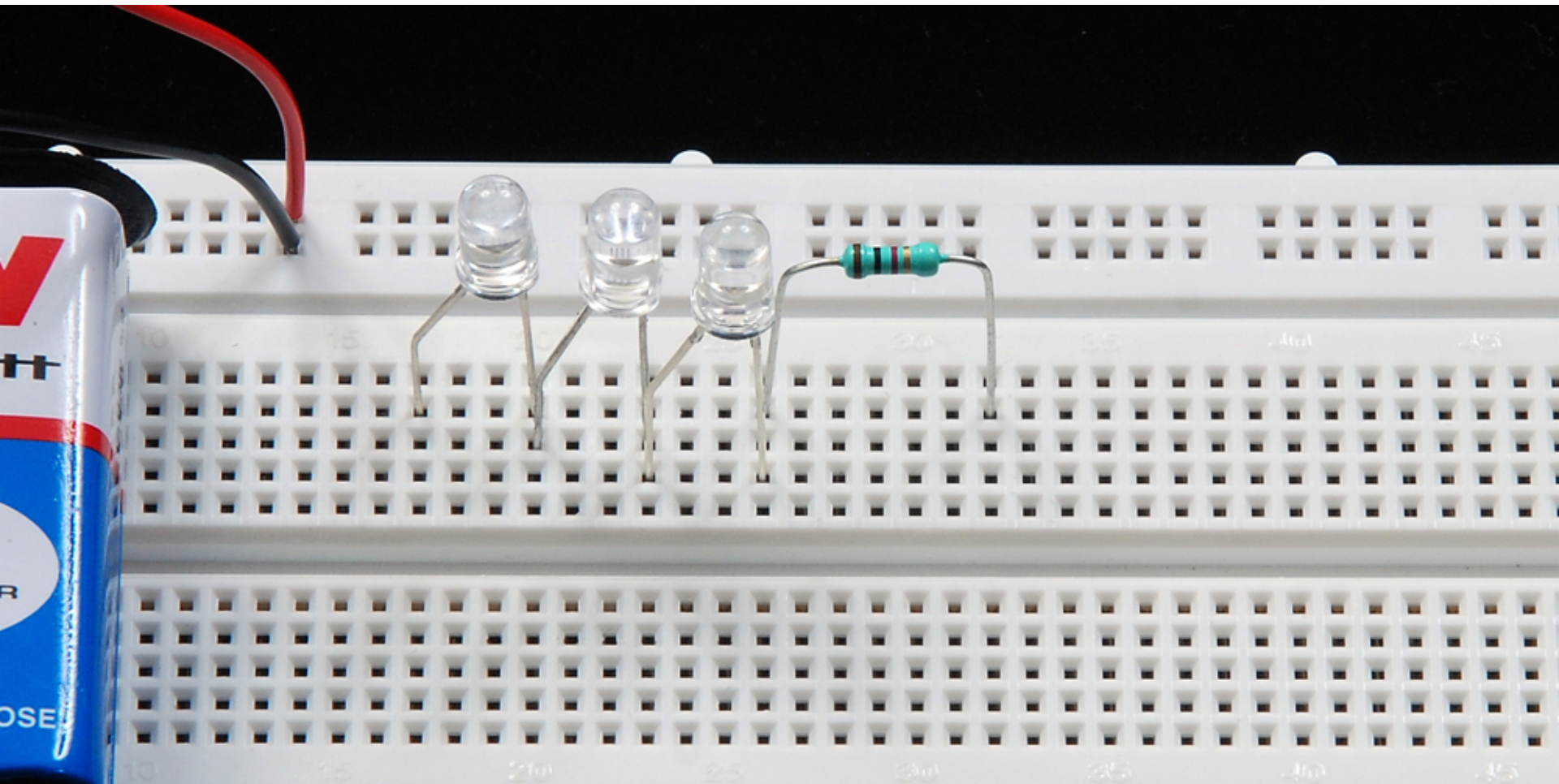Connect one leg of a 1 k Ω resistor to the negative terminal of LED₃ and its other leg to any different column of the breadboard.



Step No. 16

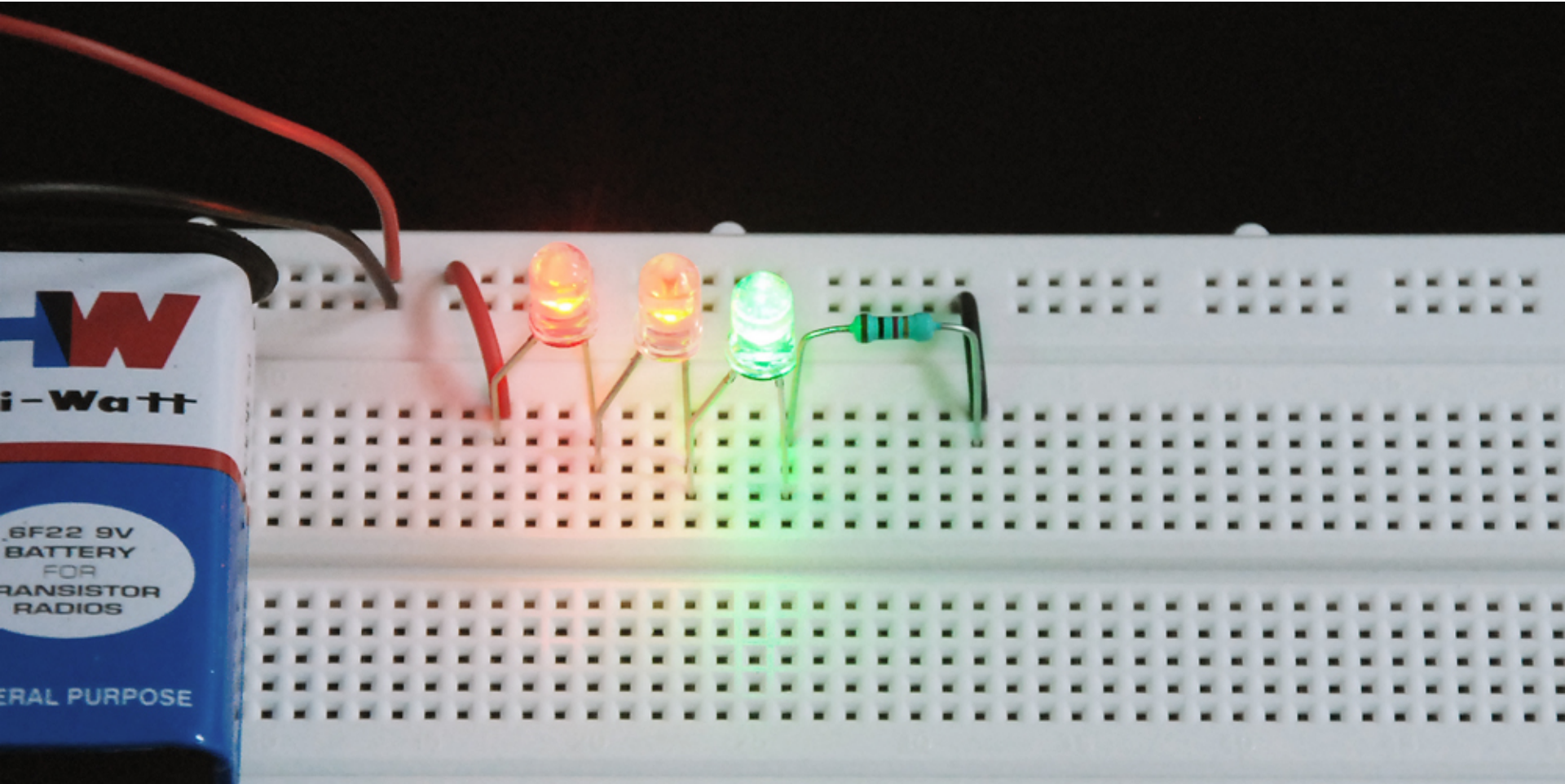Connect the positive terminal of LED₁ to Vcc and the other leg of the resistor to ground. All the LEDs glow after the circuit is complete.




Activity

Measure the voltage across each LED and the 1 k Ω resistor using a multimeter. Add up all the individual voltages and check whether the sum equals the battery voltage.


Step No. 17

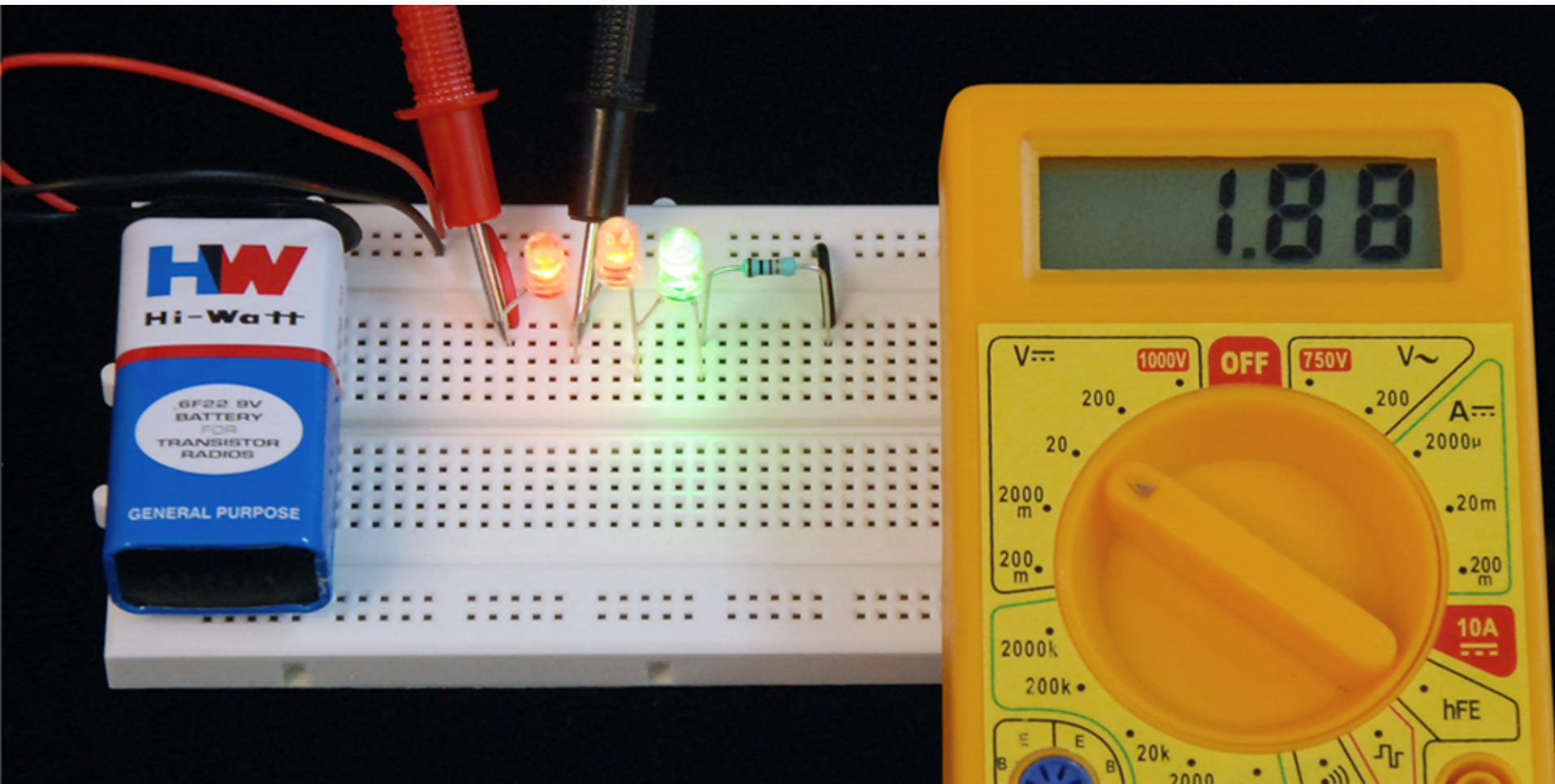To measure voltage across LED₁, rotate the multimeter dial to 20 V DC. Connect the red probe of the multimeter to the positive terminal of LED₁ and the black probe to the negative terminal of the LED. The multimeter shows the reading; let us call it V_1 . **So, $V_1 = 1.88$ V.**




Step No. 18

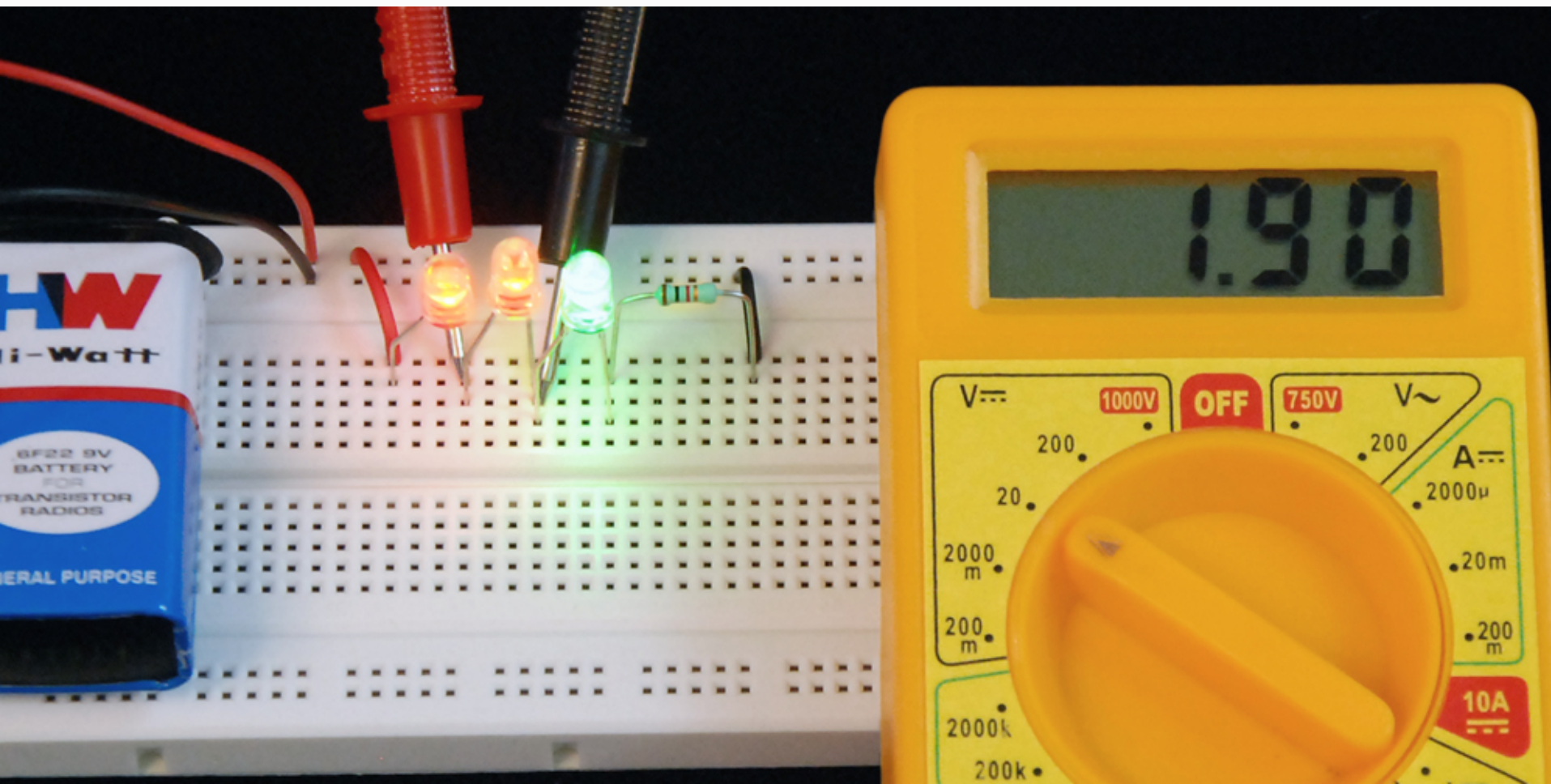To measure voltage across LED₂, connect the red probe of the multimeter to positive terminal of LED₂ and the black probe to the negative terminal of the LED. The multimeter shows the reading; let us call it V_2 . So, $V_2 = 1.9 \text{ V}$.




Step No. 19

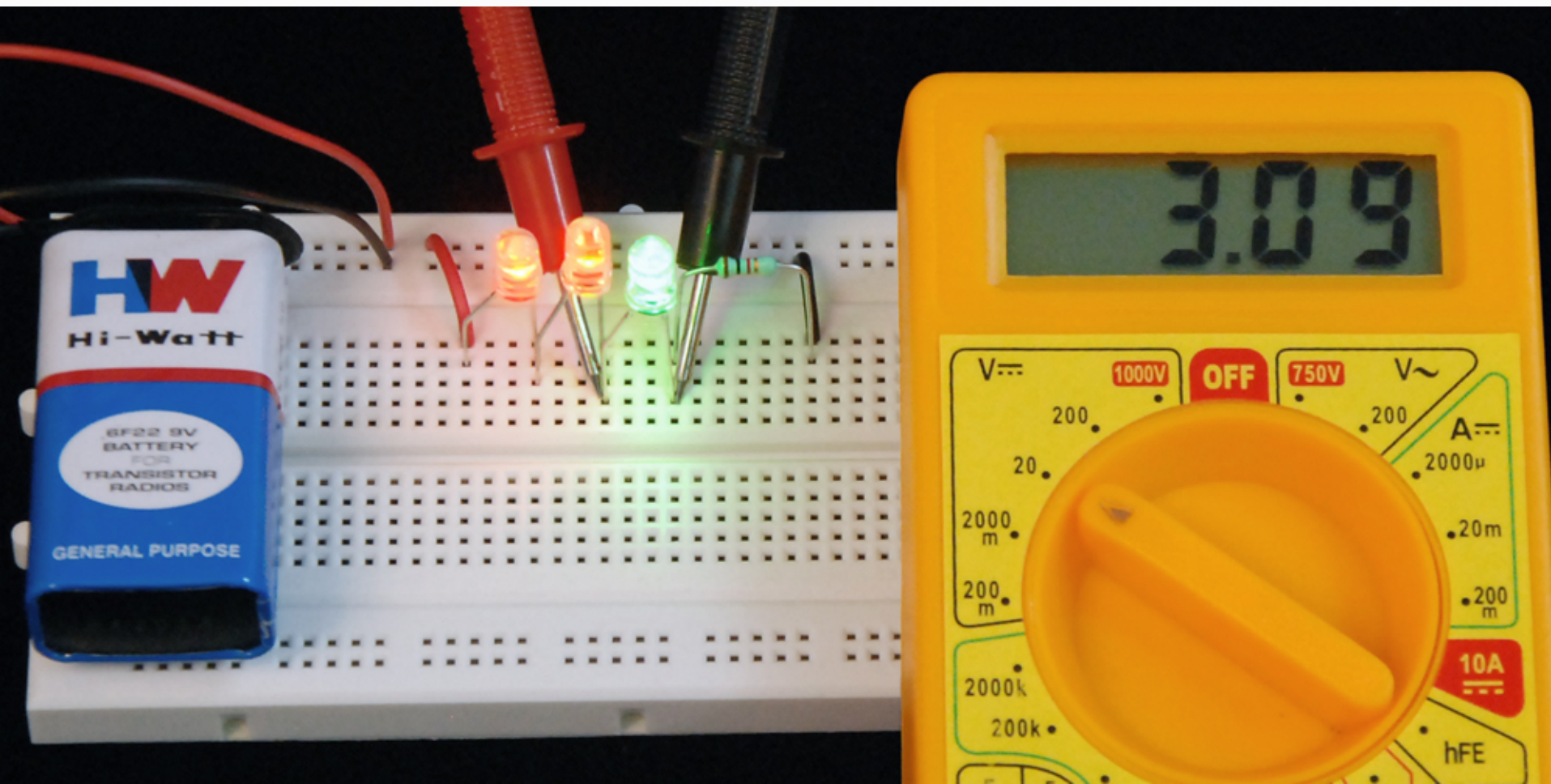To measure voltage across LED₃, connect the red probe of the multimeter to positive terminal of LED₃ and the black probe to the negative terminal of the LED. The multimeter shows the reading; let us call it V_3 . So, $V_3 = 3.09 \text{ V}$.



Step No. 20

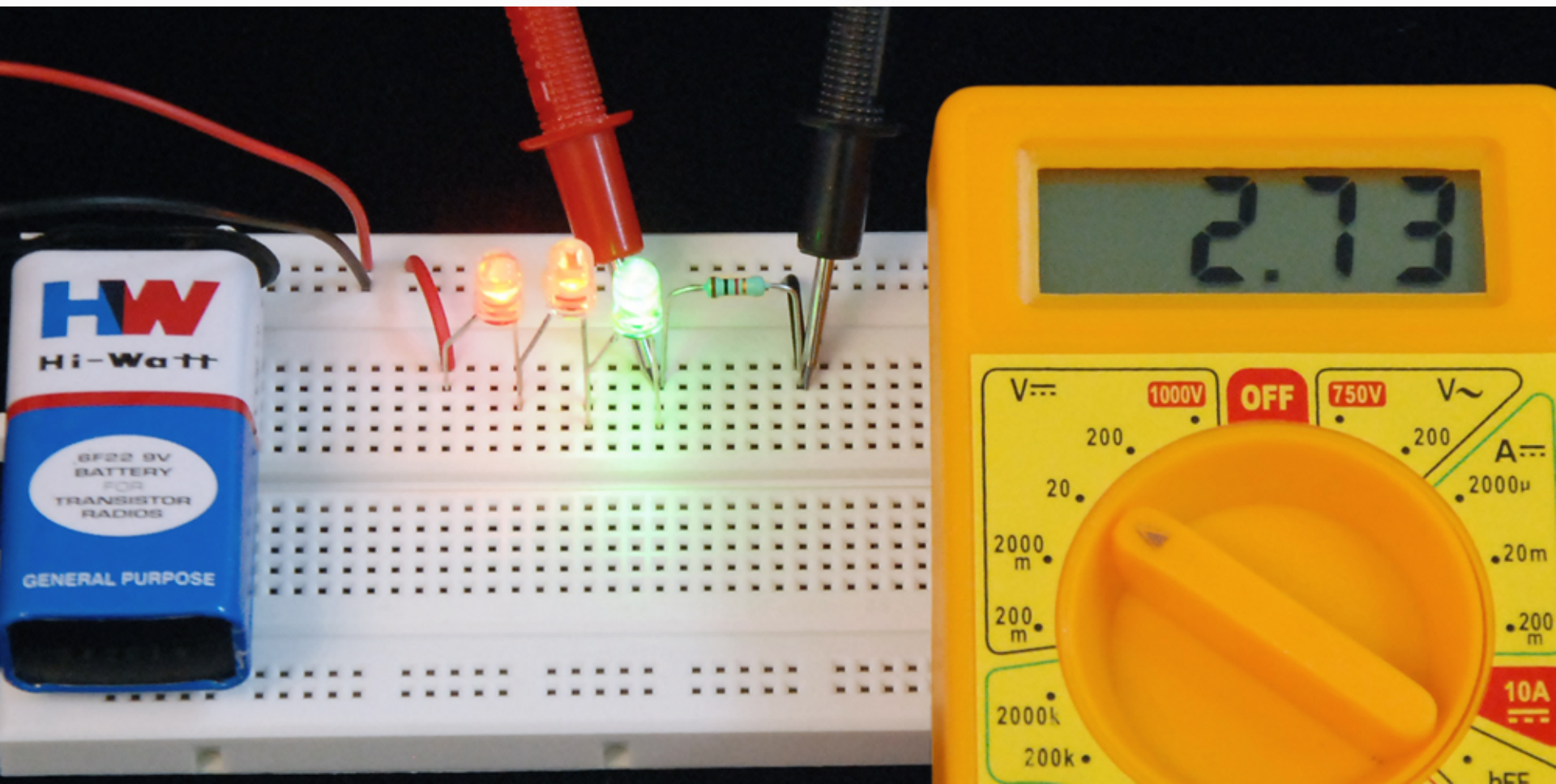To measure voltage across the resistor, connect the two probes of the multimeter across the legs of the resistor. The multimeter shows the reading; let us call it V_4 . So, $V_4 = 2.73 \text{ V}$.



Observation

On completing the circuit, all the three LEDs in series glow.

Readings

Voltage across LED₁, $V_1 = 1.88 \text{ V}$

Voltage across LED₂, $V_2 = 1.9 \text{ V}$

Voltage across LED₃, $V_3 = 3.09 \text{ V}$

Voltage across resistor, $V_4 = 2.73 \text{ V}$

$$\begin{aligned}\text{Sum} &= V_1 + V_2 + V_3 + V_4 = 1.88 + 1.9 + 3.09 + 2.73 \\ &= 9.6 \text{ V} \\ &\cong \text{Battery Voltage} \\ &\cong V_{cc}\end{aligned}$$

Result

On adding the individual voltages across all components, we will find that the total voltage supplied by the battery(source) is divided among all the components in series, i.e.,

$$V_{cc} = V_1 + V_2 + V_3 + V_4$$

This establishes Kirchhoff's Voltage Law (KVL) which states that the total voltage drop (sum of voltage drops) in a loop is zero.

$$\text{i.e., } V_{cc} - V_1 - V_2 - V_3 - V_4 = 0$$



Troubleshooting Tips

- Ensure that the battery voltage is more than 6 volt.
- Ensure that the wires of the battery connector are properly inserted into the breadboard. The red wire should be inserted into the first row, and the black wire into the second row of the breadboard.
- Ensure that all the LEDs are in working state using a multimeter.
- Ensure that the positive terminal of LED₁ is connected to Vcc.
- Ensure that the positive terminal of LED₂ is connected to the negative terminal of LED₁.





Troubleshooting Tips

- Ensure that the positive terminal of LED₃ is connected to the negative terminal of LED₂.
- Restrict the circuit to the first half of the breadboard. To provide Vcc and ground with connecting wires, use only first 25 holes of the first and second row of the breadboard.
- Ensure that the stripped ends of the connecting wires should be long enough to fit inside the holes of the breadboard completely.
- Ensure that there are no loose connections.



Project Report

To write project report, refer the following experiments from the manual:

- a) Glowing an LED
- b) Series Combination of LEDs

In the report, do include the following:

- a) Circuit diagram, Circuit Explanation
- b) Final circuit picture
- c) Pictures of 'Multimeter readings': Step No. 17, Step No. 18, Step No. 19 and Step No. 20
- d) Observation
- e) Reasoning (if any)
- f) Result (if any)
- g) General Theory: About components used (LED, resistor, multimeter, DC battery), about series combination.



Result



Precaution



Notes



Circuit



Measure



Activity



Advantages



Modification



Do you know?



Mand Labs
step by step





Mand Labs

step by step



Electronic Series, KIT-1