

Filtering a 10 MHz TTL Square Wave into a Sinewave with a 7-Pole Chebyshev Low-Pass Filter

Device:	PRL-LPF7-12MHz			
Tested By:	Steven Kan			
Date:	27 August 2020			
Equipment:	PRL-175A-10	PRL-414B-SMA	DPO3054	HP 3585A
S/N:	ENG	1L412063	C012732	1750A02039

Introduction:

This experiment tested the ability to filter a 10 MHz TTL square wave from a PRL TTL fanout buffer into a 10 MHz sinewave, using a 7-pole Chebyshev Low-Pass filter designed for a 3 dB cutoff frequency of 12 MHz.

Methodology:

The [PRL-175A-10](#) supplies a crystal-based, 10 MHz TTL clock signal. The output was cabled into a [PRL-414B-SMA](#) fanout buffer to provide 4 identical copies. Output Q1 of the [PRL-414B-SMA](#) was measured with an **HP 3585A Spectrum Analyzer** both with and without the [PRL-LPF7-12MHz](#) filter in series. Output Q1 was then captured on an oscilloscope with the filter in series, alongside output Q2 without any filtering.

The filter, model number [PRL-LPF7-12MHz](#), was constructed using a [PRL-MNET-SMF Signal Conditioning Kit](#). Ideal component values were calculated using an [online filter calculator \(Lowpass, 7 pole, 12 MHz, 50 Ω\)](#) and then the closest standard values were used to approximate the calculated design, as follows:

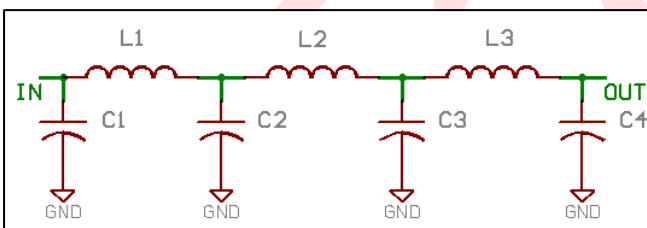


Fig. 1: Filter Schematic

Part Values				
0.1 dB Ripple Chebyshev				
Part	Calculated	Unit	Actual	Err.
L1	1.01	uH	1.0	2%
L2	1.11	uH	1.1	2%
L3	1.01	uH	1.0	2%
C1	334.62	pF	330	5%
C2	593.97	pF	593	5%
C3	593.97	pF	593	5%
C4	334.62	pF	330	5%

Table 1: Component Values


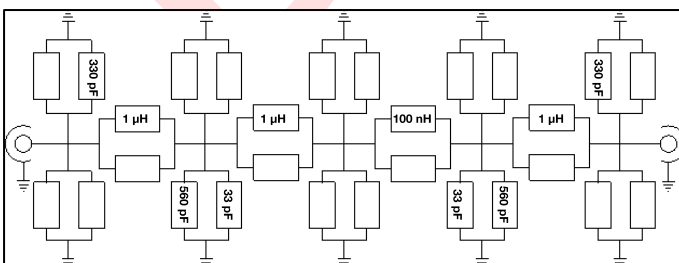



Fig. 2: Component Placement on PRL-MNET-SMF

Measurements:

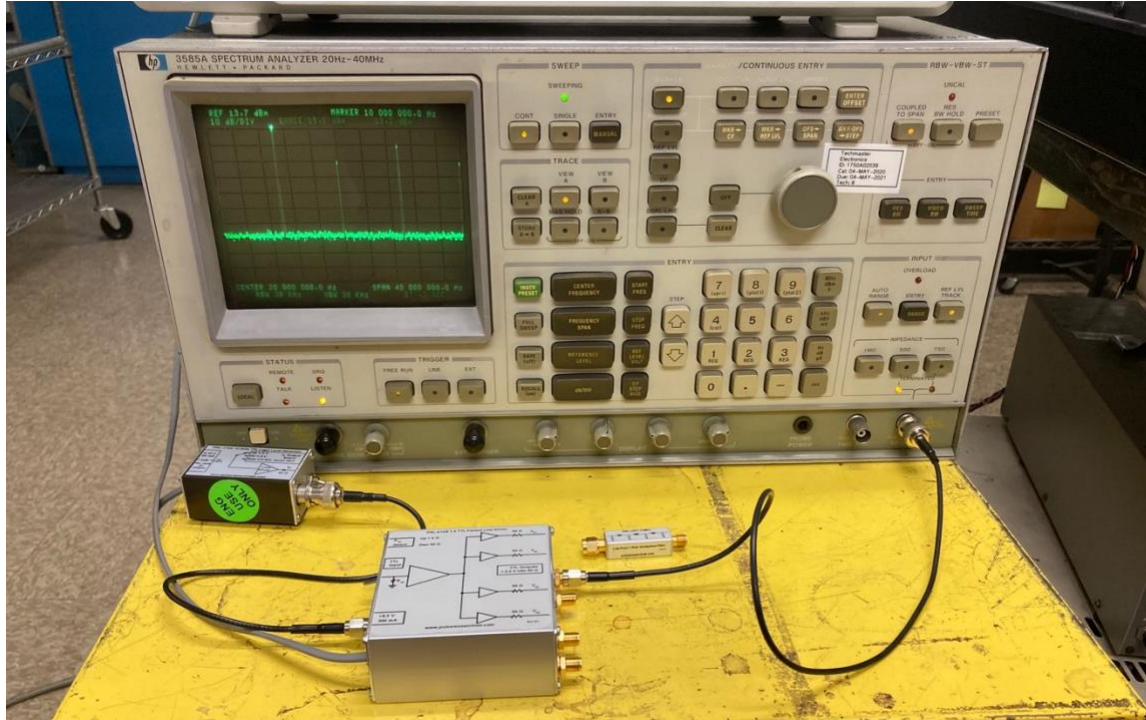


The **PRL-175A-10** produces a clean TTL square wave with good symmetry. Although the **PRL-175A-10** is capable of driving a 50 Ω load directly, the **PRL-414B-SMA** was used to re-buffer the signal, as the customer will be using this device to buffer a signal from an FPGA that will not drive a 50 Ω load. The TTL-compatible output circuit of the **PRL-175A-10** shares the same design as that of the **PRL-414B-SMA**.


With no filter in place, the power at **10 MHz** is **+13.6 dBm**, with the expected peaks at the harmonics of **20 MHz**, **30 MHz**, and **40 MHz**, as shown below. Screen captures from the **HP 3585A** were taken over GPIB via the **7470.exe HP 7470A Plotter Emulation Tool** (part of the freely available [KESFX GPIB Toolkit](#)), and then converted from PLT to PostScript format using the freely available [HP-GL Viewer](#):

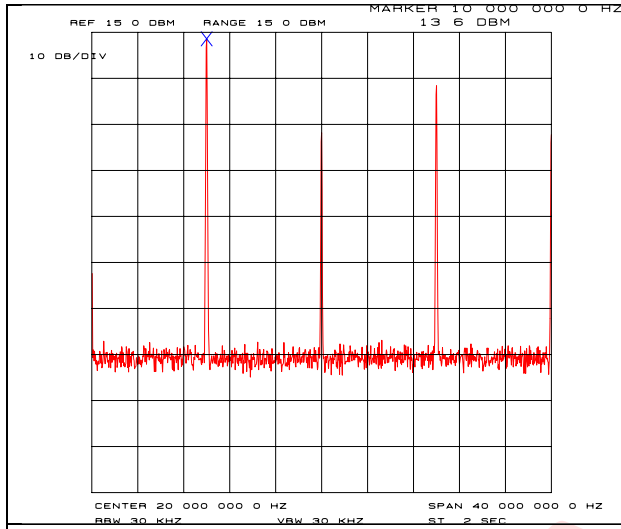


**Fig. 3: PRL-175A →PRL-414B-Q1→HP3585A
+13.6 dBm at 10 MHz**

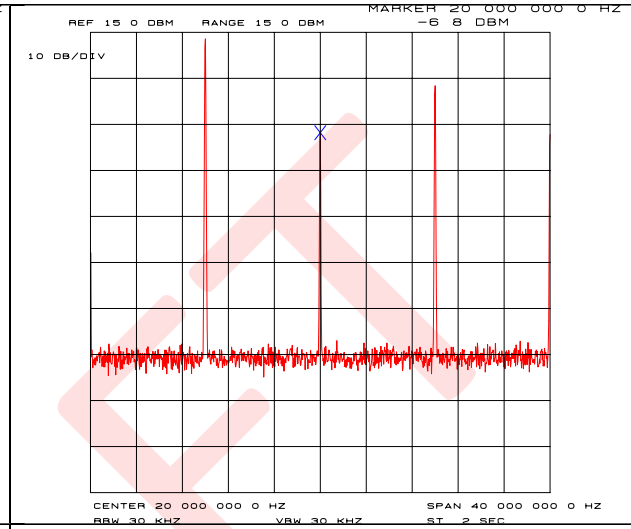

**Fig. 4: PRL-175A →PRL-414B-Q1→HP3585A
-6.8 dBm at 20 MHz**

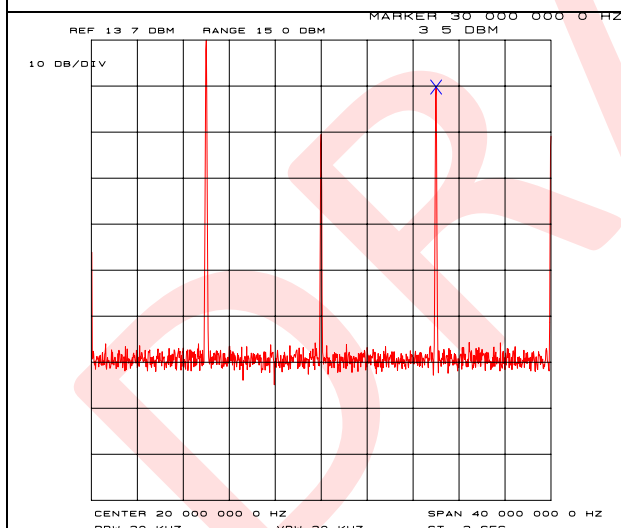


**Fig. 5: PRL-175A →PRL-414B-Q1→HP3585A
+3.5 dBm at 30 MHz**

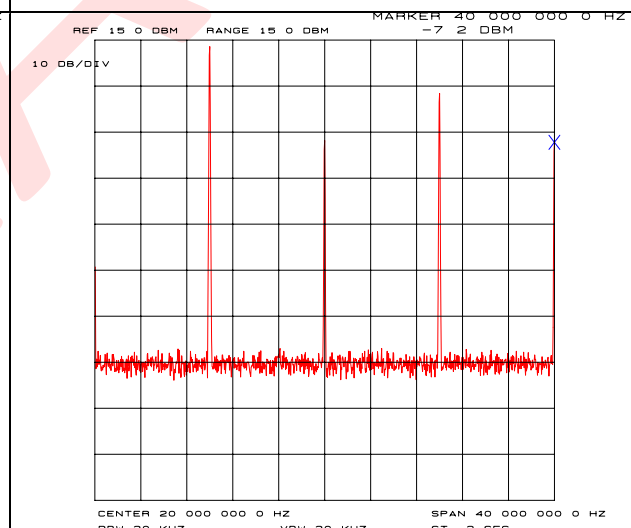


**Fig. 6: PRL-175A →PRL-414B-Q1→HP3585A
-7.2 dBm at 40 MHz**

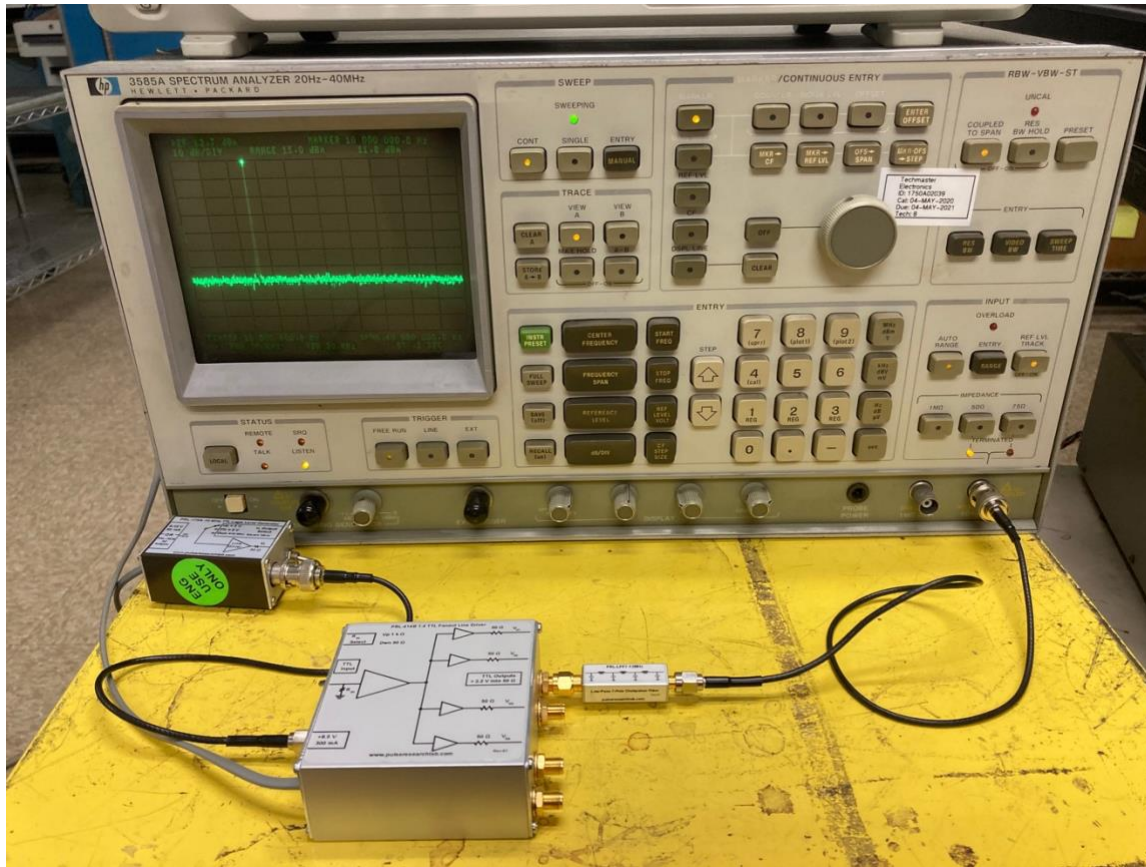With the baseline established, we installed the filter directly onto the output of the **PRL-414B-SMA**:




DR


The power at the fundamental **10 MHz** frequency is slightly attenuated down to **+11.7 dBm**, and the power at the harmonics is reduced to within the noise floor of the measurement setup, approximately -60 dBm:

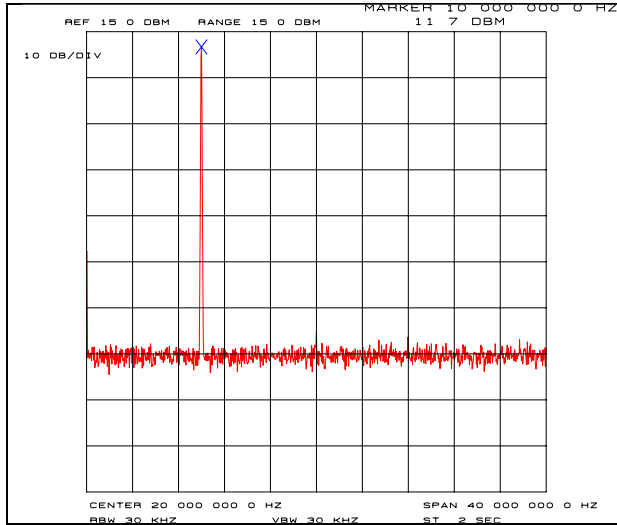


**Fig. 7: PRL-175A →PRL-414B-Q1→
PRL-LPF7-12MHz→HP3585A
+11.7 dBm at 10 MHz**

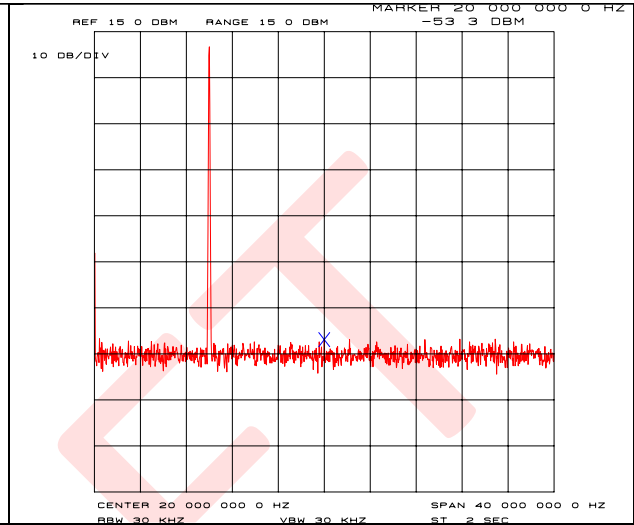

**Fig. 8: PRL-175A →PRL-414B-Q1→
PRL-LPF7-12MHz→HP3585A
-53.3 dBm at 20 MHz**

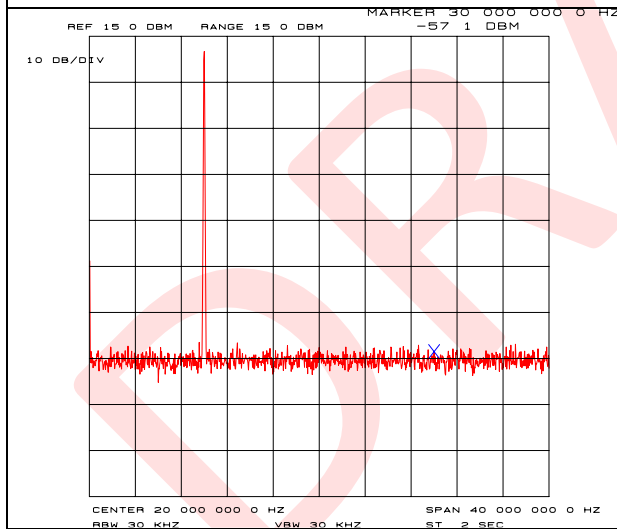

**Fig. 9: PRL-175A →PRL-414B-Q1→
PRL-LPF7-12MHz→HP3585A
-57.1. dBm at 30 MHz**

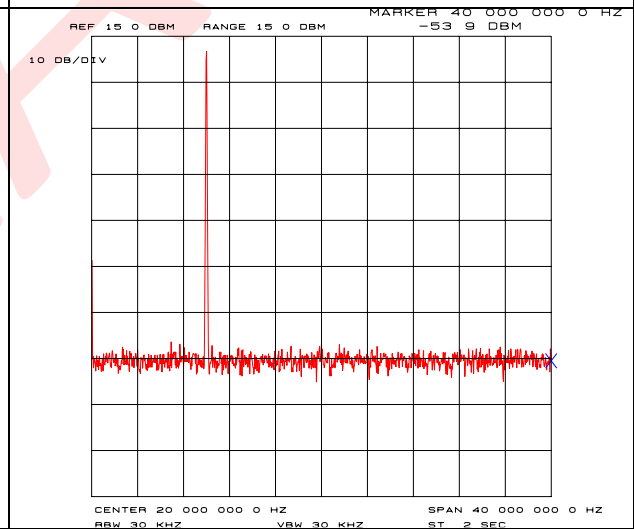


**Fig. 10: PRL-175A →PRL-414B-Q1→
PRL-LPF7-12MHz→HP3585A
-53.9 dBm at 40 MHz**

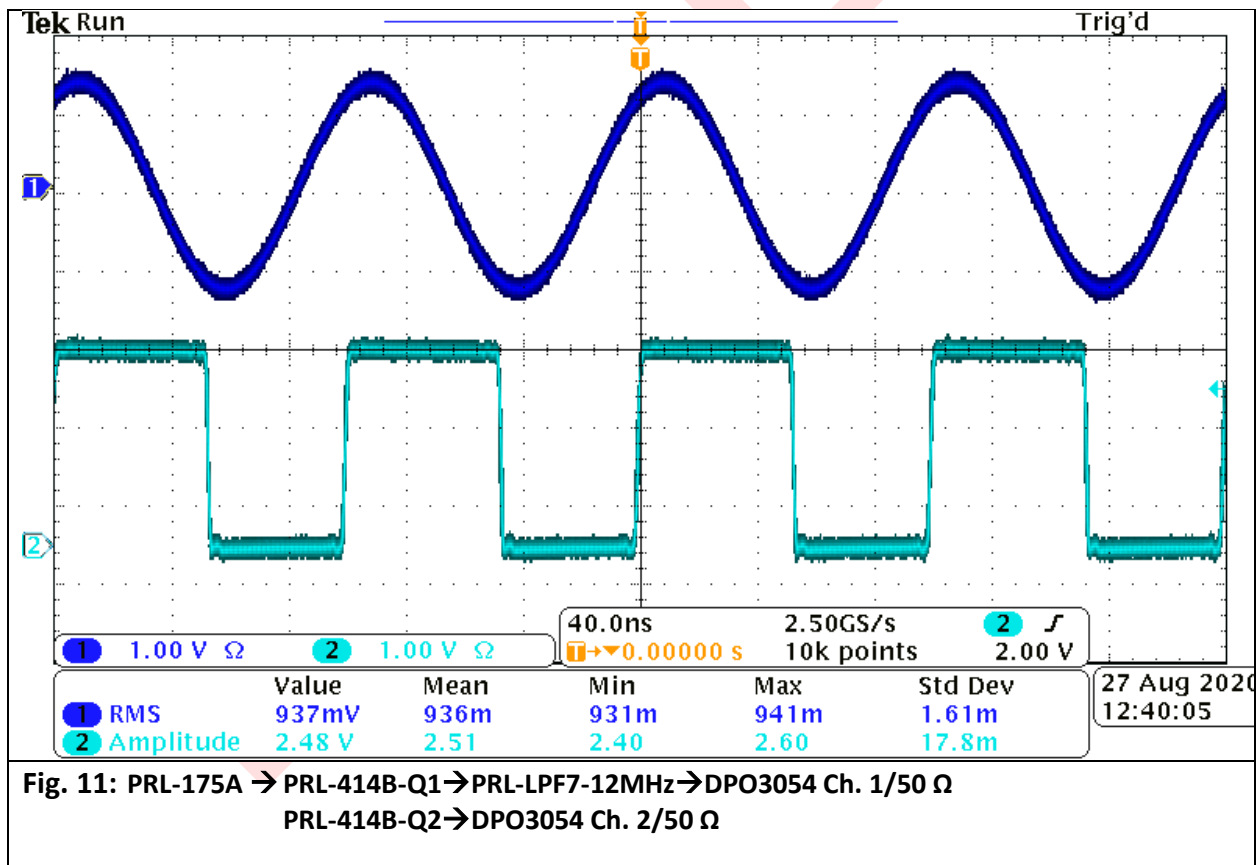Actual vs. Modeled attenuations are compared below, where any measurements below approximately -60 dBm are below the noise floor of the measurement setup:

Freq (MHz)	Power (dBm)		Attenuation: (dBm)	
	Original	Filtered	Actual	Modeled
10	+13.6	+11.7	-1.9	-0.1
20	-6.8	-53.3	-46.5	-49.4
30	+3.5	-57.1	-60.6	-78.2
40	-7.2	-53.9	-46.7	-95.8

We then cabled the **PRL-414B-SMA** into a 500 MHz oscilloscope (**DPO3054**), both with and without the filter. Screen captures were taken [directly into MS Word via the TekVISA Toolbar](#). The **PRL-414B-SMA** exhibits excellent symmetry across its 4 outputs, so output **Q2** is a very good proxy for **Q1** without the filter installed.



Conclusion:

The **PRL-LPF7-12MHz** does an excellent job filtering a 10 MHz TTL square wave from the **PRL-414B-SMA** into a clean sinewave with good spectral purity and low loss at the desired frequency.