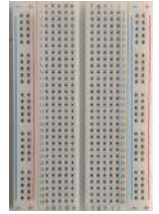




# QUIZ for Lesson 1 in the Mr Circuit Lab 1 or in STEM KIT #00 for Mr Circuit Electronics Training



## QUIZ for Lesson 1 - "Electron Theory"



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

**A** #1 Everything around you is made of \_\_\_\_\_ .

- B** A. wood
- C** B. matter
- D** C. steel
- A. water

**A** #6 Atoms have a central core called \_\_\_\_\_ .

- B** A. a middle section
- C** B. a nucleus
- D** C. a slice
- A. a modicum

**A** #2 Matter is made up of \_\_\_\_\_ .

- B** A. water
- C** B. steel
- D** C. elements
- A. wood

**A** #7 What are the positively charged particles in an atom called?

- B** A. protons
- C** B. products
- D** C. add ons
- A. neutrons

**A** #3 Atoms are what make up \_\_\_\_\_ .

- B** A. elements
- C** B. protons
- D** C. electrons
- A. neutrons

**A** #8 A particle in an atom that has no electrical charge is called \_\_\_\_\_ .

- B** A. a nothing
- C** B. a widget
- D** C. a neutron
- A. an axion

**A** #4 In the nucleus of \_\_\_\_\_ are protons and neutrons.

- B** A. an electron
- C** B. a proton
- D** C. an atom
- A. a neutron

**A** #9 The part of Physics that studies the movement of electrons is called \_\_\_\_\_ .

- B** A. resistance
- C** B. conductance
- D** C. capacitance
- A. electronics

**A** #5 The movement of electrons from atom to atom is called \_\_\_\_\_ .

- B** A. an electron current
- C** B. an electron charge
- D** C. an electron resistance
- A. a neutron flow

**A** #10 What circulates through the filament of an incandescent bulb to make it light up?

- B** A. electrons
- C** B. magnets
- D** C. protons
- A. neutrons


Score	
-------	--



# QUIZ for Lesson 2 in the Mr Circuit Lab 1 or in STEM KIT #00 for Mr Circuit Electronics Training


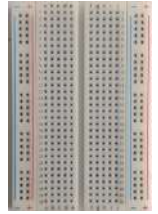
## QUIZ for Lesson 2 - "Component Identification"



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A **#1** What is the primary function of a battery in a circuit?

B

C **A.** store electric energy

D **B.** serve as a paper weight

**C.** give resistance to a circuit

**D.** amplify electricity

**#6** Which type of capacitor generally stores relatively large amount of electric charge?

**A.** a ceramic disc capacitor

**B.** an electrolytic capacitor

**C.** a surface mount capacitor

**D.** a mica capacitor

A **#2** What is the primary function of a resistor?

B **A.** resist proton flow

C **B.** add color to your circuit

D **C.** count electrons

**D.** limit or control current

**#7** What component varies its resistance according to the light intensity?

**A.** a Photocell

**B.** a Transistor

**C.** a 555 Timer IC

**D.** an SCR

A **#3** What is the primary function of an LED?

B **A.** control electron flow

C **B.** light up when current flows through it

D **C.** provide heat to keep you warm

**D.** store electrons

**#8** What component has an Emitter, Base, and Collector?

**A.** a Transistor

**B.** an SCR

**C.** a Diode

**D.** a Potentiometer

A **#4** Which set of components has a schematic symbol that includes a 'squiggly' line?

B **A.** a resistor, a photocell, and a potentiometer

C **B.** a capacitor and an SCR

D **C.** an LED and a Battery

**D.** an Integrated Circuit and a Speaker

**#9** Which of these component has a Gate, an Anode, and a Cathode lead?

**A.** an SCR

**B.** a Transistor

**C.** a Diode

**D.** a Resistor

A **#5** Which of these has a 'diode symbol' as part of its symbol?

B **A.** a Diode

C **B.** an SCR

D **C.** an LED

**D.** All the above

**#10** What is the purpose of a speaker?

**A.** convert electrical currents into sound waves

**B.** use power

**C.** be an adjustable capacitor

**D.** take up space in a circuit


Score	
-------	--



# QUIZ for Lesson 3 in the Mr Circuit Lab 1 or in STEM KIT #00 for Mr Circuit Electronics Training


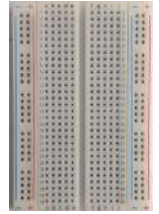
## QUIZ for Lesson 3 - "Resistor Color Code"



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A **#1** A resistor of 10,000 Ohms has \_\_\_\_\_ than a resistor of 1,000 Ohms.

B

C **A.** less opposition to current flow

D **B.** more opposition to current flow

**C.** less Ohms

**D.** larger physical size

**#6** What does the color green stand for in the Resistor Color Code?

**A.** 5

**B.** 9

**C.** 0

**D.** 3

A **#2** Resistance in electronics is the \_\_\_\_\_ .

B

C **A.** encouragement to current flow

D **B.** not important

**C.** opposition to current flow

**D.** storage of electrons

**#7** What is the value in Ohms of a resistor with color bands of yellow, violet, black, gold?

**A.** 55,000 Ohms

**B.** 360 Ohms

**C.** 47 Ohms

**D.** 68k Ohms

A **#3** The fourth color band on a  $\pm 5\%$  resistor is what color?

B

C **A.** gold

D **B.** silver

**C.** black

**D.** red

**#8** If the fourth or last band on a resistor is the color silver, what is the tolerance?

**A.**  $\pm 10\%$

**B.**  $\pm 5\%$

**C.**  $\pm 3\%$

**D.**  $\pm 2\%$

A **#4** Why do we put color bands on resistors?

B

C **A.** because numbers would be very small

D **B.** because colors make the circuit work better

**C.** electronics likes many colors

**D.** to test for colorblindness

**#9** There are four bands on a  $\pm 5\%$  resistor. The first two colors represent \_\_\_\_\_ .

**A.** alpha numerics

**B.** alpha characters

**C.** negative numbers

**D.** numerals

A **#5** What is the purpose for the Resistor Color Code?

B

C **A.** to hide the value of the resistor

D **B.** to determine the Ohms of the resistor

**C.** to add color to the circuit

**D.** to make it hard to read the value in Ohms

**#10** In the Resistor Color Code, what is the color that represents '2'?

**A.** Orange

**B.** Violet

**C.** Red

**D.** Black


Score	
-------	--



# QUIZ for Lesson 4 in the Mr Circuit Lab 1 or in STEM KIT #00 for Mr Circuit Electronics Training


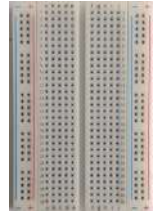
## QUIZ for Lesson 4 "Solderless Circuit Board"



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** Why do we use a Solderless Circuit Board to assemble circuits?

- A. to make the circuit more permanent
- B. to add more resistance to the circuit
- C. to slow down the electrons
- D. to make connections without soldering

- A
- B
- C
- D

**#2** What is the purpose of the channel down the middle of the solderless circuit board?

- A. to be able to install Integrated Circuits
- B. to release moisture from the circuit
- C. to separate resistors from capacitors
- D. to count the components in the circuit

- A
- B
- C
- D

**#3** Each hole in a 'vertical group' or set of 5 holes is \_\_\_\_\_ .

- A. not connected electrically
- B. full of high resistance
- C. electrically connected
- D. has a high voltage

- A
- B
- C
- D

**#4** A Solderless Circuit Board is \_\_\_\_\_ .

- A. not reusable
- B. reusable
- C. never used by technicians and engineers
- D. difficult to find

- A
- B
- C
- D

**#5** How many sets of 5 holes are there on the Solderless Circuit Board provided?

- A. 22
- B. 660
- C. 500
- D. 60

- A
- B
- C
- D

**#6** Each hole in the Solderless Circuit Board is designed to accept how many wires or leads?

- A. 1
- B. 5
- C. 3
- D. 14

- A
- B
- C
- D

**#7** On the Solderless Circuit Board, an Integrated Circuit is installed \_\_\_\_\_ .

- A. anywhere you like
- B. on one side of the other
- C. hanging off the edge of the board
- D. straddling the center channel

- A
- B
- C
- D

**#8** Inside the holes in the Solderless Circuit Board are clips made of \_\_\_\_\_ .

- A. plastic
- B. wood
- C. metal
- D. pvc material

- A
- B
- C
- D

**#9** Why are there numbers and letters on the Solderless Circuit Board?

- A. for decoration
- B. to practice counting
- C. to identify each and every hole
- D. for no real purpose

- A
- B
- C
- D

**#10** The 5 holes in a vertical group on a Solderless Circuit Board are all \_\_\_\_\_ .

- A. shorted together
- B. not shorted together
- C. are insulated from each other
- D. are glued together

Score	
-------	--



# QUIZ for Exp 01 or STEM KIT #01 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “How a Resistor Works” Experiment 1

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** In Experiment #1, the brightness of the LED depends on \_\_\_\_\_ .  
**A.** the capacitor value in the circuit  
**B.** the value of the resistor in the circuit  
**C.** the solderless circuit board  
**D.** the battery snap

**#6** The short lead on an LED is?  
**A.** the Gate  
**B.** the Anode  
**C.** the Cathode  
**D.** the Positive

A  
B  
C  
D

A  
B  
C  
D

**#2** Of the four values of resistors in Exp. #1, which value caused the LED to be the brightest?  
**A.** 100 ohm  
**B.** 220 ohm  
**C.** 1k ohm  
**D.** 6.8k ohm

**#7** What are the colors on a 1000 Ohm ±5% resistor?  
**A.** brown, black, red, gold  
**B.** green, blue, red, silver  
**C.** blue, gray, red, gold  
**D.** brown, red, green silver

A  
B  
C  
D

A  
B  
C  
D

**#3** What color is the third band on the 6.8k ohm resistor?  
**A.** blue  
**B.** green  
**C.** black  
**D.** red

**#8** With an LED in a circuit, the more \_\_\_\_\_, the greater the brightness.  
**A.** air  
**B.** capacitance  
**C.** current  
**D.** light

A  
B  
C  
D

A  
B  
C  
D

**#4** Which side of battery does the electron current flow from?  
**A.** positive side  
**B.** left side  
**C.** negative side  
**D.** top side

**#9** To reduce the amount of current flowing in a circuit, you can \_\_\_\_\_ the amount of resistance.  
**A.** increase  
**B.** decrease  
**C.** rotate  
**D.** circle

A  
B  
C  
D

A  
B  
C  
D

**#5** What is the color of the positive lead on the battery snap?  
**A.** green  
**B.** red  
**C.** black  
**D.** yellow

**#10** Of the four values of resistors in Exp. #1, which value caused the LED to be the dimmest?  
**A.** 100 ohm  
**B.** 220 ohm  
**C.** 1k ohm  
**D.** 6.8k ohm

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 02 or STEM KIT #02 in the Mr Circuit Electronics Training Lab 1



## This Quiz covers the training learned by completing “How a Potentiometer Works” Experiment 2



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** Between which leads on the Potentiometer in Experiment #02 does the resistance measure the maximum?

- A. leads A and B
- B. leads A and C
- C. leads C and B
- D. there is no maximum resistance

**#6** What is the function of the Potentiometer in Exp. #2?

- A. to vary the capacitance in the circuit
- B. to reduce proton flow
- C. to slow down the speed of the electrons
- D. to vary the resistance in the circuit

- A
- B
- C
- D

- A
- B
- C
- D

**#2** The ‘cursor’ on the Potentiometer is connected to which lead?

- A. C
- B. A
- C. it is not connected to any lead
- D. B

**#7** In Exp. #2, what is the purpose of the 100 ohm resistor in the circuit?

- A. to protect the LED from burning out
- B. to increase the amount of current flowing
- C. to make the circuit more interesting
- D. to increase the parts used in the circuit

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The resistance value of the Potentiometer is zero when the ‘cursor’ is moved next to which lead?

- A. B
- B. A
- C. black
- D. C

**#8** When you twist the shaft on a Potentiometer, it varies its \_\_\_\_\_.

- A. resistance
- B. capacitance
- C. area
- D. wattage

- A
- B
- C
- D

- A
- B
- C
- D

**#4** Does the polarity of the battery connection matter in this circuit?

- A. NO
- B. it is not important
- C. YES
- D. the LED will light up either way

**#9** To set the Potentiometer at its maximum resistance you have to move the ‘cursor’ next to which lead?

- A. B
- B. A
- C. black
- D. C

- A
- B
- C
- D

- A
- B
- C
- D

**#5** In Exp. #2, what is the name of the electronic component that you are learning about?

- A. the Potentiometer
- B. an LED
- C. a capacitor
- D. a battery snap

**#10** The LED is the brightest when the ‘cursor’ on the Potentiometer is next to which lead?

- A. B
- B. A
- C. black
- D. C

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 03 or STEM KIT #03 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “How a Photocell Works” Experiment 3



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** How many leads does a Photocell have?

- A. 1
- B. 2
- C. 3
- D. 6

**#6** This circuit has three components. They are the battery snap, a resistor, and a \_\_\_\_\_.

- A. Photocell
- B. Potentiometer
- C. capacitor
- D. microphone

- A
- B
- C
- D

- A
- B
- C
- D

**#2** Does a Photocell have polarity?

- A. YES
- B. NO
- C. maybe
- D. not necessarily

**#7** In this experiment, what do we use to shield the light from hitting the Photocell?

- A. a flashlight
- B. a fork
- C. a hand
- D. a forklift

- A
- B
- C
- D

- A
- B
- C
- D

**#3** In order for a Photocell to vary its resistance, light has to hit the \_\_\_\_\_.

- A. top surface
- B. bottom surface
- C. the leads
- D. the left side

**#8** A Photocell changes its resistance because it is sensitive to \_\_\_\_\_.

- A. air
- B. pressure
- C. gravity
- D. light

- A
- B
- C
- D

- A
- B
- C
- D

**#4** If you reverse the leads on the battery snap, how will that affect the circuit?

- A. the LED will be brighter
- B. the circuit will work just fine
- C. the LED will get hot and burn up
- D. the LED will not light up

**#9** When you block the amount of light hitting a Photocell, its resistance \_\_\_\_\_.

- A. is not affected
- B. decreases
- C. causes more capacitance in the circuit
- D. increases

- A
- B
- C
- D

- A
- B
- C
- D

**#5** If you put this circuit into a dark room, how will that affect the LED brightness?

- A. it will be super bright
- B. it will burn out
- C. it will be dimmer
- D. it will be the same as in bright light

**#10** How does the brightness of the light that hits the Photocell affect the LED in the circuit?

- A. has no effect at all
- B. brighter the light, brighter the LED
- C. LEDs don't get brighter or dimmer
- D. dimmer the light, brighter the LED

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 04 or STEM KIT #04 in the Mr Circuit Electronics Training Lab 1



## This Quiz covers the training learned by completing “How a Capacitor Works” Experiment 4



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** In Experiment #4, what is the component that you learned about?

- A. a capacitor
- B. a resistor
- C. an LED
- D. a battery snap

**#6** What happens to the LED if we reverse the polarity on the battery?

- A. it lights up just fine
- B. it burns out the LED
- C. the LED will not light up
- D. the LED will get hot

- A
- B
- C
- D

- A
- B
- C
- D

**#2** In Exp. #4, how many resistors do we use?

- A. 1
- B. 2
- C. 3
- D. 4

**#7** The more capacitance a capacitor has, the \_\_\_\_\_ electrical charge it will hold.

- A. less
- B. fuzzier
- C. worse
- D. more

- A
- B
- C
- D

- A
- B
- C
- D

**#3** In Exp. #4, when you disconnect the battery, the LED remains lit for a time because \_\_\_\_\_.

- A. the two resistors keep it lit
- B. the energy stored in the capacitor keeps it lit
- C. LEDs store electrons
- D. your eyes are playing tricks on you.

**#8** Which value of capacitor will hold more electrical charge?

- A. 1000uF
- B. 100uF
- C. 10uF
- D. 1uF

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What happens to the LED when we reduce the value of the capacitor in the circuit and then disconnect the battery?

- A. The LED remains lit for a longer time.
- B. The LED will burn out.
- C. The LED remains lit for shorter time.
- D. It will have no effect on the LED.

**#9** What is the purpose of a capacitor in a circuit?

- A. to vary the resistance
- B. to store inductance
- C. to store an electrical charge
- D. to increase the wattage

- A
- B
- C
- D

- A
- B
- C
- D

**#5** In Exp. #4, what type of capacitor are we using?

- A. an electrolytic capacitor
- B. a ceramic disc capacitor
- C. a polyester film capacitor
- D. a variable capacitor

**#10** Does the capacitor in this circuit have polarity?

- A. NO
- B. can't tell
- C. YES
- D. its an inductor

- A
- B
- C
- D

Score	
-------	--





# QUIZ for Exp 05 or STEM KIT #05 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing  
**“How a Speaker Works” Experiment 5**



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** What would happen in this circuit if you reverse the polarity of the battery snap?  
**A.** the speaker will burn out  
**B.** it will not work at all  
**C.** the speaker will whistle  
**D.** it will work just fine

**#6** What is the name of the part we learn about in Exp. #5?  
**A.** a speaker  
**B.** a capacitor  
**C.** a resistor  
**D.** a photocell

A  
B  
C  
D

A  
B  
C  
D

**#2** What do you think the purpose of the 10 Ohm resistor is in this circuit?  
**A.** to increase the amount of current  
**B.** to reduce the amount of current  
**C.** to increase the capacitance  
**D.** to decrease the inductance

**#7** What is the function of the part we learn about in Exp. #5?  
**A.** reduce the amount of current flow  
**B.** to store electrons and protons  
**C.** transform electrical energy to sound waves  
**D.** to look nice in a circuit

A  
B  
C  
D

A  
B  
C  
D

**#3** When you reverse the polarity of the battery snap in this circuit, it affects the \_\_\_\_\_ of the speaker.  
**A.** cone  
**B.** magnet  
**C.** volume  
**D.** sound quality

**#8** What part of a Speaker moves when current flows through it?  
**A.** the bracket  
**B.** the magnet  
**C.** the handle  
**D.** the cone

A  
B  
C  
D

A  
B  
C  
D

**#4** Why does the sound stop when you leave the battery connected?  
**A.** the magnet gets weak  
**B.** the speaker burns out  
**C.** the cone stops moving  
**D.** the current increases

**#9** What sound comes out of a speaker when a steady DC current is connected to its coil?  
**A.** it makes a steady tone  
**B.** it makes a click and then becomes silent  
**C.** it plays music  
**D.** it sounds like a siren

A  
B  
C  
D

A  
B  
C  
D

**#5** Why does the speaker make a ‘click’ when you connect and when you disconnect the battery?  
**A.** the cone moves each time  
**B.** the speaker is alive  
**C.** the magnet is weak  
**D.** the speaker is round

**#10** What kind of device is a Speaker?  
**A.** rectifying device  
**B.** electromechanical device  
**C.** photoelectric device  
**D.** semiconductor device

A  
B  
C  
D

Score	
-------	--




# QUIZ for Exp 06 or STEM KIT #06 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “How a Diode Works” Experiment 6

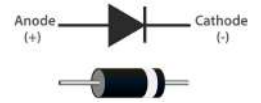

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** In Experiment #6, what is the component that you learned about?  
**A.** a capacitor  
**B.** a diode  
**C.** an LED  
**D.** a battery snap

**#6** The arrow on the schematic symbol for a diode points to the \_\_\_\_\_ .  
**A.** Anode  
**B.** Gate  
**C.** Door  
**D.** Cathode

A  
B  
C  
D

A  
B  
C  
D

**#2** A diode allows current to flow through it \_\_\_\_\_ .  
**A.** freely both ways  
**B.** in one direction only  
**C.** if it is warm  
**D.** only if there is a resistor in the circuit

**#7** An LED is also a type of \_\_\_\_\_ .  
**A.** inductor  
**B.** diode  
**C.** capacitor  
**D.** speaker

A  
B  
C  
D

A  
B  
C  
D

**#3** How is the Cathode side of a diode marked on the diode itself?  
**A.** with a double color stripe  
**B.** with an arrow  
**C.** with a white band around one end  
**D.** with an asterisk

**#8** If we were to increase the value of the resistor in the circuit from 220 Ohms to 1000 Ohms, how would that affect the LED?  
**A.** the LED would increase its brightness  
**B.** the LED would reduce in brightness  
**C.** the current flow in the LED would increase  
**D.** the brightness would stay the same

A  
B  
C  
D

A  
B  
C  
D

**#4** A diode allows an easy flow of electrons from \_\_\_\_\_ to \_\_\_\_\_ .  
**A.** top, bottom  
**B.** bottom, top  
**C.** Anode, Cathode  
**D.** Cathode, Anode

**#9** If the LED lights up the same regardless of the polarity of the diode in the circuit, what would we assume?  
**A.** the LED is defective  
**B.** the diode is working fine  
**C.** the battery is weak  
**D.** the diode is defective

A  
B  
C  
D

A  
B  
C  
D

**#5** In Exp. #6, what component do we use to indicate that current is flowing?  
**A.** a speaker  
**B.** an LED  
**C.** an electrolytic capacitor  
**D.** a disc capacitor

**#10** A diode is considered a \_\_\_\_\_ .  
**A.** simple resistor  
**B.** one-way gate  
**C.** a variable resistor  
**D.** a simple capacitor

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 07 or STEM KIT #07 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “How an SCR (Silicon Control Rectifier) Works” Exp. 7



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A **#1** What are the three connections on an SCR?

B A. Input, Output, and Neutral

C B. Up, Down, Middle

D C. Right, Left, Straight

D D. Cathode, Anode, Gate

**#6** The letters SCR in Exp. #7 stand for ‘Silicon Controlled Rectifier’. How many connection leads does an SCR have?

A. 5

B. 4

C. 3

D. 2

A **#2** Once an SCR is turned on, in order to turn it off, you need to \_\_\_\_\_.

B A. remove the voltage on the Gate

C B. clap your hands

D C. remove the power from the entire circuit

D D. double the voltage

**#7** If a positive voltage is applied to the Gate of an SCR, what happens in the circuit?

A. the electrons flow through the SCR

B. the SCR will turn off

C. the resistance of the SCR increases

D. absolutely nothing

A **#3** Most of the electron current flowing through an SCR is flowing through the \_\_\_\_\_.

B A. Anode to Cathode circuit

C B. the Gate circuit

D C. Anode to Gate circuit

D D. Cathode to Anode circuit

**#8** The Anode lead is connected internally to the \_\_\_\_\_ on the SCR.

A. metal tab with a hole in it

B. to the Gate lead

C. to the Cathode lead

D. to the round edge on the SCR

A **#4** To turn on an SCR in a circuit, you need a \_\_\_\_\_.

B A. large current on the Gate

C B. small positive voltage on the Anode

D C. small positive voltage on the Gate

D D. large current on the Cathode

**#9** If we reverse the polarity of the battery snap in the circuit, what will happen?

A. it will not work

B. it will work just fine

C. the SCR will burn out

D. the LED will self-destruct

A **#5** The Gate lead on the SCR in this experiment is marked by the \_\_\_\_\_.

B A. metal tab on the SCR

C B. left lead on the SCR

D C. beveled edge on the SCR

D D. center lead on the SCR

**#10** An SCR is considered to be a \_\_\_\_\_.

A. a variable resistor

B. a variable capacitor

C. “a diode with a difference”

D. a good potentiometer

Score	
-------	--




# QUIZ for Exp 08 or STEM KIT #08 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing
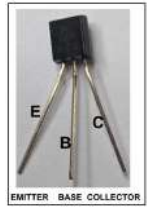
## “How an NPN Transistor Works” Experiment 8



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** The NPN transistor we use in this experiment is referred to as a \_\_\_\_\_ transistor?

- A. Bipolar
- B. Dual
- C. Double
- D. integrated

**#6** In this NPN transistor circuit, which LED should conduct the most electron current?

- A. LED 1
- B. LED 2
- C. LED 3
- D. LED 4

- A
- B
- C
- D

- A
- B
- C
- D

**#2** The schematic symbol of an NPN Transistor shows an arrow pointing to the \_\_\_\_\_ lead.

- A. cathode
- B. emitter
- C. base
- D. collector

**#7** In this circuit, the Cathode of LED 2 is connected to the \_\_\_\_\_ of the NPN transistor.

- A. Collector
- B. Base
- C. Emitter
- D. Gate

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The leads on an NPN transistor are called the Emitter, Base, and \_\_\_\_\_.

- A. Collector
- B. Cathode
- C. Anode
- D. Gate

**#8** A transistor controls a large amount of current with \_\_\_\_\_.

- A. a small amount of current
- B. a large amount of current
- C. a small amount of voltage
- D. a huge amount of voltage

- A
- B
- C
- D

- A
- B
- C
- D

**#4** Most of the current traveling through an NPN transistor travels through the \_\_\_\_\_ circuit.

- A. Emitter-Base
- B. Emitter-Collector
- C. Base-Base
- D. Cathode-Anode

**#9** An NPN transistor has three pins: a Collector, a Base, and \_\_\_\_\_.

- A. an Anode
- B. an Emitter
- C. a Cathode
- D. a Gate

- A
- B
- C
- D

- A
- B
- C
- D

**#5** In an NPN transistor, the direction of the electron flow is from \_\_\_\_\_.

- A. Base to Emitter
- B. Base to Base
- C. Emitter to Emitter
- D. Emitter to Collector

**#10** The process of having a small current controlling a large current is called \_\_\_\_\_.

- A. increase of the voltage
- B. conservation of resources
- C. reduction
- D. amplification

- A
- B
- C
- D

Score	
-------	--




# QUIZ for Exp 09 or STEM KIT #09 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing
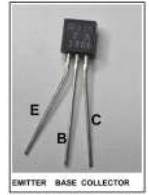
## “How an PNP Transistor Works” Experiment 9



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** In this circuit, the Emitter of the PNP is connected to the \_\_\_\_\_ of the battery.  
A. negative  
B. positive  
C. neutral  
D. ground

**#6** The PNP transistor we use in this experiment is referred to as a \_\_\_\_\_ transistor?  
A. Bipolar  
B. Dual  
C. Double  
D. Integrated

A  
B  
C  
D

A  
B  
C  
D

**#2** In Exp. #9, we use LED brightnesses to compare the amount of \_\_\_\_\_ flowing.  
A. current  
B. voltage  
C. resistance  
D. air

**#7** The schematic symbol of a PNP Transistor shows an arrow pointing to the \_\_\_\_\_ lead.  
A. Cathode  
B. Emitter  
C. Base  
D. Collector

A  
B  
C  
D

A  
B  
C  
D

**#3** In a PNP transistor circuit, which current is greater?  
A. the Collector to Emitter current  
B. the Base to Emitter current  
C. the Emitter to Collector current  
D. the Emitter to Base current

**#8** A transistor controls a large amount of current with \_\_\_\_\_ .  
A. a small amount of current  
B. a large amount of current  
C. a small amount of voltage  
D. a huge amount of voltage

A  
B  
C  
D

A  
B  
C  
D

**#4** In a transistor circuit, when there is no base current, there is \_\_\_\_\_ .  
A. no voltage  
B. more collector current  
C. no collector current  
D. no anode voltage

**#9** A PNP transistor has three pins: a Collector pin, a Base pin, and \_\_\_\_\_ pin.  
A. an Anode  
B. an Emitter  
C. a Cathode  
D. a Gate

A  
B  
C  
D

A  
B  
C  
D

**#5** In Exp. #9, the PNP transistor is working as \_\_\_\_\_ .  
A. an amplifier  
B. a voltage regulator  
C. a resistor  
D. a variable capacitor

**#10** In a PNP transistor, the direction of the electron flow is from \_\_\_\_\_ .  
A. Base to Base  
B. Emitter to Collector  
C. Emitter to Base  
D. Collector to Emitter

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 10 or STEM KIT #10 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “How a Two-Transistor Oscillator Works” Experiment 10

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This two-transistor oscillator uses an NPN transistor and \_\_\_\_\_ .  
A. an SCR  
B. a PNP Transistor  
C. a Diode  
D. a Potentiometer

**#6** In Exp. #10, how many transistors do we use to make an oscillator?  
A. 5  
B. 4  
C. 3  
D. 2

A  
B  
C  
D

A  
B  
C  
D

**#2** In this two-transistor oscillator the Collector of transistor Q2 is connected to the Base of transistor Q1 through a \_\_\_\_\_ .  
A. capacitor  
B. resistor  
C. wire  
D. speaker

**#7** The circuit in Exp. #10 generates a tone by turning the \_\_\_\_\_ on and off at an audio frequency.  
A. capacitor  
B. speaker  
C. battery  
D. capacitance

A  
B  
C  
D

A  
B  
C  
D

**#3** In this two-transistor oscillator circuit, the Emitter of Q1 3904 is connected to the Base of transistor Q2 through a \_\_\_\_\_ ?  
A. capacitor  
B. resistor  
C. wire  
D. speaker

**#8** Generally, an audio signal (one that can be heard by your ears) is in what frequency range?  
A. 1 million to 10 million (cycles per second)Hz  
B. 10 Hz to 16,000 Hz  
C. 100 thousand Hz to 100 megahertz  
D. zero to five Hz

A  
B  
C  
D

A  
B  
C  
D

**#4** If we reverse the polarity of the battery snap on the circuit, what will happen?  
A. The circuit will not work.  
B. It will work just fine.  
C. The transistors will burn out.  
D. The speaker will self-destruct.

**#9** In electronics, one Hz (Hertz) means one change per \_\_\_\_\_ or one cycle per \_\_\_\_\_ .  
A. second, second  
B. minute, minute  
C. hour, hour  
D. day, day

A  
B  
C  
D

A  
B  
C  
D

**#5** What happens if we increase the value of resistor R1 in the circuit?  
A. it will increase the frequency  
B. it will make no change in frequency  
C. it will cause the speaker to jam  
D. it will lower the frequency

**#10** What does the 10 Ohm resistor do in the circuit ?  
A. increase the current through the speaker  
B. vary the frequency of the oscillator  
C. reduce current through the speaker  
D. lower the frequency of the oscillator

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 11 or STEM KIT #11 in the Mr Circuit Electronics Training Lab 1



## This Quiz covers the training learned by completing “How a 555 Timer IC Works” Experiment 11



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** How many pins does a 555 Timer IC have?

- A. 8
- B. 3
- C. 6
- D. 12

**#6** What does the indentation or marking on the top end of the 555 Timer IC help you find?

- A. Pin 5
- B. Pin 4
- C. Pin 1
- D. the bottom of the IC

- A
- B
- C
- D

- A
- B
- C
- D

**#2** What pin is the output pin on the 555 Timer?

- A. 8
- B. 3
- C. 6
- D. 12

**#7** When a 555 Timer IC is working as a ‘clock’, it puts out pulses on \_\_\_\_\_ .

- A. Pin 8
- B. Pin 2
- C. Pin 5
- D. Pin 3

- A
- B
- C
- D

- A
- B
- C
- D

**#3** If you connect an oscilloscope to the output Pin 3 on this circuit when operating, what might you see?

- A. pulses
- B. aliens
- C. resistance values
- D. inductance variations

**#8** When you are counting the pins on a 555 Timer IC, you count them \_\_\_\_\_ .

- A. up and down
- B. clockwise
- C. by tens
- D. counter-clockwise

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What is the value of the capacitor in microfarads connected to Pin 2 of the 555 Timer IC in this circuit?

- A. 1000uF
- B. 10uF
- C. 33uF
- D. 470uF

**#9** When installing the 555 Timer IC on the solderless circuit board, you install it \_\_\_\_\_ .

- A. always on the right end of the board
- B. with pin 1 in hole 1a
- C. across the center channel
- D. on the bottom of the board

- A
- B
- C
- D

- A
- B
- C
- D

**#5** If we reverse the polarity of the battery snap on the circuit, what will happen?

- A. It will work just fine.
- B. You might destroy the 555 Timer IC.
- C. The LED will burn out.
- D. The LED will self-destruct.

**#10** When a 555 Timer IC is working as a ‘timer’, it puts out a voltage on \_\_\_\_\_ for a set period of time and then shuts off automatically.

- A. Pin 3
- B. Pin 5
- C. Pin 8
- D. Pin 2

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 12 or STEM KIT #12 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Burglar Alarm Circuit” Experiment 12



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** How do you turn off this alarm once it is tripped?  
  
A. touch a negative voltage to the Gate  
B. open the normally-open switch  
C. remove power from the circuit  
D. close the normally-closed switch

**#6** When the 33 Ohm resistor is connected to the Gate, what happens?  
  
A. the alarm is turned off  
B. the alarm is triggered  
C. the alarm is reset  
D. nothing

A  
B  
C  
D

A  
B  
C  
D

**#2** What item in this alarm circuit indicates that the alarm has been tripped?  
  
A. the LED  
B. the Diode  
C. the SCR  
D. the resistor

**#7** The cathode of the LED is connected to what pin on the SCR?  
  
A. the Gate  
B. the Cathode  
C. the Emitter  
D. the Anode

A  
B  
C  
D

A  
B  
C  
D

**#3** Which component limits the current flowing through the LED?  
  
A. the SCR  
B. the 220 ohm resistor  
C. the Diode  
D. the 0.1 disc capacitor

**#8** How many pins are there on an SCR.  
  
A. 1  
B. 2  
C. 3  
D. 4

A  
B  
C  
D

A  
B  
C  
D

**#4** To trigger the alarm, which lead on the SCR has to receive a small positive voltage?  
  
A. EMITTER  
B. CATHODE  
C. ANODE  
D. GATE

**#9** In this circuit, there are how many switches to trigger the alarm circuit?  
  
A. 1  
B. 2  
C. 3  
D. 5

A  
B  
C  
D

A  
B  
C  
D

**#5** Where would you connect a buzzer to this alarm circuit?  
  
A. across R3 and the LED  
B. across R1 and S1  
C. across R2 and D1  
D. across the SCR

**#10** How many capacitors do we use in this circuit?  
  
A. 3  
B. 2  
C. 1  
D. 4

A  
B  
C  
D

Score	
-------	--





# QUIZ for Exp 13 or STEM KIT #13 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an Automatic Night Light Circuit” Experiment 13

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This Automatic Night Light will turn on automatically \_\_\_\_\_?  
**A.** when there is light.  
**B.** when there is darkness.  
**C.** at noon each day.  
**D.** when it is humid outside.

**#6** The LEDs receive their current from which pin on the NPN transistor?  
**A.** the Collector  
**B.** the Emitter  
**C.** the Base  
**D.** the Gate

A  
B  
C  
D

A  
B  
C  
D

**#2** How many LEDs are there in this circuit?  
**A.** 1  
**B.** 3  
**C.** 2  
**D.** 5

**#7** Resistor R2, 16k Ohms, is connected directly to which terminal on the 9-Volt battery?  
**A.** the negative  
**B.** the center  
**C.** the neutral  
**D.** the positive

A  
B  
C  
D

A  
B  
C  
D

**#3** What is the purpose of the 47 Ohm resistor in the circuit?  
**A.** to increase the current in the circuit  
**B.** to serve as a fuse for the circuit  
**C.** to increase the brightness of the LEDs  
**D.** limit the current through the LEDs

**#8** The potentiometer has 3 connections. How many do we use in this circuit? .  
**A.** 0  
**B.** 2  
**C.** 3  
**D.** 1

A  
B  
C  
D

A  
B  
C  
D

**#4** What is the purpose of the Potentiometer in the circuit?  
**A.** to make the LEDs blink  
**B.** to adjust the sensitivity of the Photocell  
**C.** to adjust the loudness  
**D.** to make the battery last longer

**#9** What are the colors on Resistor R1, 47 Ohms?  
**A.** yellow, violet, black, gold  
**B.** brown, red, black, gold  
**C.** green, green, brown, gold  
**D.** gray, blue, brown, gold

A  
B  
C  
D

A  
B  
C  
D

**#5** If we reverse the polarity of the battery snap on the circuit, what will happen?  
**A.** it will work just fine.  
**B.** The LEDs will not light up.  
**C.** The LEDs will burn out.  
**D.** The LEDs will self-destruct.

**#10** This circuit is used to turn on the LEDs \_\_\_\_\_.  
**A.** when the weather is hot  
**B.** during the day  
**C.** at night  
**D.** when it is a humid day

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 14 or STEM KIT #14 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing STEM Kit #14



## “Build a DC to DC Power Supply Circuit” Experiment 14

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit has an input of a fixed DC voltage and an output of \_\_\_\_\_?  
A. a variable DC voltage  
B. an AC voltage  
C. a voltage higher than the input voltage  
D. a voltage from -5V to 5V

**#6** The voltage applied to the base of the transistor controls the \_\_\_\_\_ of the transistor.  
A. external capacitance  
B. internal resistance  
C. external resistance  
D. internal capacitance

A  
B  
C  
D

A  
B  
C  
D

**#2** What is the maximum current that can be provided by this DC to DC Power Supply?  
A. 10 milliamps  
B. 3 Amps  
C. 50 milliamps  
D. 1 Amp

**#7** The potentiometer controls the voltage applied to the \_\_\_\_\_ of the transistor.  
A. Collector  
B. Emitter  
C. Anode  
D. Base

A  
B  
C  
D

A  
B  
C  
D

**#3** You can use this power supply to supply voltage for \_\_\_\_\_ .  
A. portable transistor radios  
B. large HAM radios  
C. large Televisions and Stereos  
D. microwave ovens

**#8** The output of this DC to DC Power Supply will be a maximum when the \_\_\_\_\_ of the transistor is close to 0 volts.  
A. current applied to the Collector  
B. voltage applied to the Base  
C. voltage applied to the Emitter  
D. current applied to the Base

A  
B  
C  
D

A  
B  
C  
D

**#4** In this circuit, transistor Q1 is used as \_\_\_\_\_?  
A. a capacitor  
B. an inductor  
C. a fixed capacitance  
D. an adjustable resistor

**#9** When the \_\_\_\_\_ of transistor Q1 is high, the output voltage will be at minimum.  
A. external capacitance  
B. internal capacitance  
C. external resistance  
D. internal resistance

A  
B  
C  
D

A  
B  
C  
D

**#5** In this circuit, the potentiometer is used to \_\_\_\_\_ .  
A. vary the output voltage  
B. adjust the capacitance  
C. as a variable inductor  
D. keep the LED from burning out

**#10** In this circuit, the brightness of the LED is an indicator of the \_\_\_\_\_ .  
A. output voltage  
B. input voltage  
C. input current  
D. output capacitance

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 15 or STEM KIT #15 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an Electronic Metronome Circuit” Experiment 15

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** This metronome circuit is built using \_\_\_\_\_ .

- A. a 555 Timer IC
- B. a two-transistor oscillator
- C. an SCR
- D. a quad amplifier

**#6** In this circuit, the speaker is connected to the \_\_\_\_\_ of transistor Q2.

- A. Base
- B. Anode
- C. Collector
- D. Emitter

- A
- B
- C
- D

- A
- B
- C
- D

**#2** The potentiometer is used to adjust the \_\_\_\_\_ .

- A. the current through the speaker
- B. the capacitance of the transistors
- C. the loudness of the speaker
- D. speed of the oscillation

**#7** Transistor Q1 in this circuit is \_\_\_\_\_ .

- A. a PNP Transistor
- B. an NPN Transistor
- C. a variable diode
- D. a capacitance

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The Emitter of transistor Q1 is connected to the \_\_\_\_\_ of transistor Q2.

- A. Collector
- B. Anode
- C. Emitter
- D. Base

**#8** Based on your understanding of a two-transistor oscillator circuit, the purpose of Capacitor C1 is to \_\_\_\_\_ .

- A. reduce the current in the circuit
- B. help control the speed of the oscillator
- C. reduce the resistance of the circuit.
- D. reduce the voltage used in the circuit

- A
- B
- C
- D

- A
- B
- C
- D

**#4** The potentiometer varies the \_\_\_\_\_ on the Base of transistor Q1.

- A. voltage
- B. capacitance
- C. resistance
- D. current

**#9** The \_\_\_\_\_ of Q2 is connected directly to the positive of the battery.

- A. Emitter
- B. Collector
- C. Base
- D. Anode

- A
- B
- C
- D

- A
- B
- C
- D

**#5** As you adjust the potentiometer from 0 Ohms to its maximum Ohms, the oscillator will \_\_\_\_\_ in speed.

- A. decrease
- B. increase
- C. remain the same
- D. not be affected

**#10** The positive lead on Capacitor C1 is connected to the \_\_\_\_\_ of transistor Q1.

- A. Collector
- B. Anode
- C. Emitter
- D. Base

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 16 or STEM KIT #16 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build an Electronic Motorcycle Circuit” Experiment 16



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This motorcycle circuit is built using \_\_\_\_\_ .  
**A.** a 555 Timer IC  
**B.** a two-transistor oscillator  
**C.** an SCR  
**D.** a quad amplifier

**#6** In this circuit, the speaker is connected to the \_\_\_\_\_ of transistor Q2.  
**A.** Base  
**B.** Anode  
**C.** Collector  
**D.** Emitter

A  
B  
C  
D

A  
B  
C  
D

**#2** The potentiometer is used to adjust the \_\_\_\_\_ .  
**A.** the current through the speaker  
**B.** the capacitance of the transistors  
**C.** the loudness of the speaker  
**D.** speed of the oscillation

**#7** Transistor Q2 in this circuit is \_\_\_\_\_ .  
**A.** a PNP Transistor  
**B.** an NPN Transistor  
**C.** a variable diode  
**D.** is a capacitance

A  
B  
C  
D

A  
B  
C  
D

**#3** The Emitter of transistor Q1 is connected to the \_\_\_\_\_ of transistor Q2.  
**A.** Collector  
**B.** Anode  
**C.** Emitter  
**D.** Base

**#8** Based on your understanding of a two-transistor oscillator circuit, the purpose of Capacitor C1 is to \_\_\_\_\_ .  
**A.** reduce the current in the circuit  
**B.** help control the speed of the oscillator  
**C.** reduce the resistance of the circuit  
**D.** reduce the voltage used in the circuit

A  
B  
C  
D

A  
B  
C  
D

**#4** The potentiometer varies the \_\_\_\_\_ on the Base of transistor Q1.  
**A.** voltage  
**B.** capacitance  
**C.** resistance  
**D.** current

**#9** The \_\_\_\_\_ of Q2 is connected through a 10 Ohm resistor to the positive of the battery.  
**A.** Emitter  
**B.** Collector  
**C.** Base  
**D.** Anode

A  
B  
C  
D

A  
B  
C  
D

**#5** As you adjust the potentiometer from 0 Ohms to its maximum Ohms, the oscillator will \_\_\_\_\_ in speed.  
**A.** decrease  
**B.** increase  
**C.** remain the same  
**D.** not be affected

**#10** The positive lead on Capacitor C1 is connected to the \_\_\_\_\_ of transistor Q1 and to the potentiometer.  
**A.** Collector  
**B.** Anode  
**C.** Emitter  
**D.** Base

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 17 or STEM KIT #17 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Railroad Lights Circuit” Experiment 17



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** This circuit uses \_\_\_\_\_ working as a clock?

- A. an NPN Transistor
- B. a 555 Timer IC
- C. a PNP Transistor
- D. a Potentiometer

**#6** The speed if the blinking LEDs is \_\_\_\_\_ .

- A. variable
- B. super fast
- C. fixed
- D. super slow

- A
- B
- C
- D

- A
- B
- C
- D

**#2** When pin 3 on the 555 Timer is positive, \_\_\_\_\_ will be forward biased.

- A. LED 1
- B. Resistor R1
- C. Resistor R3
- D. LED 2

**#7** When this circuit is working, the LEDs will \_\_\_\_\_ ?

- A. blink on and off alternately
- B. remain off permanently
- C. remain on
- D. get hot and self-destruct

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The two LEDs in this circuit are installed in \_\_\_\_\_ polarity.

- A. the same
- B. amplifying
- C. opposite
- D. dual

**#8** When an LED is \_\_\_\_\_ it means that the Anode is positive and the Cathode is negative.

- A. reverse-biased
- B. forward-biased
- C. will not turn on
- D. will change from Red to Green

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?

- A. 1000uF
- B. 10uF
- C. 33uF
- D. 470uF

**#9** When an LED is \_\_\_\_\_ it means that the Anode is negative and the Cathode is positive.

- A. reverse-biased
- B. forward-biased
- C. will not turn on
- D. will change from Red to Green

- A
- B
- C
- D

- A
- B
- C
- D

**#5** If we reverse the polarity of the battery snap on the circuit, what will happen?

- A. it will work just fine
- B. you might destroy the 555 Timer IC
- C. the LED will burn out
- D. the LED will self-destruct

**#10** When an LED is forward biased, it will \_\_\_\_\_ .

- A. self-destruct
- B. turn on
- C. get hot
- D. turn off

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 18 or STEM KIT #18 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Variable Speed Lights Circuit” Experiment 18

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A #1 This circuit uses \_\_\_\_\_  
working as a clock?

- B
- C
- D
- A. an NPN Transistor
- B. a PNP Transistor
- C. a 555 Timer IC
- D. a Potentiometer

#6 LED 1 is connect to pin 3 of the 555 Timer IC  
through \_\_\_\_\_ .

- A. a 220 Ohm resistor
- B. a 10uF capacitor
- C. a 6.8k Ohm resistor
- D. a 1k Ohm resistor

A #2 You can adjust the speed of the blinking  
lights by using \_\_\_\_\_ .

- B
- C
- D
- A. the Diode
- B. the LED
- C. the Potentiometer
- D. transistor

#7 When this circuit is working, the LEDs will  
\_\_\_\_\_ ?

- A. remain on
- B. remain off permanently
- C. blink on and off alternately
- D. get hot and self-destruct

A #3 The two LEDs in this circuit are installed in  
\_\_\_\_\_ polarity.

- B
- C
- D
- A. the same
- B. amplifying
- C. dual
- D. opposite

#8 When an LED is \_\_\_\_\_ it  
means that the Anode is positive and the  
Cathode is negative.

- A. reverse-biased
- B. will not turn on
- C. forward biased
- D. will change from Red to Green

A #4 What is the value of the capacitor connected  
to Pin 2 of the 555 Timer IC in this circuit?

- B
- C
- D
- A. 1000uF
- B. 330uF
- C. 33uF
- D. 10uF

#9 When an LED is \_\_\_\_\_ it  
means that the Anode is negative and the  
Cathode is positive.

- A. will change from Red to Green
- B. forward-biased
- C. will not turn on
- D. reverse-biased

A #5 If we reverse the polarity of the battery snap  
on the circuit, what will happen?

- B
- C
- D
- A. it will work just fine
- B. the LED will burn out
- C. you might destroy the 555 Timer IC
- D. the LED will self-destruct

#10 A Potentiometer is also known as  
\_\_\_\_\_ .

- A. variable transistor
- B. fixed capacitor
- C. a variable resistor
- D. fixed resistor

Score	
-------	--



# QUIZ for Exp 19 or STEM KIT #19 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Continuity Tester Circuit” Experiment 19



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A

#1 This circuit uses 555 Timer IC working as a \_\_\_\_\_ .

B

A. an amplifier

C

B. a timer

D

C. a clock

D. a light generator

#6 Resistor R3 is connected to \_\_\_\_\_ of the 555 Timer IC.

A. Pin 3

B. Pin 4

C. Pin 1

D. Pin 6

A

#2 The loudness of the tone is \_\_\_\_\_ .

B

A. adjustable

C

B. fixed

D

C. controlled by Resistor R1

D. controlled by Capacitor C1

#7 When this circuit is working, the speaker will \_\_\_\_\_ when there is continuity.

A. remain silent

B. self-destruct

C. emit a tone

D. get hot

A

#3 The speaker in this circuit is connected to the \_\_\_\_\_ of transistor Q1.

B

A. Gate

C

B. Emitter

D

C. Collector

D. Base

#8 When you touch the two probes together, the speaker will \_\_\_\_\_ .

A. remain silent

B. self-destruct

C. get hot

D. emit a tone

A

#4 What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?

B

A. 0.01uF

C

B. 330uF

D

C. 33uF

D. 10uF

#9 One probe is connected to R1 and the other one is connected \_\_\_\_\_ .

A. to the negative of the battery

B. to the speaker

C. to the 0.01uF capacitor

D. to the positive of the battery

A

#5 If we reverse the polarity of the battery snap on the circuit, what will happen?

B

A. you might destroy the 555 Timer IC

C

B. the LED will burn out

D

C. it will work just fine

D. the LED will self-destruct

#10 This circuit emits \_\_\_\_\_ signal.

A. an inaudible

B. an rf

C. an ultrasonic

D. an audio

--



# QUIZ for Exp 20 or STEM KIT #20 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build an Audio Generator Circuit” Experiment 20



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** This circuit uses 555 Timer IC working as a \_\_\_\_\_ .

- A. a clock
- B. a timer
- C. an amplifier
- D. a light generator

**#6** Resistor R2 is connect to \_\_\_\_\_ of the 555 Timer IC.

- A. Pin 3
- B. Pin 4
- C. Pin 7
- D. Pin 6

- A
- B
- C
- D

- A
- B
- C
- D

**#2** The loudness of the tone is \_\_\_\_\_ .

- A. adjustable
- B. controlled by Resistor R1
- C. fixed
- D. controlled by Capacitor C1

**#7** When this circuit is working, the speaker will \_\_\_\_\_ .

- A. remain silent
- B. self-destruct
- C. emit a variable audiotone
- D. get hot

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The speaker in this circuit is connected to the \_\_\_\_\_ of transistor Q1.

- A. Collector
- B. Emitter
- C. Gate
- D. Base

**#8** To vary the frequency of this oscillator, you adjust \_\_\_\_\_ .

- A. the potentiometer
- B. the transistor
- C. 555 Timer IC
- D. battery snap

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?

- A. 10uF
- B. 330uF
- C. 33uF
- D. 0.01uF

**#9** Pins 4 and 8 on the 555 Timer IC are \_\_\_\_\_ .

- A. connected together
- B. are insulated from each other
- C. do not need to be connected
- D. are not important in this circuit

- A
- B
- C
- D

- A
- B
- C
- D

**#5** If we reverse the polarity of the battery snap on the circuit, what will happen?

- A. the LED will self-destruct
- B. the LED will burn out
- C. it will work just fine
- D. you might destroy the 555 Timer IC

**#10** The word ‘tone’ is the same thing as \_\_\_\_\_ .

- A. loudness
- B. pitch
- C. excitation
- D. bias

- A
- B
- C
- D

Score	
-------	--





# QUIZ for Exp 21 or STEM KIT #21 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build an Electronic Police Siren Circuit” Experiment 21

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** This circuit uses 555 Timer IC working as a \_\_\_\_\_ .

- A. a light generator
- B. a timer
- C. an amplifier
- D. clock

**#6** Resistors R5 and R6 are \_\_\_\_\_ .

- A. not connected
- B. connected
- C. not important
- D. are connected to pin 7

- A
- B
- C
- D

- A
- B
- C
- D

**#2** The loudness of the tone is \_\_\_\_\_ .

- A. adjustable
- B. controlled by Resistor R1
- C. controlled by Capacitor C1
- D. fixed

**#7** When this circuit is working, the speaker will \_\_\_\_\_ .

- A. remain silent
- B. self-destruct
- C. emit a variable audiotone
- D. get hot

- A
- B
- C
- D

- A
- B
- C
- D

**#3** The speaker in this circuit is connected to the \_\_\_\_\_ of transistor Q1.

- A. Base
- B. Emitter
- C. Gate
- D. Collector

**#8** To vary the frequency of this oscillator, you \_\_\_\_\_ .

- A. adjust the potentiometer
- B. use the pushbutton switch
- C. use the battery snap
- D. remove resistor R1

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What is the value of the capacitor connected to Pin 6 of the 555 Timer IC in this circuit?

- A. 10uF
- B. 330uF
- C. 33uF
- D. 0.01uF

**#9** The rising and falling of the frequency of the oscillator is controlled by \_\_\_\_\_ .

- A. the distance C2 is from the battery
- B. charging and discharging of C2
- C. charging and discharging of C1
- D. the size of the speaker

- A
- B
- C
- D

- A
- B
- C
- D

**#5** If we reverse the polarity of the battery snap on the circuit, what will happen?

- A. the LED will self-destruct
- B. the LED will burn out
- C. you might destroy the 555 Timer IC
- D. it will work just fine

**#10** Switch S1 is in series with \_\_\_\_\_ .

- A. C1 and C2
- B. R1 and R2
- C. R5 and R6
- D. R3 and R4

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 22 or STEM KIT #22 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Wake-Up Alarm Circuit” Experiment 22



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
- B
- C
- D

**#1** This circuit uses a \_\_\_\_\_ to sense light intensity?

- A. an SCR
- B. a 555 Timer IC
- C. a transistor
- D. a Photocell

**#6** Pins 4 and 8 of the 555 Timer IC are \_\_\_\_\_.

- A. connected
- B. are not connected
- C. are isolated from each other
- D. are not important

- A
- B
- C
- D

- A
- B
- C
- D

**#2** What pin on the 555 Timer is connected to a 220 Ohm resistor?

- A. 8
- B. 3
- C. 6
- D. 12

**#7** When the Photocell receives a lot of light, the alarm will \_\_\_\_\_.

- A. go silent
- B. make noise
- C. burn up
- D. give off moisture

- A
- B
- C
- D

- A
- B
- C
- D

**#3** With this circuit, you can generate a variety of interesting \_\_\_\_\_ by shadowing the surface of the Photocell with your hand.

- A. weather conditions
- B. electronic displays
- C. light displays
- D. sound effects

**#8** To increase the amplitude of the pulses coming from the output Pin 3 of the 555 Timer IC we use \_\_\_\_\_.

- A. an SCR
- B. a PNP transistor
- C. an NPN Transistor
- D. variable capacitor

- A
- B
- C
- D

- A
- B
- C
- D

**#4** What is the value of the capacitor connected to Pin 2 and Pin 6 of the 555 Timer IC in this circuit?

- A. 0.01uF
- B. 10uF
- C. 0.1uF
- D. 470uF

**#9** The Photocell is connected to Pins 7, 6, and \_\_\_\_\_.

- A. 8
- B. 4
- C. 1
- D. 2

- A
- B
- C
- D

- A
- B
- C
- D

**#5** How many pins on the 555 Timer IC do we use in this circuit?

- A. 7
- B. 3
- C. 8
- D. 1

**#10** Pin 1 of the 555 Timer IC is connected to the negative of the battery, to Pin 1 and \_\_\_\_\_.

- A. the Emitter of the NPN Transistor
- B. the Collector of the PNP Transistor
- C. the 100 Ohm resistor
- D. the speaker

- A
- B
- C
- D

Score	
-------	--



# QUIZ for Exp 23 or STEM KIT #23 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Variable Timer Circuit” Experiment 23



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit uses a 555 Timer IC as a \_\_\_\_\_ .  
**A.** a clock  
**B.** variable capacitor  
**C.** a timer  
**D.** variable resistor

**#6** If you want the LED to stay on longer, what would you do?  
**A.** replace C1 with 1000uF  
**B.** remove C1 from the circuit  
**C.** reduce the capacitance of C1  
**D.** short C1

A  
B  
C  
D

A  
B  
C  
D

**#2** What pin on the 555 Timer is connected to an LED?  
**A.** 8  
**B.** 3  
**C.** 6  
**D.** 12

**#7** The positive of C1 is connected to \_\_\_\_\_.  
**A.** Pin 4  
**B.** Pin 2  
**C.** Pin 6  
**D.** Pin 8

A  
B  
C  
D

A  
B  
C  
D

**#3** All the pins on the 555 Timer IC are used in this circuit except \_\_\_\_\_.  
**A.** Pin 5  
**B.** Pin 1  
**C.** Pin 8  
**D.** Pin 4

**#8** To ‘trigger’ the timer to start, you \_\_\_\_\_.  
**A.** apply a positive voltage to Pin 1  
**B.** remove the voltage from Pin 3  
**C.** increase the voltage on Pin 8  
**D.** apply a negative voltage to Pin 2

A  
B  
C  
D

A  
B  
C  
D

**#4** The Switch S1 is connected to Pin 2 and to \_\_\_\_\_.  
**A.** Pin 4  
**B.** Pin 6  
**C.** Pin 1  
**D.** Pin 3

**#9** The Potentiometer is connected to \_\_\_\_\_.  
**A.** Pins 7 and 8  
**B.** Pins 6 and 7  
**C.** Pins 4 and 5  
**D.** Pins 3 and 4

A  
B  
C  
D

A  
B  
C  
D

**#5** What is the purpose of the Potentiometer in this circuit?  
**A.** to vary how long the LED is ON  
**B.** to vary the volume of the sound  
**C.** to count the pulses  
**D.** to vary the brightness of the LED

**#10** The amount of time the LED remains on after the timer is ‘triggered’ depends on the values of R2, R4, and \_\_\_\_\_.  
**A.** R3  
**B.** C1  
**C.** R1  
**D.** the LED

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 24 or STEM KIT #24 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Moisture Detector Circuit” Experiment 24



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A **#1** This circuit uses a 555 Timer IC as a \_\_\_\_\_ .

B

C **A.** a clock

D **B.** variable capacitor

**C.** a timer

**D.** variable resistor

**#6** The more moisture in the soil, the \_\_\_\_\_ .

**A.** the slower the blinks of the LED

**B.** the hotter the LED gets

**C.** the faster the blinks of the LED

**D.** the higher the input voltage

A **#2** What is connected to pin 3 on the 555 Timer IC?

B **A.** an LED

C **B.** a 220 Ohm resistor

D **C.** a 10uF capacitor

**D.** a Photocell

**#7** Pin 1 of the 555 Timer IC is connected is connected to \_\_\_\_\_ .

**A.** the negative of the battery.

**B.** Pin 5

**C.** the positive of the battery

**D.** the positive of C1

A **#3** On the 555 Timer \_\_\_\_\_ .

B **A.** only 6 pins are used

C **B.** all but pin 5 are used

D **C.** all 8 pins are used

**D.** all but pin 4 are used

**#8** To make sure the circuit is working, you \_\_\_\_\_ .

**A.** touch the probes together

**B.** short capacitor C1

**C.** remove the LED

**D.** disconnect the battery

A **#4** The purpose of this circuit is to \_\_\_\_\_ in soil.

B **A.** sense moisture

C **B.** sense vibrations

D **C.** sense heat

**D.** sense light

**#9** Pins 6 and 2 are \_\_\_\_\_ .

**A.** not connected

**B.** connected

**C.** not important

**D.** determine the brightness of the LED.

A **#5** What controls the frequency of the output tone?

B **A.** humidity in the air

C **B.** the air temperature

D **C.** resistance between the probes

**D.** the brightness of the sun

**#10** If the soil is dry, the LED will \_\_\_\_\_ .

**A.** blink

**B.** remain either ON or OFF

**C.** get hot

**D.** the LED will self-destruct

Score	
-------	--



# QUIZ for Exp 25 or STEM KIT #25 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing

## “Build a Code Oscillator Circuit” Experiment 25



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit uses a 555 Timer IC as \_\_\_\_\_ .  
A. a variable resistor  
B. a variable capacitor  
C. a timer  
D. a clock

**#6** The loudness of the emitted tone \_\_\_\_\_ .  
A. is fixed  
B. is adjustable by the value of R1  
C. is adjustable by the value of C1  
D. is controlled by S1

A  
B  
C  
D

A  
B  
C  
D

**#2** R3 is connected to pin 3 on the 555 Timer IC and to the \_\_\_\_\_ on Q1.  
A. Emitter  
B. Base  
C. Collector  
D. Anode

**#7** If you do not press the pushbutton switch, the circuit \_\_\_\_\_ .  
A. will consume power  
B. will cause the speaker to emit a tone  
C. will apply voltage to the 555 Timer IC  
D. will not consume power

A  
B  
C  
D

A  
B  
C  
D

**#3** On the 555 Timer \_\_\_\_\_ .  
A. only 6 pins are used  
B. all but pin 5 are used  
C. all 8 pins are used  
D. all but pin 4 are used

**#8** To make sure the circuit is working, you \_\_\_\_\_ .  
A. press the pushbutton switch to make a tone  
B. short capacitor C1  
C. remove the LED  
D. disconnect the battery

A  
B  
C  
D

A  
B  
C  
D

**#4** The purpose of this circuit is to \_\_\_\_\_ as you press the pushbutton switch.  
A. sense moisture  
B. sense vibrations  
C. emit an audio tone  
D. sense light

**#9** Pins 4 and 8 are \_\_\_\_\_ .  
A. not connected  
B. connected  
C. not important  
D. determine the brightness of the LED.

A  
B  
C  
D

A  
B  
C  
D

**#5** How do you send Morse Code with this oscillator circuit?  
A. you press the pushbutton switch  
B. you squeeze resistor R1  
C. you remove the 10 Ohm resistor  
D. you adjust the speaker

**#10** What controls the speed at which you send code with this oscillator?  
A. the battery  
B. the speaker  
C. you do.  
D. the transistor

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 26 or STEM KIT #26 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an Audible Water Detector Circuit” Experiment 26

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit uses a 555 Timer IC as \_\_\_\_\_ .  
A. a variable resistor  
B. a variable capacitor  
C. a clock  
D. a timer

**#6** The loudness of the emitted tone \_\_\_\_\_ .  
A. is fixed  
B. is adjustable by the value of R1  
C. is adjustable by the value of C1  
D. is controlled by S1

A  
B  
C  
D

A  
B  
C  
D

**#2** R4 is connected to \_\_\_\_\_ and to the positive of the battery.  
A. the speaker  
B. the transistor  
C. the 555 Timer IC  
D. the capacitor C1

**#7** Resistors R1 and R2 \_\_\_\_\_ .  
A. are connected  
B. are not connected  
C. are not important in the circuit  
D. control the loudness of the speaker

A  
B  
C  
D

A  
B  
C  
D

**#3** On the 555 Timer \_\_\_\_\_ .  
A. only 6 pins are used  
B. all but pin 4 are used  
C. all 8 pins are used  
D. all but pin 5 are used

**#8** To make sure the circuit is working, you \_\_\_\_\_ .  
A. remove resistor R4  
B. short capacitor C1  
C. put the probes into water  
D. disconnect the battery

A  
B  
C  
D

A  
B  
C  
D

**#4** The purpose of this circuit is to \_\_\_\_\_ .  
A. sense the presence of water  
B. sense vibrations  
C. sense heat  
D. sense light

**#9** Pins 1 and 3 of the 555 Timer IC are \_\_\_\_\_ .  
A. not connected  
B. connected  
C. not important  
D. determine the loudness of the speaker

A  
B  
C  
D

A  
B  
C  
D

**#5** What happens when this circuit is triggered?  
A. you hear a tone in the speaker  
B. you hear a loud cracking sound  
C. an LED starts blinking  
D. the capacitor gets hot

**#10** Capacitor C1 is connected to Pin 1 and to \_\_\_\_\_ .  
A. Pin 8  
B. Pin 7  
C. Pin 4  
D. the Emitter of transistor Q1

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 27 or STEM KIT #27 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an English Police Siren Circuit” Experiment 27

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit uses a 555 Timer IC as \_\_\_\_\_ .  
A. a clock  
B. a variable capacitor  
C. a variable resistor  
D. a timer

**#6** The loudness of the emitted tone \_\_\_\_\_ .  
A. is controlled by S1  
B. is adjustable by the value of R1  
C. is adjustable by the value of C1  
D. is fixed

A  
B  
C  
D

A  
B  
C  
D

**#2** R5 is connected to R1, R2 , Switch S1 and to \_\_\_\_\_ .  
A. Pin 7  
B. the transistor  
C. the speaker  
D. capacitor C1

**#7** Resistors R1, R2 and R5 \_\_\_\_\_ .  
A. are not connected  
B. control the loudness of the speaker  
C. are not important in the circuit  
D. are connected

A  
B  
C  
D

A  
B  
C  
D

**#3** On the 555 Timer \_\_\_\_\_ .  
A. all but pin 5 are used  
B. all but pin 4 are used  
C. all 8 pins are used  
D. only 6 pins are used

**#8** When this circuit is working correctly, as soon as you \_\_\_\_\_ it will emit a tone.  
A. press the switch S1  
B. connect the battery  
C. remove the 555 Timer IC  
D. install capacitor C1

A  
B  
C  
D

A  
B  
C  
D

**#4** The purpose of this circuit is to \_\_\_\_\_ .  
A. emit a siren sound  
B. emit bird chirps  
C. sense heat  
D. sense light

**#9** Pressing Switch S1 puts \_\_\_\_\_ in parallel.  
A. R1 and R2  
B. R2 and R3  
C. R5 and R2  
D. R4 and R5

A  
B  
C  
D

A  
B  
C  
D

**#5** How do you make the circuit emit two tones?  
A. connect and disconnect the battery  
B. remove and replace the 10 Ohm resistor  
C. press and release the pushbutton switch  
D. squeeze capacitor C1

**#10** In order to shut off this circuit, you must \_\_\_\_\_ .  
A. disconnect the battery  
B. hold down the pushbutton switch  
C. hold your ears  
D. change capacitor C1 to a different value

A  
B  
C  
D

Score	
-------	--



# QUIZ for Exp 28 or STEM KIT #28 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an Electronic Canary Circuit” Experiment 28

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A  
B  
C  
D

**#1** This circuit uses a 555 Timer IC and \_\_\_\_\_ .  
**A.** an SCR  
**B.** a variable capacitor  
**C.** a two-transistor oscillator  
**D.** a Photocell

**#6** The output of the two-transistor oscillator is fed into \_\_\_\_\_ of the 555 Timer IC .  
**A.** Pin 5  
**B.** Pin 6  
**C.** Pin 7  
**D.** Pin 8

A  
B  
C  
D

A  
B  
C  
D

**#2** R1 is connected to \_\_\_\_\_ .  
**A.** R3  
**B.** R7  
**C.** C1  
**D.** R2

**#7** Switch S1 is connected to \_\_\_\_\_ .  
**A.** Pin 4  
**B.** Pin 1  
**C.** Pin 3  
**D.** Pin 6

A  
B  
C  
D

A  
B  
C  
D

**#3** On the 555 Timer \_\_\_\_\_ .  
**A.** all but pin 5 are used  
**B.** all but pin 4 are used  
**C.** all 8 pins are used  
**D.** only 6 pins are used

**#8** One side of the speaker is connected directly to \_\_\_\_\_ .  
**A.** the Base of Q1  
**B.** the Emitter of Q2  
**C.** Pin 2 on the 555 Timer IC  
**D.** the positive of the battery

A  
B  
C  
D

A  
B  
C  
D

**#4** The purpose of this circuit is to \_\_\_\_\_ .  
**A.** emit a siren sound  
**B.** emit bird chirps  
**C.** sense heat  
**D.** sense light

**#9** C4 and R6 are connected in parallel to the speaker and \_\_\_\_\_ of the 555 Timer IC.  
**A.** Pin 3  
**B.** Pin 4  
**C.** Pin 5  
**D.** Pin 8

A  
B  
C  
D

A  
B  
C  
D

**#5** How do you make the circuit emit different tones?  
**A.** connect and disconnect the battery  
**B.** adjust R7 and press the pushbutton  
**C.** vary the heat in the room  
**D.** feed it birdseed

**#10** Capacitor C1 is part of \_\_\_\_\_ .  
**A.** the two-transistor oscillator circuit  
**B.** the voltage regulator circuit  
**C.** the power supply circuit  
**D.** output circuit

A  
B  
C  
D

Score	
-------	--





# QUIZ for Exp 29 or STEM KIT #29 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build a fantasy Space Machine Gun Circuit” Experiment 29

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- |                  |  |                  |
|------------------|--|------------------|
| A<br>B<br>C<br>D | <b>#1</b> This circuit uses a 555 Timer IC and _____ .<br><br><b>A.</b> an SCR<br><b>B.</b> a variable capacitor<br><b>C.</b> a Photocell<br><b>D.</b> a two-transistor oscillator   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#2</b> R4 is connected to _____ .<br><br><b>A.</b> Pin 7<br><b>B.</b> R7<br><b>C.</b> C1<br><b>D.</b> R2  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#3</b> On the 555 Timer _____ .<br><br><b>A.</b> all 8 pins are used<br><b>B.</b> all but pin 4 are used<br><b>C.</b> all but pin 5 are used<br><b>D.</b> only 6 pins are used  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#4</b> The purpose of this circuit is to _____ .<br><br><b>A.</b> emit a siren sound<br><b>B.</b> emit bird chirps<br><b>C.</b> emit phasor machine gun sounds<br><b>D.</b> emit crunching sounds   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#5</b> In addition to fantasy machine gun sounds what else does the circuit do?<br><br><b>A.</b> vibrates like a snake<br><b>B.</b> chirps like a bird<br><b>C.</b> varies the heat in the room<br><b>D.</b> emits a light effect with an LED | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#6</b> The Collector of transistor Q2 is connected to _____ of the 555 Timer IC.<br><br><b>A.</b> Pin 5<br><b>B.</b> Pin 6<br><b>C.</b> Pin 7<br><b>D.</b> Pin 8  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#7</b> Switch S1 is connected to _____ .<br><br><b>A.</b> the positive of the battery<br><b>B.</b> resistor R6<br><b>C.</b> the Base of transistor Q2<br><b>D.</b> the negative of the battery  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#8</b> One side of the speaker is connected directly to _____ .<br><br><b>A.</b> an LED<br><b>B.</b> Pin 3 on the 555 Timer IC<br><b>C.</b> Pin 7 on the 555 Timer IC<br><b>D.</b> the positive of the battery                                | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#9</b> The Anode of the LED is connected directly to _____ .<br><br><b>A.</b> Pin 3<br><b>B.</b> the positive of the battery<br><b>C.</b> the negative of the battery<br><b>D.</b> Pin 7  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#10</b> Resistor R5 is connected across _____ .<br><br><b>A.</b> pins 6 and 7 of the 555 Timer IC<br><b>B.</b> the speaker<br><b>C.</b> the power supply circuit<br><b>D.</b> output circuit  | A<br>B<br>C<br>D |

Score	
-------	--



# QUIZ for Exp 30 or STEM KIT #30 in the Mr Circuit Electronics Training Lab 1



This Quiz covers the training learned by completing



## “Build an Ultrasonic Pest Repeller Circuit” Experiment 30

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- |                  |  |                  |
|------------------|--|------------------|
| A<br>B<br>C<br>D | <b>#1</b> This circuit uses a 555 Timer IC and _____ .<br><b>A.</b> a two-transistor oscillator<br><b>B.</b> a variable capacitor<br><b>C.</b> a Photocell<br><b>D.</b> an SCR   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#2</b> R6 is connected to _____ .<br><b>A.</b> Pin 7<br><b>B.</b> R7<br><b>C.</b> C1<br><b>D.</b> Pin 3   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#3</b> On the 555 Timer _____ .<br><b>A.</b> all but pin 4 are used<br><b>B.</b> all 8 pins are used<br><b>C.</b> all but pin 5 are used<br><b>D.</b> only 6 pins are used  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#4</b> The purpose of this circuit is to _____ .<br><b>A.</b> emit a siren sound<br><b>B.</b> emit ultrasonic sounds<br><b>C.</b> emit phasor machine gun sounds<br><b>D.</b> emit crunching sounds                                 | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#5</b> What are the signals from this circuit supposed to do?<br><b>A.</b> repel pests<br><b>B.</b> chirp like a birds<br><b>C.</b> varies the heat in the room<br><b>D.</b> vibrate like a snake                                   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#6</b> The frequencies that may repel pests are from 13.5 thousand cycles per second to _____ .<br><b>A.</b> 1 Megacycle (1Mhz)<br><b>B.</b> 80 thousand cycles per second (80kHz)<br><b>C.</b> 25 Giga Hz<br><b>D.</b> 10 milli Hz | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#7</b> How can you tell if the circuit is working?<br><b>A.</b> you can feel the speaker vibrate<br><b>B.</b> resistor R6 will be smoking<br><b>C.</b> the LED will light up<br><b>D.</b> the battery will be hot                   | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#8</b> One side of the speaker is connected directly to _____ .<br><b>A.</b> the positive of the battery<br><b>B.</b> Pin 3 on the 555 Timer IC<br><b>C.</b> Pin 7 on the 555 Timer IC<br><b>D.</b> an LED                          | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#9</b> C1 is 10uF and it is part of the _____ .<br><b>A.</b> two-transistor oscillator<br><b>B.</b> power supply circuit<br><b>C.</b> output circuit<br><b>D.</b> heat sensing circuit  | A<br>B<br>C<br>D |
| A<br>B<br>C<br>D | <b>#10</b> What capacitor is connected to R3 and R4?<br><b>A.</b> C1<br><b>B.</b> C2<br><b>C.</b> C3<br><b>D.</b> Q2   | A<br>B<br>C<br>D |

Score	
-------	--

## QUICK-CHECK ANSWER KEY for Lesson 1 QUIZ for Mr Circuit Electronics Training (“Electron “Theory”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> Everything around you is made of ____ .</p> <p>A. wood B. matter C. steel D. water</p>	<p><b>#6</b> Atoms have a central core called _____ .</p> <p>A. a middle section B. a nucleus C. a slice D. a modicum</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#2</b> Matter is made up of _____ .</p> <p>A. water B. steel C. elements D. wood</p>	<p><b>#7</b> What are the positively charged particles in an atom called?</p> <p>A. protons B. products C. add ons D. neutrons</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#3</b> Atoms are what make up _____ .</p> <p>A. elements B. protons C. electrons D. neutrons</p>	<p><b>#8</b> A particle in an atom that has no electrical charge is called _____ .</p> <p>A. a nothing B. a widget C. a neutron D. an axion</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#4</b> In the nucleus of _____ are protons and neutrons.</p> <p>A. an electron B. a proton C. an atom D. a neutron</p>	<p><b>#9</b> The part of Physics that studies the movement of electrons is called _____ .</p> <p>A. resistance B. conductance C. capacitance D. electronics</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> The movement of electrons from atom to atom is called _____ .</p> <p>A. an electron current B. an electron charge C. an electron resistance D. a neutron flow</p>	<p><b>#10</b> What circulates through the filament of an incandescent bulb to make it light up?</p> <p>A. electrons B. magnets C. protons D. neutrons</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Lesson 2 QUIZ for Mr Circuit Electronics Training (“Component Identification”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> What is the primary function of a battery in a circuit?</p> <p>A. store electric energy B. serve as a paper weight C. give resistance to a circuit D. amplify electricity</p>	<p><b>#6</b> Which type of capacitor generally stores relatively large amount of electric charge?</p> <p>A. a ceramic disc capacitor B. an electrolytic capacitor C. a surface mount capacitor D. a mica capacitor</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> What is the primary function of a resistor?</p> <p>A. resist proton flow B. add color to your circuit C. count electrons D. limit or control current</p>	<p><b>#7</b> What component varies its resistance according to the light intensity?</p> <p>A. a Photocell B. a Transistor C. a 555 Timer IC D. an SCR</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> What is the primary function of an LED?</p> <p>A. control electron flow B. light up when current flows through it C. provide heat to keep you warm D. store electrons</p>	<p><b>#8</b> What component has an Emitter, Base, and Collector?</p> <p>A. a Transistor B. an SCR C. a Diode D. a Potentiometer</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#4</b> Which set of components has a schematic symbol that includes a ‘squiggly’ line?</p> <p>A. a resistor, a photocell, and a potentiometer B. a capacitor and an SCR C. an LED and a Battery D. an Integrated Circuit and a Speaker</p>	<p><b>#9</b> Which of these component has a Gate, an Anode, and a Cathode lead?</p> <p>A. an SCR B. a Transistor C. a Diode D. a Resistor</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#5</b> Which of these has a ‘diode symbol’ as part of its symbol?</p> <p>A. a Diode B. an SCR C. an LED D. All the above</p>	<p><b>#10</b> What is the purpose of a speaker?</p> <p>A. convert electrical currents into sound waves B. use power C. be an adjustable capacitor D. take up space in a circuit</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Lesson 3 QUIZ for Mr Circuit Electronics Training (“Resistor Color Code”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A <input checked="" type="radio"/> B C D</p>	<p><b>#1</b> A resistor of 10,000 Ohms has _____ than a resistor of 1,000 Ohms.</p> <p>A. less opposition to current flow B. more opposition to current flow C. less Ohms D. larger physical size</p>	<p><b>#6</b> What does the color green stand for in the Resistor Color Code?</p> <p>A. 5 B. 9 C. 0 D. 3</p>	<p><input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D</p>
<p>A B <input checked="" type="radio"/> C D</p>	<p><b>#2</b> Resistance in electronics is the _____.</p> <p>A. encouragement to current flow B. not important C. opposition to current flow D. storage of electrons</p>	<p><b>#7</b> What is the value in Ohms of a resistor with color bands of yellow, violet, black, gold?</p> <p>A. 55,000 Ohms B. 360 Ohms C. 47 Ohms D. 68k Ohms</p>	<p>A B <input checked="" type="radio"/> C D</p>
<p><input checked="" type="radio"/> A B C D</p>	<p><b>#3</b> The fourth color band on a <math>\pm 5\%</math> resistor is what color?</p> <p>A. gold B. silver C. black D. red</p>	<p><b>#8</b> If the fourth or last band on a resistor is the color silver, what is the tolerance?</p> <p>A. <math>\pm 10\%</math> B. <math>\pm 5\%</math> C. <math>\pm 3\%</math> D. <math>\pm 2\%</math></p>	<p><input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D</p>
<p><input checked="" type="radio"/> A B C D</p>	<p><b>#4</b> Why do we put color bands on resistors?</p> <p>A. because numbers would be very small B. because colors make the circuit work better C. electronics likes many colors D. to test for colorblindness</p>	<p><b>#9</b> There are four bands on a <math>\pm 5\%</math> resistor. The first two colors represent _____.</p> <p>A. alpha numerics B. alpha characters C. negative numbers D. numerals</p>	<p>A B C <input checked="" type="radio"/> D</p>
<p>A <input checked="" type="radio"/> B C D</p>	<p><b>#5</b> What is the purpose for the Resistor Color Code?</p> <p>A. to hide the value of the resistor B. to determine the Ohms of the resistor C. to add color to the circuit D. to make it hard to read the value in Ohms</p>	<p><b>#10</b> In the Resistor Color Code, what is the color that represents ‘2’?</p> <p>A. Orange B. Violet C. Red D. Black</p>	<p>A B <input checked="" type="radio"/> C D</p>

## QUICK-CHECK ANSWER KEY for Lesson 4 QUIZ for Mr Circuit Electronics Training (“Solderless Circuit Board”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#1</b> Why do we use a Solderless Circuit Board to assemble circuits?</p> <p>A. to make the circuit more permanent</p> <p>B. to add more resistance to the circuit</p> <p>C. to slow down the electrons</p> <p>D. to make connections without soldering</p>	<p><b>#6</b> Each hole in the Solderless Circuit Board is designed to accept how many wires or leads?</p> <p>A. 1</p> <p>B. 5</p> <p>C. 3</p> <p>D. 14</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#2</b> What is the purpose of the channel down the middle of the solderless circuit board?</p> <p>A. to be able to install Integrated Circuits</p> <p>B. to release moisture from the circuit</p> <p>C. to separate resistors from capacitors</p> <p>D. to count the components in the circuit</p>	<p><b>#7</b> On the Solderless Circuit Board, an Integrated Circuit is installed _____ .</p> <p>A. anywhere you like</p> <p>B. on one side of the other</p> <p>C. hanging off the edge of the board</p> <p>D. straddling the center channel</p>	<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#3</b> Each hole in a ‘vertical group’ or set of 5 holes is _____ .</p> <p>A. not connected electrically</p> <p>B. full of high resistance</p> <p>C. electrically connected</p> <p>D. has a high voltage</p>	<p><b>#8</b> Inside the holes in the Solderless Circuit Board are clips made of _____ .</p> <p>A. plastic</p> <p>B. wood</p> <p>C. metal</p> <p>D. pvc material</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>
<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>	<p><b>#4</b> A Solderless Circuit Board is _____ .</p> <p>A. not reusable</p> <p>B. reusable</p> <p>C. never used by technicians and engineers</p> <p>D. difficult to find</p>	<p><b>#9</b> Why are there numbers and letters on the Solderless Circuit Board?</p> <p>A. for decoration</p> <p>B. to practice counting</p> <p>C. to identify each and every hole</p> <p>D. for no real purpose</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#5</b> How many sets of 5 holes are there on the Solderless Circuit Board provided?</p> <p>A. 22</p> <p>B. 660</p> <p>C. 500</p> <p>D. 60</p>	<p><b>#10</b> The 5 holes in a vertical group on a Solderless Circuit Board are all _____ .</p> <p>A. shorted together</p> <p>B. not shorted together</p> <p>C. are insulated from each other</p> <p>D. are glued together</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 01 QUIZ for Mr Circuit Electronics Training (“Resistor”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> In Experiment #1, the brightness of the LED depends on _____.</p> <p>A. the capacitor value in the circuit</p> <p>B. the value of the resistor in the circuit</p> <p>C. the solderless circuit board</p> <p>D. the battery snap</p>	<p><b>#6</b> The short lead on an LED is?</p> <p>A. the Gate</p> <p>B. the Anode</p> <p>C. the Cathode</p> <p>D. the Positive</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#2</b> Of the four values of resistors in Exp. #1, which value caused the LED to be the brightest?</p> <p>A. 100 ohm</p> <p>B. 220 ohm</p> <p>C. 1k ohm</p> <p>D. 6.8k ohm</p>	<p><b>#7</b> What are the colors on a 1000 Ohm <math>\pm 5\%</math> resistor?</p> <p>A. brown, black, red, gold</p> <p>B. green, blue, red, silver</p> <p>C. blue, gray, red, gold</p> <p>D. brown, red, green silver</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#3</b> What color is the third band on the 6.8k ohm resistor?</p> <p>A. blue</p> <p>B. green</p> <p>C. black</p> <p>D. red</p>	<p><b>#8</b> With an LED in a circuit, the more _____, the greater the brightness.</p> <p>A. air</p> <p>B. capacitance</p> <p>C. current</p> <p>D. light</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#4</b> Which side of battery does the electron current flow from?</p> <p>A. positive side</p> <p>B. left side</p> <p>C. negative side</p> <p>D. top side</p>	<p><b>#9</b> To reduce the amount of current flowing in a circuit, you can _____ the amount of resistance.</p> <p>A. increase</p> <p>B. decrease</p> <p>C. rotate</p> <p>D. circle</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#5</b> What is the color of the positive lead on the battery snap?</p> <p>A. green</p> <p>B. red</p> <p>C. black</p> <p>D. yellow</p>	<p><b>#10</b> Of the four values of resistors in Exp. #1, which value caused the LED to be the dimmest?</p> <p>A. 100 ohm</p> <p>B. 220 ohm</p> <p>C. 1k ohm</p> <p>D. 6.8k ohm</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 02 QUIZ for Mr Circuit Electronics Training (“Potentiometer”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> Between which leads on the Potentiometer in Experiment #02 does the resistance measure the maximum?</p> <p><b>A.</b> leads A and B</p> <p><b>B.</b> leads A and C</p> <p><b>C.</b> leads C and B</p> <p><b>D.</b> there is no maximum resistance</p>	<p><b>#6</b> What is the function of the Potentiometer in Exp. #2?</p> <p><b>A.</b> to vary the capacitance in the circuit</p> <p><b>B.</b> to reduce proton flow</p> <p><b>C.</b> to slow down the speed of the electrons</p> <p><b>D.</b> to vary the resistance in the circuit</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#2</b> The ‘cursor’ on the Potentiometer is connected to which lead?</p> <p><b>A.</b> C</p> <p><b>B.</b> A</p> <p><b>C.</b> it is not connected to any lead</p> <p><b>D.</b> B</p>	<p><b>#7</b> In Exp. #2, what is the purpose of the 100 ohm resistor in the circuit?</p> <p><b>A.</b> to protect the LED from burning out</p> <p><b>B.</b> to increase the amount of current flowing</p> <p><b>C.</b> to make the circuit more interesting</p> <p><b>D.</b> to increase the parts used in the circuit</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> The resistance value of the Potentiometer is zero when the ‘cursor’ is moved next to which lead?</p> <p><b>A.</b> B</p> <p><b>B.</b> A</p> <p><b>C.</b> black</p> <p><b>D.</b> C</p>	<p><b>#8</b> When you twist the shaft on a Potentiometer, it varies its _____.</p> <p><b>A.</b> resistance</p> <p><b>B.</b> capacitance</p> <p><b>C.</b> area</p> <p><b>D.</b> wattage</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#4</b> Does the polarity of the battery connection matter in this circuit?</p> <p><b>A.</b> NO</p> <p><b>B.</b> it is not important</p> <p><b>C.</b> YES</p> <p><b>D.</b> the LED will light up either way</p>	<p><b>#9</b> To set the Potentiometer at its maximum resistance you have to move the ‘cursor’ next to which lead?</p> <p><b>A.</b> B</p> <p><b>B.</b> A</p> <p><b>C.</b> black</p> <p><b>D.</b> C</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#5</b> In Exp. #2, what is the name of the electronic component that you are learning about?</p> <p><b>A.</b> the Potentiometer</p> <p><b>B.</b> an LED</p> <p><b>C.</b> a capacitor</p> <p><b>D.</b> a battery snap</p>	<p><b>#10</b> The LED is the brightest when the ‘cursor’ on the Potentiometer is next to which lead?</p> <p><b>A.</b> B</p> <p><b>B.</b> A</p> <p><b>C.</b> black</p> <p><b>D.</b> C</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>



## QUICK-CHECK ANSWER KEY for Experiment 03 QUIZ for Mr Circuit Electronics Training (“Photocell”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 How many leads does a Photocell have?

- B  
 A. 1  
 C. 2  
 D. 3  
 D. 6

**A** #6 This circuit has three components. They are the battery snap, a resistor, and a \_\_\_\_\_.

- A. Photocell  
 B. Potentiometer  
 C. capacitor  
 D. microphone

**B** #2 Does a Photocell have polarity?

- A. YES  
 B. NO  
 C. maybe  
 D. not necessarily

**A** #7 In this experiment, what do we use to shield the light from hitting the Photocell?

- A. a flashlight  
 B. a fork  
 C. a hand  
 D. a forklift

**A** #3 In order for a Photocell to vary its resistance, light has to hit the \_\_\_\_\_.

- B  
 A. top surface  
 C. bottom surface  
 D. the leads  
 D. the left side

**A** #8 A Photocell changes its resistance because it is sensitive to \_\_\_\_\_.

- A. air  
 B. pressure  
 C. gravity  
 D. light

**B** #4 If you reverse the leads on the battery snap, how will that affect the circuit?

- A. the LED will be brighter  
 B. the circuit will work just fine  
 C. the LED will get hot and burn up  
 D. the LED will not light up

**A** #9 When you block the amount of light hitting a Photocell, its resistance \_\_\_\_\_.

- A. is not affected  
 B. decreases  
 C. causes more capacitance in the circuit  
 D. increases

**C** #5 If you put this circuit into a dark room, how will that affect the LED brightness?

- A. it will be super bright  
 B. it will burn out  
 C. it will be dimmer  
 D. it will be the same as in bright light

**B** #10 How does the brightness of the light that hits the Photocell affect the LED in the circuit?

- A. has no effect at all  
 B. brighter the light, brighter the LED  
 C. LEDs don't get brighter or dimmer  
 D. dimmer the light, brighter the LED

## QUICK-CHECK ANSWER KEY for Experiment 04 QUIZ for Mr Circuit Electronics Training (“Capacitor”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> In Experiment #4, what is the component that you learned about?</p> <p>A. a capacitor B. a resistor C. an LED D. a battery snap</p>	<p><b>#6</b> What happens to the LED if we reverse the polarity on the battery?</p> <p>A. it lights up just fine B. it burns out the LED C. the LED will not light up D. the LED will get hot</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#2</b> In Exp. #4, how many resistors do we use?</p> <p>A. 1 B. 2 C. 3 D. 4</p>	<p><b>#7</b> The more capacitance a capacitor has, the _____ electrical charge it will hold.</p> <p>A. less B. fuzzier C. worse D. more</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> In Exp. #4, when you disconnect the battery, the LED remains lit for a time because _____.</p> <p>A. the two resistors keep it lit B. the energy stored in the capacitor keeps it lit C. LEDs store electrons D. your eyes are playing tricks on you.</p>	<p><b>#8</b> Which value of capacitor will hold more electrical charge?</p> <p>A. 1000uF B. 100uF C. 10uF D. 1uF</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#4</b> What happens to the LED when we reduce the value of the capacitor in the circuit and then disconnect the battery?</p> <p>A. The LED remains lit for a longer time. B. The LED will burn out. C. The LED remains lit for shorter time. D. It will have no effect on the LED.</p>	<p><b>#9</b> What is the purpose of a capacitor in a circuit?</p> <p>A. to vary the resistance B. to store inductance C. to store an electrical charge D. to increase the wattage</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#5</b> In Exp. #4, what type of capacitor are we using?</p> <p>A. an electrolytic capacitor B. a ceramic disc capacitor C. a polyester film capacitor D. a variable capacitor</p>	<p><b>#10</b> Does the capacitor in this circuit have polarity?</p> <p>A. NO B. can't tell C. YES D. its an inductor</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 05 QUIZ for Mr Circuit Electronics Training (“Speaker”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#1</b> What would happen in this circuit if you reverse the polarity of the battery snap?</p> <p>A. the speaker will burn out</p> <p>B. it will not work at all</p> <p>C. the speaker will whistle</p> <p>D. it will work just fine</p>	<p><b>#6</b> What is the name of the part we learn about in Exp. #5?</p> <p>A. a speaker</p> <p>B. a capacitor</p> <p>C. a resistor</p> <p>D. a photocell</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>	<p><b>#2</b> What do you think the purpose of the 10 Ohm resistor is in this circuit?</p> <p>A. to increase the amount of current</p> <p>B. to reduce the amount of current</p> <p>C. to increase the capacitance</p> <p>D. to decrease the inductance</p>	<p><b>#7</b> What is the function of the part we learn about in Exp. #5?</p> <p>A. reduce the amount of current flow</p> <p>B. to store electrons and protons</p> <p>C. transform electrical energy to sound waves</p> <p>D. to look nice in a circuit</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>
<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#3</b> When you reverse the polarity of the battery snap in this circuit, it affects the _____ of the speaker.</p> <p>A. cone</p> <p>B. magnet</p> <p>C. volume</p> <p>D. sound quality</p>	<p><b>#8</b> What part of a Speaker moves when current flows through it?</p> <p>A. the bracket</p> <p>B. the magnet</p> <p>C. the handle</p> <p>D. the cone</p>	<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#4</b> Why does the sound stop when you leave the battery connected?</p> <p>A. the magnet gets weak</p> <p>B. the speaker burns out</p> <p>C. the cone stops moving</p> <p>D. the current increases</p>	<p><b>#9</b> What sound comes out of a speaker when a steady DC current is connected to its coil?</p> <p>A. it makes a steady tone</p> <p>B. it makes a click and then becomes silent</p> <p>C. it plays music</p> <p>D. it sounds like a siren</p>	<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>
<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> Why does the speaker make a ‘click’ when you connect and when you disconnect the battery?</p> <p>A. the cone moves each time</p> <p>B. the speaker is alive</p> <p>C. the magnet is weak</p> <p>D. the speaker is round</p>	<p><b>#10</b> What kind of device is a Speaker?</p> <p>A. rectifying device</p> <p>B. electromechanical device</p> <p>C. photoelectric device</p> <p>D. semiconductor device</p>	<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 06 QUIZ for Mr Circuit Electronics Training (“Diode”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 In Experiment #6, what is the component that you learned about?

- B**  
**C**  
**D**
- A.** a capacitor
  - B.** a diode
  - C.** an LED
  - D.** a battery snap

**#6** The arrow on the schematic symbol for a diode points to the \_\_\_\_\_ .

- A.** Anode
- B.** Gate
- C.** Door
- D.** Cathode

- A**  
**B**  
**C**  
 **D**

**A** #2 A diode allows current to flow through it \_\_\_\_\_ .

- B**  
**C**  
**D**
- A.** freely both ways
  - B.** in one direction only
  - C.** if it is warm
  - D.** only if there is a resistor in the circuit

**#7** An LED is also a type of \_\_\_\_\_ .

- A.** inductor
- B.** diode
- C.** capacitor
- D.** speaker

- A**  
 **B**  
**C**  
**D**

**A** #3 How is the Cathode side of a diode marked on the diode itself?

- B**  
 **C**  
**D**
- A.** with a double color stripe
  - B.** with an arrow
  - C.** with a white band around one end
  - D.** with an asterisk

**#8** If we were to increase the value of the resistor in the circuit from 220 Ohms to 1000 Ohms, how would that affect the LED?

- A.** the LED would increase its brightness
- B.** the LED would reduce in brightness
- C.** the current flow in the LED would increase
- D.** the brightness would stay the same

- A**  
 **B**  
**C**  
**D**

**A** #4 A diode allows an easy flow of electrons from \_\_\_\_\_ to \_\_\_\_\_ .

- B**  
**C**  
 **D**
- A.** top, bottom
  - B.** bottom, top
  - C.** Anode, Cathode
  - D.** Cathode, Anode

**#9** If the LED lights up the same regardless of the polarity of the diode in the circuit, what would we assume?

- A.** the LED is defective
- B.** the diode is working fine
- C.** the battery is weak
- D.** the diode is defective

- A**  
**B**  
**C**  
 **D**

**A** #5 In Exp. #6, what component do we use to indicate that current is flowing?

- B**  
**C**  
**D**
- A.** a speaker
  - B.** an LED
  - C.** an electrolytic capacitor
  - D.** a disc capacitor

**#10** A diode is considered a \_\_\_\_\_ .

- A.** simple resistor
- B.** one-way gate
- C.** a variable resistor
- D.** a simple capacitor

- A**  
 **B**  
**C**  
**D**

## QUICK-CHECK ANSWER KEY for Experiment 07 QUIZ for Mr Circuit Electronics Training (“SCR - Silicon Control Rectifier”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#1</b> What are the three connections on an SCR?</p> <p>A. Input, Output, and Neutral</p> <p>B. Up, Down, Middle</p> <p>C. Right, Left, Straight</p> <p>D. Cathode, Anode, Gate</p>	<p><b>#6</b> The letters SCR in Exp. #7 stand for ‘Silicon Controlled Rectifier’. How many connection leads does an SCR have?</p> <p>A. 5</p> <p>B. 4</p> <p>C. 3</p> <p>D. 2</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#2</b> Once an SCR is turned on, in order to turn it off, you need to _____.</p> <p>A. remove the voltage on the Gate</p> <p>B. clap your hands</p> <p>C. remove the power from the entire circuit</p> <p>D. double the voltage</p>	<p><b>#7</b> If a positive voltage is applied to the Gate of an SCR, what happens in the circuit?</p> <p>A. the electrons flow through the SCR</p> <p>B. the SCR will turn off</p> <p>C. the resistance of the SCR increases</p> <p>D. absolutely nothing</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#3</b> Most of the electron current flowing through an SCR is flowing through the _____.</p> <p>A. Anode to Cathode circuit</p> <p>B. the Gate circuit</p> <p>C. Anode to Gate circuit</p> <p>D. Cathode to Anode circuit</p>	<p><b>#8</b> The Anode lead is connected internally to the _____ on the SCR.</p> <p>A. metal tab with a hole in it</p> <p>B. to the Gate lead</p> <p>C. to the Cathode lead</p> <p>D. to the round edge on the SCR</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#4</b> To turn on an SCR in a circuit, you need a _____.</p> <p>A. large current on the Gate</p> <p>B. small positive voltage on the Anode</p> <p>C. small positive voltage on the Gate</p> <p>D. large current on the Cathode</p>	<p><b>#9</b> If we reverse the polarity of the battery snap in the circuit, what will happen?</p> <p>A. it will not work</p> <p>B. it will work just fine</p> <p>C. the SCR will burn out</p> <p>D. the LED will self-destruct</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#5</b> The Gate lead on the SCR in this experiment is marked by the _____.</p> <p>A. metal tab on the SCR</p> <p>B. left lead on the SCR</p> <p>C. beveled edge on the SCR</p> <p>D. center lead on the SCR</p>	<p><b>#10</b> An SCR is considered to be a _____.</p> <p>A. a variable resistor</p> <p>B. a variable capacitor</p> <p>C. “a diode with a difference”</p> <p>D. a good potentiometer</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 08 QUIZ for Mr Circuit Electronics Training (“NPN Transistor”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#1</b> The NPN transistor we use in this experiment is referred to as a _____ transistor?</p> <p><b>A.</b> Bipolar</p> <p><b>B.</b> Dual</p> <p><b>C.</b> Double</p> <p><b>D.</b> integrated</p>	<p><b>#6</b> In this NPN transistor circuit, which LED should conduct the most electron current?</p> <p><b>A.</b> LED 1</p> <p><b>B.</b> LED 2</p> <p><b>C.</b> LED 3</p> <p><b>D.</b> LED 4</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#2</b> The schematic symbol of an NPN Transistor shows an arrow pointing to the _____ lead.</p> <p><b>A.</b> cathode</p> <p><b>B.</b> emitter</p> <p><b>C.</b> base</p> <p><b>D.</b> collector</p>	<p><b>#7</b> In this circuit, the Cathode of LED 2 is connected to the _____ of the NPN transistor.</p> <p><b>A.</b> Collector</p> <p><b>B.</b> Base</p> <p><b>C.</b> Emitter</p> <p><b>D.</b> Gate</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#3</b> The leads on an NPN transistor are called the Emitter, Base, and _____.</p> <p><b>A.</b> Collector</p> <p><b>B.</b> Cathode</p> <p><b>C.</b> Anode</p> <p><b>D.</b> Gate</p>	<p><b>#8</b> A transistor controls a large amount of current with _____.</p> <p><b>A.</b> a small amount of current</p> <p><b>B.</b> a large amount of current</p> <p><b>C.</b> a small amount of voltage</p> <p><b>D.</b> a huge amount of voltage</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#4</b> Most of the current traveling through an NPN transistor travels through the _____ circuit.</p> <p><b>A.</b> Emitter-Base</p> <p><b>B.</b> Emitter-Collector</p> <p><b>C.</b> Base-Base</p> <p><b>D.</b> Cathode-Anode</p>	<p><b>#9</b> An NPN transistor has three pins: a Collector, a Base, and _____.</p> <p><b>A.</b> an Anode</p> <p><b>B.</b> an Emitter</p> <p><b>C.</b> a Cathode</p> <p><b>D.</b> a Gate</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#5</b> In an NPN transistor, the direction of the electron flow is from _____.</p> <p><b>A.</b> Base to Emitter</p> <p><b>B.</b> Base to Base</p> <p><b>C.</b> Emitter to Emitter</p> <p><b>D.</b> Emitter to Collector</p>	<p><b>#10</b> The process of having a small current controlling a large current is called _____.</p> <p><b>A.</b> increase of the voltage</p> <p><b>B.</b> conservation of resources</p> <p><b>C.</b> reduction</p> <p><b>D.</b> amplification</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>

## QUICK-CHECK ANSWER KEY for Experiment 09 QUIZ for Mr Circuit Electronics Training (“PNP Transistor”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> In this circuit, the Emitter of the PNP is connected to the _____ of the battery.</p> <p>A. negative B. positive C. neutral D. ground</p>	<p><b>#6</b> The PNP transistor we use in this experiment is referred to as a _____ transistor?</p> <p>A. Bipolar B. Dual C. Double D. Integrated</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#2</b> In Exp. #9, we use LED brightnesses to compare the amount of _____ flowing.</p> <p>A. current B. voltage C. resistance D. air</p>	<p><b>#7</b> The schematic symbol of a PNP Transistor shows an arrow pointing to the _____ lead.</p> <p>A. Cathode B. Emitter C. Base D. Collector</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#3</b> In a PNP transistor circuit, which current is greater?</p> <p>A. the Collector to Emitter current B. the Base to Emitter current C. the Emitter to Collector current D. the Emitter to Base current</p>	<p><b>#8</b> A transistor controls a large amount of current with _____.</p> <p>A. a small amount of current B. a large amount of current C. a small amount of voltage D. a huge amount of voltage</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#4</b> In a transistor circuit, when there is no base current, there is _____.</p> <p>A. no voltage B. more collector current C. no collector current D. no anode voltage</p>	<p><b>#9</b> A PNP transistor has three pins: a Collector pin, a Base pin, and _____ pin.</p> <p>A. an Anode B. an Emitter C. a Cathode D. a Gate</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> In Exp. #9, the PNP transistor is working as _____.</p> <p>A. an amplifier B. a voltage regulator C. a resistor D. a variable capacitor</p>	<p><b>#10</b> In a PNP transistor, the direction of the electron flow is from _____.</p> <p>A. Base to Base B. Emitter to Collector C. Emitter to Base D. Collector to Emitter</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 10 QUIZ for Mr Circuit Electronics Training (“Two-Transistor Oscillator”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 This two-transistor oscillator uses an NPN transistor and \_\_\_\_\_ .

- B**  
**C**  
**D**
- A. an SCR
  - B. a PNP Transistor
  - C. a Diode
  - D. a Potentiometer

#6 In Exp. #10, how many transistors do we use to make an oscillator?

- A. 5
- B. 4
- C. 3
- D. 2

**A**  
**B**  
**C**  
**D**

**A** #2 In this two-transistor oscillator the Collector of transistor Q2 is connected to the Base of transistor Q1 through a \_\_\_\_\_ .

- B**  
**C**  
**D**
- A. capacitor
  - B. resistor
  - C. wire
  - D. speaker

#7 The circuit in Exp. #10 generates a tone by turning the \_\_\_\_\_ on and off at an audio frequency.

- A. capacitor
- B. speaker
- C. battery
- D. capacitance

**A**  
**B**  
**C**  
**D**

**A** #3 In this two-transistor oscillator circuit, the Emitter of Q1 3904 is connected to the Base of transistor Q2 through a \_\_\_\_\_?

- B**  
**C**  
**D**
- A. capacitor
  - B. resistor
  - C. wire
  - D. speaker

#8 Generally, an audio signal (one that can be heard by your ears) is in what frequency range?

- A. 1 million to 10 million (cycles per second)Hz
- B. 10 Hz to 16,000 Hz
- C. 100 thousand Hz to 100 megahertz
- D. zero to five Hz

**A**  
**B**  
**C**  
**D**

**A** 4 If we reverse the polarity of the battery snap on the circuit, what will happen?

- B**  
**C**  
**D**
- A. The circuit will not work.
  - B. It will work just fine.
  - C. The transistors will burn out.
  - D. The speaker will self-destruct.

#9 In electronics, one Hz (Hertz) means one change per \_\_\_\_\_ or one cycle per \_\_\_\_\_ .

- A. second, second
- B. minute, minute
- C. hour, hour
- D. day, day

**A**  
**B**  
**C**  
**D**

**A** #5 What happens if we increase the value of resistor R1 in the circuit?

- B**  
**C**  
**D**
- A. it will increase the frequency
  - B. it will make no change in frequency
  - C. it will cause the speaker to jam
  - D. it will lower the frequency

#10 What does the 10 Ohm resistor do in the circuit ?

- A. increase the current through the speaker
- B. vary the frequency of the oscillator
- C. reduce current through the speaker
- D. lower the frequency of the oscillator

**A**  
**B**  
**C**  
**D**



## QUICK-CHECK ANSWER KEY for Experiment 11 QUIZ for Mr Circuit Electronics Training (“555 Timer IC”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D	<b>#1</b> How many pins does a 555 Timer IC have?  <b>A.</b> 8 <b>B.</b> 3 <b>C.</b> 6 <b>D.</b> 12	<b>#6</b> What does the indentation or marking on the top end of the 555 Timer IC help you find?  <b>A.</b> Pin 5 <b>B.</b> Pin 4 <b>C.</b> Pin 1 <b>D.</b> the bottom of the IC	<input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D
<input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D	<b>#2</b> What pin is the output pin on the 555 Timer?  <b>A.</b> 8 <b>B.</b> 3 <b>C.</b> 6 <b>D.</b> 12	<b>#7</b> When a 555 Timer IC is working as a ‘clock’, it puts out pulses on _____.  <b>A.</b> Pin 8 <b>B.</b> Pin 2 <b>C.</b> Pin 5 <b>D.</b> Pin 3	<input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D
<input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D	<b>#3</b> If you connect an oscilloscope to the output Pin 3 on this circuit when operating, what might you see? <b>A.</b> pulses <b>B.</b> aliens <b>C.</b> resistance values <b>D.</b> inductance variations	<b>#8</b> When you are counting the pins on a 555 Timer IC, you count them _____.  <b>A.</b> up and down <b>B.</b> clockwise <b>C.</b> by tens <b>D.</b> counter-clockwise	<input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D
<input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D	<b>#4</b> What is the value of the capacitor in microfarads connected to Pin 2 of the 555 Timer IC in this circuit? <b>A.</b> 1000uF <b>B.</b> 10uF <b>C.</b> 33uF <b>D.</b> 470uF	<b>#9</b> When installing the 555 Timer IC on the solderless circuit board, you install it _____. <b>A.</b> always on the right end of the board <b>B.</b> with pin 1 in hole 1a <b>C.</b> across the center channel <b>D.</b> on the bottom of the board	<input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D
<input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D	<b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen? <b>A.</b> It will work just fine. <b>B.</b> You might destroy the 555 Timer IC. <b>C.</b> The LED will burn out. <b>D.</b> The LED will self-destruct.	<b>#10</b> When a 555 Timer IC is working as a ‘timer’, it puts out a voltage on _____ for a set period of time and then shuts off automatically. <b>A.</b> Pin 3 <b>B.</b> Pin 5 <b>C.</b> Pin 8 <b>D.</b> Pin 2	<input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D

## QUICK-CHECK ANSWER KEY for Experiment 12 QUIZ for Mr Circuit Electronics Training (“Burglar Alarm”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#1</b> How do you turn off this alarm once it is tripped?</p> <p>A. touch a negative voltage to the Gate</p> <p>B. open the normally-open switch</p> <p>C. remove power from the circuit</p> <p>D. close the normally-closed switch</p>	<p><b>#6</b> When the 33 Ohm resistor is connected to the Gate, what happens?</p> <p>A. the alarm is turned off</p> <p>B. the alarm is triggered</p> <p>C. the alarm is reset</p> <p>D. nothing</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#2</b> What item in this alarm circuit indicates that the alarm has been tripped?</p> <p>A. the LED</p> <p>B. the Diode</p> <p>C. the SCR</p> <p>D. the resistor</p>	<p><b>#7</b> The cathode of the LED is connected to what pin on the SCR?</p> <p>A. the Gate</p> <p>B. the Cathode</p> <p>C. the Emitter</p> <p>D. the Anode</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#3</b> Which component limits the current flowing through the LED?</p> <p>A. the SCR</p> <p>B. the 220 ohm resistor</p> <p>C. the Diode</p> <p>D. the 0.1 disc capacitor</p>	<p><b>#8</b> How many pins are there on an SCR.</p> <p>A. 1</p> <p>B. 2</p> <p>C. 3</p> <p>D. 4</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#4</b> To trigger the alarm, which lead on the SCR has to receive a small positive voltage?</p> <p>A. EMITTER</p> <p>B. CATHODE</p> <p>C. ANODE</p> <p>D. GATE</p>	<p><b>#9</b> In this circuit, there are how many switches to trigger the alarm circuit?</p> <p>A. 1</p> <p>B. 2</p> <p>C. 3</p> <p>D. 5</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> Where would you connect a buzzer to this alarm circuit?</p> <p>A. across R3 and the LED</p> <p>B. across R1 and S1</p> <p>C. across R2 and D1</p> <p>D. across the SCR</p>	<p><b>#10</b> How many capacitors do we use in this circuit?</p> <p>A. 3</p> <p>B. 2</p> <p>C. 1</p> <p>D. 4</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 13 QUIZ for Mr Circuit Electronics Training (“Automatic Night Light”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> This Automatic Night Light will turn on automatically _____?</p> <p>A. when there is light.</p> <p>B. when there is darkness.</p> <p>C. at noon each day.</p> <p>D. when it is humid outside.</p>	<p><b>#6</b> The LEDs receive their current from which pin on the NPN transistor?</p> <p>A. the Collector</p> <p>B. the Emitter</p> <p>C. the Base</p> <p>D. the Gate</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#2</b> How many LEDs are there in this circuit?</p> <p>A. 1</p> <p>B. 3</p> <p>C. 2</p> <p>D. 5</p>	<p><b>#7</b> Resistor R2, 16k Ohms, is connected directly to which terminal on the 9-Volt battery?</p> <p>A. the negative</p> <p>B. the center</p> <p>C. the neutral</p> <p>D. the positive</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#3</b> What is the purpose of the 47 Ohm resistor in the circuit?</p> <p>A. to increase the current in the circuit</p> <p>B. to serve as a fuse for the circuit</p> <p>C. to increase the brightness of the LEDs</p> <p>D. limit the current through the LEDs</p>	<p><b>#8</b> The potentiometer has 3 connections. How many do we use in this circuit? .</p> <p>A. 0</p> <p>B. 2</p> <p>C. 3</p> <p>D. 1</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#4</b> What is the purpose of the Potentiometer in the circuit?</p> <p>A. to make the LEDs blink</p> <p>B. to adjust the sensitivity of the Photocell</p> <p>C. to adjust the loudness</p> <p>D. to make the battery last longer</p>	<p><b>#9</b> What are the colors on Resistor R1, 47 Ohms?</p> <p>A. yellow, violet, black, gold</p> <p>B. brown, red, black, gold</p> <p>C. green, green, brown, gold</p> <p>D. gray, blue, brown, gold</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p>A. It will work just fine.</p> <p>B. The LEDs will not light up.</p> <p>C. The LEDs will burn out.</p> <p>D. The LEDs will self-destruct.</p>	<p><b>#10</b> This circuit is used to turn on the LEDs _____.</p> <p>A. when the weather is hot</p> <p>B. during the day</p> <p>C. at night</p> <p>D. when it is a humid day</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 14 QUIZ for Mr Circuit Electronics Training (“DC to DC Power Supply”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A B C D</p>	<p><b>#1</b> This circuit has an input of a fixed DC voltage and an output of _____? <b>A.</b> a variable DC voltage <b>B.</b> an AC voltage <b>C.</b> a voltage higher than the input voltage <b>D.</b> a voltage from -5V to 5V</p>	<p><b>#6</b> The voltage applied to the base of the transistor controls the _____ of the transistor. <b>A.</b> external capacitance <b>B.</b> internal resistance <b>C.</b> external resistance <b>D.</b> internal capacitance</p>	<p>A B C D</p>
<p>A B C D</p>	<p><b>#2</b> What is the maximum current that can be provided by this DC to DC Power Supply? <b>A.</b> 10 milliamps <b>B.</b> 3 Amps <b>C.</b> 50 milliamps <b>D.</b> 1 Amp</p>	<p><b>#7</b> The potentiometer controls the voltage applied to the _____ of the transistor. <b>A.</b> Collector <b>B.</b> Emitter <b>C.</b> Anode <b>D.</b> Base</p>	<p>A B C D</p>
<p>A B C D</p>	<p><b>#3</b> You can use this power supply to supply voltage for _____. <b>A.</b> portable transistor radios <b>B.</b> large HAM radios <b>C.</b> large Televisions and Stereos <b>D.</b> microwave ovens</p>	<p><b>#8</b> The output of this DC to DC Power Supply will be a maximum when the _____ of the transistor is close to 0 volts. <b>A.</b> current applied to the Collector <b>B.</b> voltage applied to the Base <b>C.</b> voltage applied to the Emitter <b>D.</b> current applied to the Base</p>	<p>A B C D</p>
<p>A B C D</p>	<p><b>#4</b> In this circuit, transistor Q1 is used as _____? <b>A.</b> a capacitor <b>B.</b> an inductor <b>C.</b> a fixed capacitance <b>D.</b> an adjustable resistor</p>	<p><b>#9</b> When the _____ of transistor Q1 is high, the output voltage will be at minimum. <b>A.</b> external capacitance <b>B.</b> internal capacitance <b>C.</b> external resistance <b>D.</b> internal resistance</p>	<p>A B C D</p>
<p>A B C D</p>	<p><b>#5</b> In this circuit, the potentiometer is used to _____. <b>A.</b> vary the output voltage <b>B.</b> adjust the capacitance <b>C.</b> as a variable inductor <b>D.</b> keep the LED from burning out</p>	<p><b>#10</b> In this circuit, the brightness of the LED is an indicator of the _____. <b>A.</b> output voltage <b>B.</b> input voltage <b>C.</b> input current <b>D.</b> output capacitance</p>	<p>A B C D</p>

## QUICK-CHECK ANSWER KEY for Experiment 15 QUIZ for Mr Circuit Electronics Training (“Electronic Metronome”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> This metronome circuit is built using _____.</p> <p>A. a 555 Timer IC B. a two-transistor oscillator C. an SCR D. a quad amplifier</p>	<p><b>#6</b> In this circuit, the speaker is connected to the _____ of transistor Q2.</p> <p>A. Base B. Anode C. Collector D. Emitter</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> The potentiometer is used to adjust the _____.</p> <p>A. the current through the speaker B. the capacitance of the transistors C. the loudness of the speaker D. speed of the oscillation</p>	<p><b>#7</b> Transistor Q1 in this circuit is _____.</p> <p>A. a PNP Transistor B. an NPN Transistor C. a variable diode D. a capacitance</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#3</b> The Emitter of transistor Q1 is connected to the _____ of transistor Q2.</p> <p>A. Collector B. Anode C. Emitter D. Base</p>	<p><b>#8</b> Based on your understanding of a two-transistor oscillator circuit, the purpose of Capacitor C1 is to _____.</p> <p>A. reduce the current in the circuit B. help control the speed of the oscillator C. reduce the resistance of the circuit. D. reduce the voltage used in the circuit</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#4</b> The potentiometer varies the _____ on the Base of transistor Q1.</p> <p>A. voltage B. capacitance C. resistance D. current</p>	<p><b>#9</b> The _____ of Q2 is connected directly to the positive of the battery.</p> <p>A. Emitter B. Collector C. Base D. Anode</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> As you adjust the potentiometer from 0 Ohms to its maximum Ohms, the oscillator will _____ in speed.</p> <p>A. decrease B. increase C. remain the same D. not be affected</p>	<p><b>#10</b> The positive lead on Capacitor C1 is connected to the _____ of transistor Q1.</p> <p>A. Collector B. Anode C. Emitter D. Base</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 16 QUIZ for Mr Circuit Electronics Training (“Electronic Motorcycle”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> This motorcycle circuit is built using _____.</p> <p>A. a 555 Timer IC B. a two-transistor oscillator C. an SCR D. a quad amplifier</p>	<p><b>#6</b> In this circuit, the speaker is connected to the _____ of transistor Q2.</p> <p>A. Base B. Anode C. Collector D. Emitter</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> The potentiometer is used to adjust the _____.</p> <p>A. the current through the speaker B. the capacitance of the transistors C. the loudness of the speaker D. speed of the oscillation</p>	<p><b>#7</b> Transistor Q2 in this circuit is _____.</p> <p>A. a PNP Transistor B. an NPN Transistor C. a variable diode D. is a capacitance</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#3</b> The Emitter of transistor Q1 is connected to the _____ of transistor Q2.</p> <p>A. Collector B. Anode C. Emitter D. Base</p>	<p><b>#8</b> Based on your understanding of a two-transistor oscillator circuit, the purpose of Capacitor C1 is to _____.</p> <p>A. reduce the current in the circuit B. help control the speed of the oscillator C. reduce the resistance of the circuit. D. reduce the voltage used in the circuit</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#4</b> The potentiometer varies the _____ on the Base of transistor Q1.</p> <p>A. voltage B. capacitance C. resistance D. current</p>	<p><b>#9</b> The _____ of Q2 is connected through a 10 Ohm resistor to the positive of the battery.</p> <p>A. Emitter B. Collector C. Base D. Anode</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> As you adjust the potentiometer from 0 Ohms to its maximum Ohms, the oscillator will _____ in speed.</p> <p>A. decrease B. increase C. remain the same D. not be affected</p>	<p><b>#10</b> The positive lead on Capacitor C1 is connected to the _____ of transistor Q1 and to the potentiometer.</p> <p>A. Collector B. Anode C. Emitter D. Base</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 17 QUIZ for Mr Circuit Electronics Training (“Railroad Lights”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#1</b> This circuit uses _____ working as a clock?</p> <p>A. an NPN Transistor B. a 555 Timer IC C. a PNP Transistor D. a Potentiometer</p>	<p><b>#6</b> The speed if the blinking LEDs is _____.</p> <p>A. variable B. super fast C. fixed D. super slow</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> When pin 3 on the 555 Timer is positive, _____ will be forward biased.</p> <p>A. LED 1 B. Resistor R1 C. Resistor R3 D. LED 2</p>	<p><b>#7</b> When this circuit is working, the LEDs will _____ ?</p> <p>A. blink on and off alternately B. remain off permanently C. remain on D. get hot and self-destruct</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#3</b> The two LEDs in this circuit are installed in _____ polarity.</p> <p>A. the same B. amplifying C. opposite D. dual</p>	<p><b>#8</b> When an LED is _____ it means that the Anode is positive and the Cathode is negative.</p> <p>A. reverse-biased B. forward-biased C. will not turn on D. will change from Red to Green</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?</p> <p>A. 1000uF B. 10uF C. 33uF D. 470uF</p>	<p><b>#9</b> When an LED is _____ it means that the Anode is negative and the Cathode is positive.</p> <p>A. reverse-biased B. forward-biased C. will not turn on D. will change from Red to Green</p>	<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p>A. it will work just fine B. you might destroy the 555 Timer IC C. the LED will burn out D. the LED will self-destruct</p>	<p><b>#10</b> When an LED is forward biased, it will _____.</p> <p>A. self-destruct B. turn on C. get hot D. turn off</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 18 QUIZ for Mr Circuit Electronics Training (“Variable Speed Lights”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



A **#1** This circuit uses \_\_\_\_\_  
working as a clock?

- B  
C  **A.** an NPN Transistor  
**B.** a PNP Transistor  
**C.** a 555 Timer IC  
**D.** a Potentiometer

**#6** LED 1 is connect to pin 3 of the 555 Timer IC  
through \_\_\_\_\_ .

- A.** a 220 Ohm resistor  
**B.** a 10uF capacitor  
**C.** a 6.8k Ohm resistor  
**D.** a 1k Ohm resistor

A

B

C

D

A **#2** You can adjust the speed of the blinking  
lights by using \_\_\_\_\_ .

- B  
C  **A.** the Diode  
**B.** the LED  
**C.** the Potentiometer  
**D.** transistor

**#7** When this circuit is working, the LEDs will  
\_\_\_\_\_ ?

- A.** remain on  
**B.** remain off permanently  
**C.** blink on and off alternately  
**D.** get hot and self-destruct

A

B

C

D

A **#3** The two LEDs in this circuit are installed in  
\_\_\_\_\_ polarity.

- B  
C  
D  **A.** the same  
**B.** amplifying  
**C.** dual  
**D.** opposite

**#8** When an LED is \_\_\_\_\_ it  
means that the Anode is positive and the  
Cathode is negative.

- A.** reverse-biased  
**B.** will not turn on  
**C.** forward biased  
**D.** will change from Red to Green

A

B

C

D

A **#4** What is the value of the capacitor connected  
to Pin 2 of the 555 Timer IC in this circuit?

- B  
C  
D  **A.** 1000uF  
**B.** 330uF  
**C.** 33uF  
**D.** 10uF

**#9** When an LED is \_\_\_\_\_ it  
means that the Anode is negative and the  
Cathode is positive.

- A.** will change from Red to Green  
**B.** forward-biased  
**C.** will not turn on  
**D.** reverse-biased

A

B

C

D

A **#5** If we reverse the polarity of the battery snap  
on the circuit, what will happen?

- B  
C  **A.** it will work just fine  
**B.** the LED will burn out  
**C.** you might destroy the 555 Timer IC  
**D.** the LED will self-destruct

**#10** A Potentiometer is also known as  
\_\_\_\_\_ .

- A.** variable transistor  
**B.** fixed capacitor  
**C.** a variable resistor  
**D.** fixed resistor

A

B

C

D



## QUICK-CHECK ANSWER KEY for Experiment 19 QUIZ for Mr Circuit Electronics Training (“Continuity Tester”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 This circuit uses 555 Timer IC working as a \_\_\_\_\_.

- B**
- C**
- D**
- A.** an amplifier
  - B.** a timer
  - C.** a clock
  - D.** a light generator

**#6** Resistor R3 is connected to \_\_\_\_\_ of the 555 Timer IC.

- A.** Pin 3
- B.** Pin 4
- C.** Pin 1
- D.** Pin 6

**A**

**B**

**C**

**D**

**A** #2 The loudness of the tone is \_\_\_\_\_.

- B**
- C**
- D**
- A.** adjustable
  - B.** fixed
  - C.** controlled by Resistor R1
  - D.** controlled by Capacitor C1

**#7** When this circuit is working, the speaker will \_\_\_\_\_ when there is continuity.

- A.** remain silent
- B.** self-destruct
- C.** emit a tone
- D.** get hot

**A**

**B**

**C**

**D**

**A** #3 The speaker in this circuit is connected to the \_\_\_\_\_ of transistor Q1.

- B**
- C**
- D**
- A.** Gate
  - B.** Emitter
  - C.** Collector
  - D.** Base

**#8** When you touch the two probes together, the speaker will \_\_\_\_\_.

- A.** remain silent
- B.** self-destruct
- C.** get hot
- D.** emit a tone

**A**

**B**

**C**

**D**

**A** #4 What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?

- B**
- C**
- D**
- A.** 0.01uF
  - B.** 330uF
  - C.** 33uF
  - D.** 10uF

**#9** One probe is connected to R1 and the other one is connected \_\_\_\_\_.

- A.** to the negative of the battery
- B.** to the speaker
- C.** to the 0.01uF capacitor
- D.** to the positive of the battery

**A**

**B**

**C**

**D**

**A** #5 If we reverse the polarity of the battery snap on the circuit, what will happen?

- B**
- C**
- D**
- A.** you might destroy the 555 Timer IC
  - B.** the LED will burn out
  - C.** it will work just fine
  - D.** the LED will self-destruct

**#10** This circuit emits \_\_\_\_\_ signal.

- A.** an inaudible
- B.** an rf
- C.** an ultrasonic
- D.** an audio

**A**

**B**

**C**

**D**

## QUICK-CHECK ANSWER KEY for Experiment 20 QUIZ for Mr Circuit Electronics Training (“Audio Generator”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> This circuit uses 555 Timer IC working as a _____.</p> <p><b>A.</b> a clock</p> <p><b>B.</b> a timer</p> <p><b>C.</b> an amplifier</p> <p><b>D.</b> a light generator</p>	<p><b>#6</b> Resistor R2 is connect to _____ of the 555 Timer IC.</p> <p><b>A.</b> Pin 3</p> <p><b>B.</b> Pin 4</p> <p><b>C.</b> Pin 7</p> <p><b>D.</b> Pin 6</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#2</b> The loudness of the tone is _____.</p> <p><b>A.</b> adjustable</p> <p><b>B.</b> controlled by Resistor R1</p> <p><b>C.</b> fixed</p> <p><b>D.</b> controlled by Capacitor C1</p>	<p><b>#7</b> When this circuit is working, the speaker will _____.</p> <p><b>A.</b> remain silent</p> <p><b>B.</b> self-destruct</p> <p><b>C.</b> emit a variable audiotone</p> <p><b>D.</b> get hot</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> The speaker in this circuit is connected to the _____ of transistor Q1.</p> <p><b>A.</b> Collector</p> <p><b>B.</b> Emitter</p> <p><b>C.</b> Gate</p> <p><b>D.</b> Base</p>	<p><b>#8</b> To vary the frequency of this oscillator, you adjust _____.</p> <p><b>A.</b> the potentiometer</p> <p><b>B.</b> the transistor</p> <p><b>C.</b> 555 Timer IC</p> <p><b>D.</b> battery snap</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?</p> <p><b>A.</b> 10uF</p> <p><b>B.</b> 330uF</p> <p><b>C.</b> 33uF</p> <p><b>D.</b> 0.01uF</p>	<p><b>#9</b> Pins 4 and 8 on the 555 Timer IC are _____.</p> <p><b>A.</b> connected together</p> <p><b>B.</b> are insulated from each other</p> <p><b>C.</b> do not need to be connected</p> <p><b>D.</b> are not important in this circuit</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p><b>A.</b> the LED will self-destruct</p> <p><b>B.</b> the LED will burn out</p> <p><b>C.</b> it will work just fine</p> <p><b>D.</b> you might destroy the 555 Timer IC</p>	<p><b>#10</b> The word ‘tone’ is the same thing as _____.</p> <p><b>A.</b> loudness</p> <p><b>B.</b> pitch</p> <p><b>C.</b> excitation</p> <p><b>D.</b> bias</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 21 QUIZ for Mr Circuit Electronics Training (“Electronic Police Siren”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#1</b> This circuit uses 555 Timer IC working as a _____.</p> <p>A. a light generator</p> <p>B. a timer</p> <p>C. an amplifier</p> <p>D. clock</p>	<p><b>#6</b> Resistors R5 and R6 are _____.</p> <p>A. not connected</p> <p>B. connected</p> <p>C. not important</p> <p>D. are connected to pin 7</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> The loudness of the tone is _____.</p> <p>A. adjustable</p> <p>B. controlled by Resistor R1</p> <p>C. controlled by Capacitor C1</p> <p>D. fixed</p>	<p><b>#7</b> When this circuit is working, the speaker will _____.</p> <p>A. remain silent</p> <p>B. self-destruct</p> <p>C. emit a variable audiotone</p> <p>D. get hot</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#3</b> The speaker in this circuit is connected to the _____ of transistor Q1.</p> <p>A. Base</p> <p>B. Emitter</p> <p>C. Gate</p> <p>D. Collector</p>	<p><b>#8</b> To vary the frequency of this oscillator, you _____.</p> <p>A. adjust the potentiometer</p> <p>B. use the pushbutton switch</p> <p>C. use the battery snap</p> <p>D. remove resistor R1</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 6 of the 555 Timer IC in this circuit?</p> <p>A. 10uF</p> <p>B. 330uF</p> <p>C. 33uF</p> <p>D. 0.01uF</p>	<p><b>#9</b> The rising and falling of the frequency of the oscillator is controlled by _____.</p> <p>A. the distance C2 is from the battery</p> <p>B. charging and discharging of C2</p> <p>C. charging and discharging of C1</p> <p>D. the size of the speaker</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p>A. the LED will self-destruct</p> <p>B. the LED will burn out</p> <p>C. you might destroy the 555 Timer IC</p> <p>D. it will work just fine</p>	<p><b>#10</b> Switch S1 is in series with _____.</p> <p>A. C1 and C2</p> <p>B. R1 and R2</p> <p>C. R5 and R6</p> <p>D. R3 and R4</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 22 QUIZ for Mr Circuit Electronics Training (“Wake-Up Alarm”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A B C <b>D</b></p>	<p><b>#1</b> This circuit uses a _____ to sense light intensity?</p> <p>A. an SCR B. a 555 Timer IC C. a transistor D. a Photocell</p>	<p><b>#6</b> Pins 4 and 8 of the 555 Timer IC are _____.</p> <p>A. connected B. are not connected C. are isolated from each other D. are not important</p>	<p><b>A</b> B C D</p>
<p>A <b>B</b> C D</p>	<p><b>#2</b> What pin on the 555 Timer is connected to a 220 Ohm resistor?</p> <p>A. 8 B. 3 C. 6 D. 12</p>	<p><b>#7</b> When the Photocell receives a lot of light, the alarm will _____.</p> <p>A. go silent B. make noise C. burn up D. give off moisture</p>	<p>A <b>B</b> C D</p>
<p>A B C <b>D</b></p>	<p><b>#3</b> With this circuit, you can generate a variety of interesting _____ by shadowing the surface of the Photocell with your hand.</p> <p>A. weather conditions B. electronic displays C. light displays D. sound effects</p>	<p><b>#8</b> To increase the amplitude of the pulses coming from the output Pin 3 of the 555 Timer IC we use _____.</p> <p>A. an SCR B. a PNP transistor C. an NPN Transistor D. variable capacitor</p>	<p>A B <b>C</b> D</p>
<p>A B <b>C</b> D</p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 2 and Pin 6 of the 555 Timer IC in this circuit?</p> <p>A. 0.01uF B. 10uF C. 0.1uF D. 470uF</p>	<p><b>#9</b> The Photocell is connected to Pins 7, 6, and _____.</p> <p>A. 8 B. 4 C. 1 D. 2</p>	<p>A B C <b>D</b></p>
<p><b>A</b> B C D</p>	<p><b>#5</b> How many pins on the 555 Timer IC do we use in this circuit?</p> <p>A. 7 B. 3 C. 8 D. 1</p>	<p><b>#10</b> Pin 1 of the 555 Timer IC is connected to the negative of the battery, to Pin 1 and _____.</p> <p>A. the Emitter of the NPN Transistor B. the Collector of the PNP Transistor C. the 100 Ohm resistor D. the speaker</p>	<p><b>A</b> B C D</p>

## QUICK-CHECK ANSWER KEY for Experiment 23 QUIZ for Mr Circuit Electronics Training (“Variable Timer”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 This circuit uses a 555 Timer IC as a \_\_\_\_\_ .

- B**  
**C**  
**D**
- A.** a clock
  - B.** variable capacitor
  - C.** a timer
  - D.** variable resistor

**#6** If you want the LED to stay on longer, what would you do?

- A.** replace C1 with 1000uF
- B.** remove C1 from the circuit
- C.** reduce the capacitance of C1
- D.** short C1

**A**

**B**

**C**

**D**

**A** #2 What pin on the 555 Timer is connected to an LED?

- B**  
**C**  
**D**
- A.** 8
  - B.** 3
  - C.** 6
  - D.** 12

**#7** The positive of C1 is connected to \_\_\_\_\_ .

- A.** Pin 4
- B.** Pin 2
- C.** Pin 6
- D.** Pin 8

**A**

**B**

**C**

**D**

**A** #3 All the pins on the 555 Timer IC are used in this circuit except \_\_\_\_\_ .

- B**  
**C**  
**D**
- A.** Pin 5
  - B.** Pin 1
  - C.** Pin 8
  - D.** Pin 4

**#8** To ‘trigger’ the timer to start, you \_\_\_\_\_ .

- A.** apply a positive voltage to Pin 1
- B.** remove the voltage from Pin 3
- C.** increase the voltage on Pin 8
- D.** apply a negative voltage to Pin 2

**A**

**B**

**C**

**D**

**A** #4 The Switch S1 is connected to Pin 2 and to \_\_\_\_\_ .

- B**  
**C**  
**D**
- A.** Pin 4
  - B.** Pin 6
  - C.** Pin 1
  - D.** Pin 3

**#9** The Potentiometer is connected to \_\_\_\_\_ .

- A.** Pins 7 and 8
- B.** Pins 6 and 7
- C.** Pins 4 and 5
- D.** Pins 3 and 4

**A**

**B**

**C**

**D**

**A** #5 What is the purpose of the Potentiometer in this circuit?

- B**  
**C**  
**D**
- A.** to vary how long the LED is ON
  - B.** to vary the volume of the sound
  - C.** to count the pulses
  - D.** to vary the brightness of the LED

**#10** The amount of time the LED remains on after the timer is ‘triggered’ depends on the values of R2, R4, and \_\_\_\_\_ .

- A.** R3
- B.** C1
- C.** R1
- D.** the LED

**A**

**B**

**C**

**D**

## QUICK-CHECK ANSWER KEY for Experiment 24 QUIZ for Mr Circuit Electronics Training (“Moisture Detector”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> This circuit uses a 555 Timer IC as a _____ .</p> <p><b>A.</b> a clock</p> <p><b>B.</b> variable capacitor</p> <p><b>C.</b> a timer</p> <p><b>D.</b> variable resistor</p>	<p><b>#6</b> The more moisture in the soil, the _____ .</p> <p><b>A.</b> the slower the blinks of the LED</p> <p><b>B.</b> the hotter the LED gets</p> <p><b>C.</b> the faster the blinks of the LED</p> <p><b>D.</b> the higher the input voltage</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#2</b> What is connected to pin 3 on the 555 Timer IC?</p> <p><b>A.</b> an LED</p> <p><b>B.</b> a 220 Ohm resistor</p> <p><b>C.</b> a 10uF capacitor</p> <p><b>D.</b> a Photocell</p>	<p><b>#7</b> Pin 1 of the 555 Timer IC is connected is connected to _____ .</p> <p><b>A.</b> the negative of the battery.</p> <p><b>B.</b> Pin 5</p> <p><b>C.</b> the positive of the battery</p> <p><b>D.</b> the positive of C1</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> On the 555 Timer _____ .</p> <p><b>A.</b> only 6 pins are used</p> <p><b>B.</b> all but pin 5 are used</p> <p><b>C.</b> all 8 pins are used</p> <p><b>D.</b> all but pin 4 are used</p>	<p><b>#8</b> To make sure the circuit is working, you _____ .</p> <p><b>A.</b> touch the probes together</p> <p><b>B.</b> short capacitor C1</p> <p><b>C.</b> remove the LED</p> <p><b>D.</b> disconnect the battery</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#4</b> The purpose of this circuit is to _____ in soil.</p> <p><b>A.</b> sense moisture</p> <p><b>B.</b> sense vibrations</p> <p><b>C.</b> sense heat</p> <p><b>D.</b> sense light</p>	<p><b>#9</b> Pins 6 and 2 are _____ .</p> <p><b>A.</b> not connected</p> <p><b>B.</b> connected</p> <p><b>C.</b> not important</p> <p><b>D.</b> determine the brightness of the LED.</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#5</b> What controls the frequency of the output tone?</p> <p><b>A.</b> humidity in the air</p> <p><b>B.</b> the air temperature</p> <p><b>C.</b> resistance between the probes</p> <p><b>D.</b> the brightness of the sun</p>	<p><b>#10</b> If the soil is dry, the LED will _____ .</p> <p><b>A.</b> blink</p> <p><b>B.</b> remain either ON or OFF</p> <p><b>C.</b> get hot</p> <p><b>D.</b> the LED will self-destruct</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>

## QUICK-CHECK ANSWER KEY for Experiment 25 QUIZ for Mr Circuit Electronics Training (“Code Oscillator”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>	<p><b>#1</b> This circuit uses a 555 Timer IC as _____.</p> <p>A. a variable resistor</p> <p>B. a variable capacitor</p> <p>C. a timer</p> <p>D. a clock</p>	<p><b>#6</b> The loudness of the emitted tone _____.</p> <p>A. is fixed</p> <p>B. is adjustable by the value of R1</p> <p>C. is adjustable by the value of C1</p> <p>D. is controlled by S1</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>	<p><b>#2</b> R3 is connected to pin 3 on the 555 Timer IC and to the _____ on Q1.</p> <p>A. Emitter</p> <p>B. Base</p> <p>C. Collector</p> <p>D. Anode</p>	<p><b>#7</b> If you do not press the pushbutton switch, the circuit _____.</p> <p>A. will consume power</p> <p>B. will cause the speaker to emit a tone</p> <p>C. will apply voltage to the 555 Timer IC</p> <p>D. will not consume power</p>	<p>A</p> <p>B</p> <p>C</p> <p><b>D</b></p>
<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>	<p><b>#3</b> On the 555 Timer _____.</p> <p>A. only 6 pins are used</p> <p>B. all but pin 5 are used</p> <p>C. all 8 pins are used</p> <p>D. all but pin 4 are used</p>	<p><b>#8</b> To make sure the circuit is working, you _____.</p> <p>A. press the pushbutton switch to make a tone</p> <p>B. short capacitor C1</p> <p>C. remove the LED</p> <p>D. disconnect the battery</p>	<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>	<p><b>#4</b> The purpose of this circuit is to _____ as you press the pushbutton switch.</p> <p>A. sense moisture</p> <p>B. sense vibrations</p> <p>C. emit an audio tone</p> <p>D. sense light</p>	<p><b>#9</b> Pins 4 and 8 are _____.</p> <p>A. not connected</p> <p>B. connected</p> <p>C. not important</p> <p>D. determine the brightness of the LED.</p>	<p>A</p> <p><b>B</b></p> <p>C</p> <p>D</p>
<p><b>A</b></p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> How do you send Morse Code with this oscillator circuit?</p> <p>A. you press the pushbutton switch</p> <p>B. you squeeze resistor R1</p> <p>C. you remove the 10 Ohm resistor</p> <p>D. you adjust the speaker</p>	<p><b>#10</b> What controls the speed at which you send code with this oscillator?</p> <p>A. the battery</p> <p>B. the speaker</p> <p>C. you do.</p> <p>D. the transistor</p>	<p>A</p> <p>B</p> <p><b>C</b></p> <p>D</p>

## QUICK-CHECK ANSWER KEY for Experiment 26 QUIZ for Mr Circuit Electronics Training (“Audible Water Detector”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 This circuit uses a 555 Timer IC as

- B** \_\_\_\_\_ .
- A.** a variable resistor
  - B.** a variable capacitor
  - C.** a clock
  - D.** a timer

**#6** The loudness of the emitted tone

- \_\_\_\_\_ .
- A.** is fixed
  - B.** is adjustable by the value of R1
  - C.** is adjustable by the value of C1
  - D.** is controlled by S1

**A** #2 R4 is connected to \_\_\_\_\_ and

- B** to the positive of the battery.
- A.** the speaker
  - B.** the transistor
  - C.** the 555 Timer IC
  - D.** the capacitor C1

**#7** Resistors R1 and R2 \_\_\_\_\_ .

- A.** are connected
- B.** are not connected
- C.** are not important in the circuit
- D.** control the loudness of the speaker

**A** #3 On the 555 Timer \_\_\_\_\_ .

- B**
- A.** only 6 pins are used
  - B.** all but pin 4 are used
  - C.** all 8 pins are used
  - D.** all but pin 5 are used

**#8** To make sure the circuit is working, you

- \_\_\_\_\_ .
- A.** remove resistor R4
  - B.** short capacitor C1
  - C.** put the probes into water
  - D.** disconnect the battery

**A** #4 The purpose of this circuit is to

- B** \_\_\_\_\_ .
- A.** sense the presence of water
  - B.** sense vibrations
  - C.** sense heat
  - D.** sense light

**#9** Pins 1 and 3 of the 555 Timer IC are

- \_\_\_\_\_ .
- A.** not connected
  - B.** connected
  - C.** not important
  - D.** determine the loudness of the speaker

**A** #5 What happens when this circuit is triggered?

- B**
- A.** you hear a tone in the speaker
  - B.** you hear a loud cracking sound
  - C.** an LED starts blinking
  - D.** the capacitor gets hot

**#10** Capacitor C1 is connected to Pin 1 and to

- \_\_\_\_\_ .
- A.** Pin 8
  - B.** Pin 7
  - C.** Pin 4
  - D.** the Emitter of transistor Q1



## QUICK-CHECK ANSWER KEY for Experiment 27 QUIZ for Mr Circuit Electronics Training (“English Police Siren”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#1</b> This circuit uses a 555 Timer IC as _____.</p> <p><b>A.</b> a clock</p> <p><b>B.</b> a variable capacitor</p> <p><b>C.</b> a variable resistor</p> <p><b>D.</b> a timer</p>	<p><b>#6</b> The loudness of the emitted tone _____.</p> <p><b>A.</b> is controlled by S1</p> <p><b>B.</b> is adjustable by the value of R1</p> <p><b>C.</b> is adjustable by the value of C1</p> <p><b>D.</b> is fixed</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#2</b> R5 is connected to R1, R2 , Switch S1 and to _____.</p> <p><b>A.</b> Pin 7</p> <p><b>B.</b> the transistor</p> <p><b>C.</b> the speaker</p> <p><b>D.</b> capacitor C1</p>	<p><b>#7</b> Resistors R1, R2 and R5 _____.</p> <p><b>A.</b> are not connected</p> <p><b>B.</b> control the loudness of the speaker</p> <p><b>C.</b> are not important in the circuit</p> <p><b>D.</b> are connected</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#3</b> On the 555 Timer _____.</p> <p><b>A.</b> all but pin 5 are used</p> <p><b>B.</b> all but pin 4 are used</p> <p><b>C.</b> all 8 pins are used</p> <p><b>D.</b> only 6 pins are used</p>	<p><b>#8</b> When this circuit is working correctly, as soon as you _____ it will emit a tone.</p> <p><b>A.</b> press the switch S1</p> <p><b>B.</b> connect the battery</p> <p><b>C.</b> remove the 555 Timer IC</p> <p><b>D.</b> install capacitor C1</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#4</b> The purpose of this circuit is to _____.</p> <p><b>A.</b> emit a siren sound</p> <p><b>B.</b> emit bird chirps</p> <p><b>C.</b> sense heat</p> <p><b>D.</b> sense light</p>	<p><b>#9</b> Pressing Switch S1 puts _____ in parallel.</p> <p><b>A.</b> R1 and R2</p> <p><b>B.</b> R2 and R3</p> <p><b>C.</b> R5 and R2</p> <p><b>D.</b> R4 and R5</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>
<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>	<p><b>#5</b> How do you make the circuit emit two tones?</p> <p><b>A.</b> connect and disconnect the battery</p> <p><b>B.</b> remove and replace the 10 Ohm resistor</p> <p><b>C.</b> press and release the pushbutton switch</p> <p><b>D.</b> squeeze capacitor C1</p>	<p><b>#10</b> In order to shut off this circuit, you must _____.</p> <p><b>A.</b> disconnect the battery</p> <p><b>B.</b> hold down the pushbutton switch</p> <p><b>C.</b> hold your ears</p> <p><b>D.</b> change capacitor C1 to a different value</p>	<p><b>A</b></p> <p><b>B</b></p> <p><b>C</b></p> <p><b>D</b></p>

## QUICK-CHECK ANSWER KEY for Experiment 28 QUIZ for Mr Circuit Electronics Training (“Electronic Canary”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



A #1 This circuit uses a 555 Timer IC and \_\_\_\_\_ .

B

C

D

- A. an SCR
- B. a variable capacitor
- C. a two-transistor oscillator
- D. a Photocell

#6 The output of the two-transistor oscillator is fed into \_\_\_\_\_ of the 555 Timer IC .

A. Pin 5

B. Pin 6

C. Pin 7

D. Pin 8

A

B

C

D

A #2 R1 is connected to \_\_\_\_\_ .

B

C

D

- A. R3
- B. R7
- C. C1
- D. R2

#7 Switch S1 is connected to \_\_\_\_\_ .

A. Pin 4

B. Pin 1

C. Pin 3

D. Pin 6

A

B

C

D

A #3 On the 555 Timer \_\_\_\_\_ .

B

C

D

- A. all but pin 5 are used
- B. all but pin 4 are used
- C. all 8 pins are used
- D. only 6 pins are used

#8 One side of the speaker is connected directly to \_\_\_\_\_ .

A. the Base of Q1

B. the Emitter of Q2

C. Pin 2 on the 555 Timer IC

D. the positive of the battery

A

B

C

D

A #4 The purpose of this circuit is to \_\_\_\_\_ .

B

C

D

- A. emit a siren sound
- B. emit bird chirps
- C. sense heat
- D. sense light

#9 C4 and R6 are connected in parallel to the speaker and \_\_\_\_\_ of the 555 Timer IC.

A. Pin 3

B. Pin 4

C. Pin 5

D. Pin 8

A

B

C

D

A #5 How do you make the circuit emit different tones?

B

C

D

- A. connect and disconnect the battery
- B. adjust R7 and press the pushbutton
- C. vary the heat in the room
- D. feed it birdseed

#10 Capacitor C1 is part of \_\_\_\_\_ .

A. the two-transistor oscillator circuit

B. the voltage regulator circuit

C. the power supply circuit

D. output circuit

A

B

C

D

## QUICK-CHECK ANSWER KEY for Experiment 29 QUIZ for Mr Circuit Electronics Training (“fantasy Space Machine Gun”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



**A** #1 This circuit uses a 555 Timer IC and \_\_\_\_\_ .

**B**

**C**

**D**

- A.** an SCR
- B.** a variable capacitor
- C.** a Photocell
- D.** a two-transistor oscillator

**#6** The Collector of transistor Q2 is connected to \_\_\_\_\_ of the 555 Timer IC.

- A.** Pin 5
- B.** Pin 6
- C.** Pin 7
- D.** Pin 8

**A**

**B**

**C**

**D**

**A** #2 R4 is connected to \_\_\_\_\_ .

**B**

**C**

**D**

- A.** Pin 7
- B.** R7
- C.** C1
- D.** R2

**#7** Switch S1 is connected to \_\_\_\_\_ .

- A.** the positive of the battery
- B.** resistor R6
- C.** the Base of transistor Q2
- D.** the negative of the battery

**A**

**B**

**C**

**D**

**A** #3 On the 555 Timer \_\_\_\_\_ .

**B**

**C**

**D**

- A.** all 8 pins are used
- B.** all but pin 4 are used
- C.** all but pin 5 are used
- D.** only 6 pins are used

**#8** One side of the speaker is connected directly to \_\_\_\_\_ .

- A.** an LED
- B.** Pin 3 on the 555 Timer IC
- C.** Pin 7 on the 555 Timer IC
- D.** the positive of the battery

**A**

**B**

**C**

**D**

**A** #4 The purpose of this circuit is to \_\_\_\_\_ .

**B**

**C**

**D**

- A.** emit a siren sound
- B.** emit bird chirps
- C.** emit phasor machine gun sounds
- D.** emit crunching sounds

**#9** The Anode of the LED is connected directly to \_\_\_\_\_ .

- A.** Pin 3
- B.** the positive of the battery
- C.** the negative of the battery
- D.** Pin 7

**A**

**B**

**C**

**D**

**A** #5 In addition to fantasy machine gun sounds what else does the circuit do?

**B**

**C**

**D**

- A.** vibrates like a snake
- B.** chirps like a bird
- C.** varies the heat in the room
- D.** emits a light effect with an LED

**#10** Resistor R5 is connected across \_\_\_\_\_ .

- A.** pins 6 and 7 of the 555 Timer IC
- B.** the speaker
- C.** the power supply circuit
- D.** output circuit

**A**

**B**

**C**

**D**

## QUICK-CHECK ANSWER KEY for Experiment 30 QUIZ for Mr Circuit Electronics Training (“Ultrasonic Pest Repeller”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.



<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#1</b> This circuit uses a 555 Timer IC and _____.</p> <p>A. a two-transistor oscillator</p> <p>B. a variable capacitor</p> <p>C. a Photocell</p> <p>D. an SCR</p>	<p><b>#6</b> The frequencies that may repel pests are from 13.5 thousand cycles per second to _____.</p> <p>A. 1 Megacycle (1Mhz)</p> <p>B. 80 thousand cycles per second (80kHz)</p> <p>C. 25 Giga Hz</p> <p>D. 10 milli Hz</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>	<p><b>#2</b> R6 is connected to _____.</p> <p>A. Pin 7</p> <p>B. R7</p> <p>C. C1</p> <p>D. Pin 3</p>	<p><b>#7</b> How can you tell if the circuit is working?</p> <p>A. you can feel the speaker vibrate</p> <p>B. resistor R6 will be smoking</p> <p>C. the LED will light up</p> <p>D. the battery will be hot</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#3</b> On the 555 Timer _____.</p> <p>A. all but pin 4 are used</p> <p>B. all 8 pins are used</p> <p>C. all but pin 5 are used</p> <p>D. only 6 pins are used</p>	<p><b>#8</b> One side of the speaker is connected directly to _____.</p> <p>A. the positive of the battery</p> <p>B. Pin 3 on the 555 Timer IC</p> <p>C. Pin 7 on the 555 Timer IC</p> <p>D. an LED</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#4</b> The purpose of this circuit is to _____.</p> <p>A. emit a siren sound</p> <p>B. emit ultrasonic sounds</p> <p>C. emit phasor machine gun sounds</p> <p>D. emit crunching sounds</p>	<p><b>#9</b> C1 is 10uF and it is part of the _____.</p> <p>A. two-transistor oscillator</p> <p>B. power supply circuit</p> <p>C. output circuit</p> <p>D. heat sensing circuit</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p><b>#5</b> What are the signals from this circuit supposed to do?</p> <p>A. repel pests</p> <p>B. chirp like a birds</p> <p>C. varies the heat in the room</p> <p>D. vibrate like a snake</p>	<p><b>#10</b> What capacitor is connected to R3 and R4?</p> <p>A. C1</p> <p>B. C2</p> <p>C. C3</p> <p>D. Q2</p>	<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>