

LESSON 15

2 resistors in Series

Watch video Lesson 15



If you put **two resistors in series**, the total resistance in the circuit is equal to the sum of the two resistors.

If we put a 100 ohm resistor in series with a 330 ohm resistor, the total resistance in the circuit is 100 plus 330 or 430 ohms.

Use Ohm's Law to calculate the current:

$$E = 9 \text{ volts}$$

$$R (\text{total}) = 100 + 330 = 430$$

$$I = ?$$

Ohm's Law says:

$$I = E / R$$

$$I = 9 / 430 = \mathbf{0.02 \text{ Amps}}$$
 or 20 mA
(twenty milliamps)




Mr
CIRCUIT



Practice Quiz
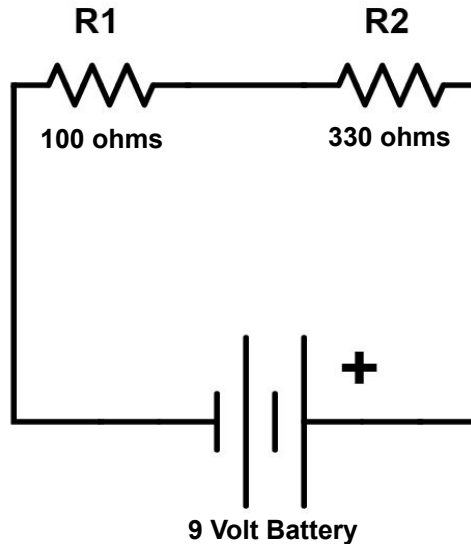
#1

Schematic Diagram of
two resistors, R1 and R2,
in **SERIES** with a 9-volt battery




$$I = E / R$$

How much is the current
flowing in this circuit?

Copyright Mr Circuit Technology 2023
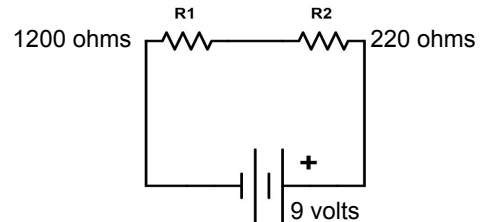
#2

Here is a schematic of two series resistors and a battery. Calculate the **current** flowing in this circuit?




Answer: Current (I) = E / R

$$I = 9 / 1420$$

$$I = \mathbf{0.006 \text{ Amps or } 0.6 \text{ mAmps}}$$
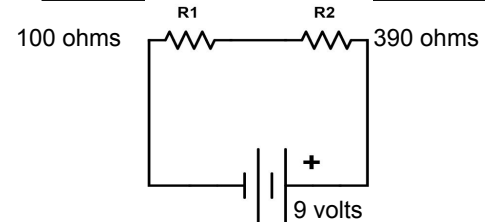
#3

Here is a schematic of two series resistors and a battery. Calculate the **current** flowing in this circuit?



Answer: Current (I) = E / R

$$I = 9 / 490$$

$$= \mathbf{0.018 \text{ Amps or } 18 \text{ mAmps}}$$

Solve the following
problems using Ohm's Law

Activity Page


2 resistors in Series
With Ohm's Law

15b


Here are circuits with 2 resistors in Series. With Ohm's Law, calculate the **current** flowing in each circuit.

(Round your answer to the nearest thousandth.)


1

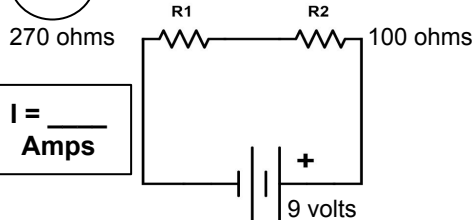


2

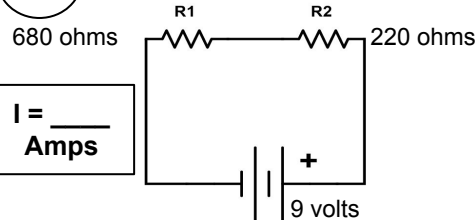


3

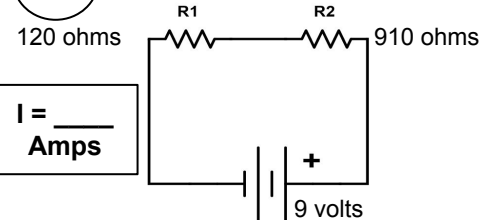


4

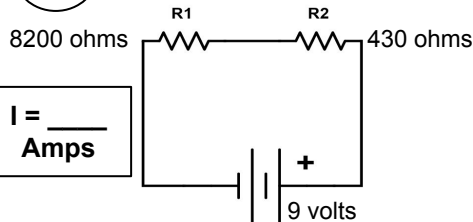

5

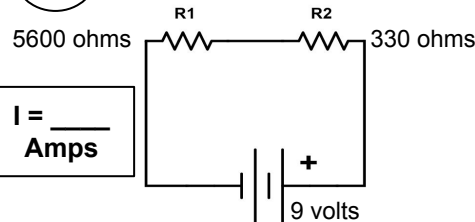

6

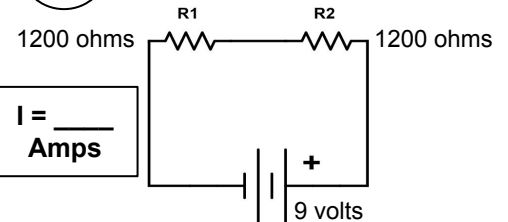

Ans: 0.024, 0.010, 0.009, 0.006, 0.002, 0.004

