

**LESSON 26****Measuring Current With 1000  $\Omega$** 

Using the meter setup procedure as explained in Lesson 23, build this circuit with a 1000 ohm resistor and measure the current.

Use the picture on the right to help you build the circuit. Use meter probe tips instead of alligator clips to complete the circuit.


As you touch the tips to the circuit, observe the meter display to see how much current is flowing.

Our meter shows 7.40 mAmps. How much current is flowing in "your" circuit?

\_\_\_\_\_ mAmps



Practice Quiz 26

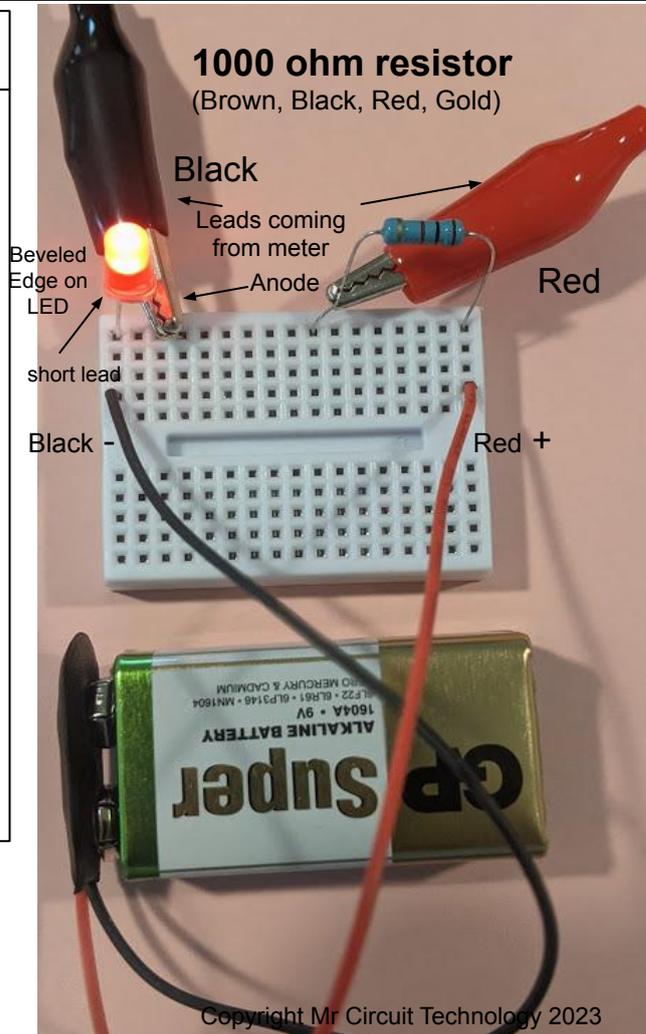

Copyright Mr Circuit Technology 2023

Multimeter set up as an Ammeter to measure current (on 20 mA scale)



showing 7.40 mA  
of current flowing

## Answer these questions

(1) True or False? In this experiment, the black probe tip of the meter is touching the positive or Anode of the LED

\_\_\_\_\_

(2) What is the black probe tip of the multimeter touching?

\_\_\_\_\_

(3) Is one side of the 1000 ohm resistor connected to the red red wire on the battery snap?

\_\_\_\_\_

(4) The electrons leave the battery from the negative side and travel first through the

\_\_\_\_\_

## Activity Page

(5) True or False? The multimeter in series with the rest of the circuit?

\_\_\_\_\_

(6) Is the LED less bright than in Lesson 25?

\_\_\_\_\_

(7) If we remove the meter from the circuit, will the LED continue to be lit?

\_\_\_\_\_

(8) True or False? There is less current flowing now than in Lesson 25 because we have increased the ohms of the resistor in the circuit.

\_\_\_\_\_

Copyright Mr Circuit Technology 2023

Comparing the current in a circuit with 1000  $\Omega$ 

26b

(9) How many **milliAmps** is it showing on the multimeter display on page 26a?

\_\_\_\_\_

(10) How many **milliAmps** was showing on your multimeter display when you built this new circuit?

\_\_\_\_\_

