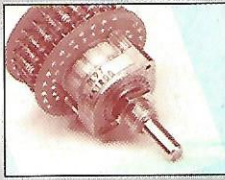



Frans Scheyving,  
p. 32

3 Stages  
2 Tubes  
4.3 Watts



Dan Norman, p. 38

Matched  
Precise  
Levels

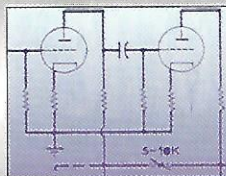

Joseph Marshall, p. 56

Better  
Power  
Designs

Volume 11 Number 5 1999

\$6.00  
CANADA \$8.57

# GLASS AUDIO



## 70W 6L6GC Low-Distortion Amp

BY SCOTT K. REYNOLDS



This construction project began several years ago when I bought a pair of Magneplanars. It wasn't long after I set them up in my living room that I realized I would need a more powerful amplifier. I had been using a 20W-per-channel, Class A tube amplifier, and although it was delightful to listen to in combination with the Maggies at low or moderate volumes, it really didn't have enough punch to reproduce symphonic music or jazz at realistic levels.

I decided to try the Maggies with my Williamson 20/20 amplifier,<sup>1</sup> which (with a regulated power supply) will deliver 60+W into a 5Ω load. I found the 20/20 to be a more satisfying choice for reproducing higher-volume levels, and I suppose that a reasonable person would just have sat back to enjoy the music at that point. However, no one has ever accused me of being reasonable about stereo equipment, and I still thought there was more to gain sonically and aesthetically by building a more powerful tube amplifier.

Based on my experience with the 20/20, I set 70W per channel as a minimum design target. I also set a goal of matching the 20/20's distortion performance,

to page 14



from page 1

which proved to be very difficult, since I wasn't willing to use a large amount of negative feedback in my design. Finally, I decided to use the 6L6GC as the output tube, because I liked the way it performed in my smaller class A amplifier, and also because it is used so widely in guitar amplifiers that there is a good selection of brands and types (the KT-66, 7581A, and 7027A are all essentially identical to the 6L6GC, and the Sovtek 5881 is similar).

I have found the 6L6GC to be rugged, reliable, and stable, but it does have some disadvantages. It is a very old design, with lower transconductance than more modern power tubes such as the EL-34, 6550, or 8417. Operated without feedback, it also tends to have higher measured distortion than those tubes. Nevertheless, the advantages outweighed the disadvantages for me, and I began work.

### CIRCUIT DESCRIPTION

With my goal of achieving low distortion in mind, I decided to try a slightly unusual circuit topology involving nested feedback loops (Fig. 1). Table 1 is the parts list. The push-pull-parallel output stage is conventional, but I used about 14.4dB of local negative feedback to linearize the 6L6GCs. This feedback is then surrounded by a conventional global feedback loop with about 15dB of negative feedback.

The result is a highly stable and low-distortion amplifier. It does not quite match the performance of the 20/20, but it does achieve THD of <0.15% at 70W and 1kHz, a respectable number in the

world of vacuum tubes. Distortion decreases at lower power levels. The Plitron output transformer has a nominal power rating of 70W, but at midband (50Hz–10kHz) the amplifier delivers more than 90W at 1% THD. Other specifications are summarized in Table 2.

This description makes the design process seem quite simple and straightforward, but in reality I experimented with just about every aspect of the circuit before coming to the final result in Fig. 1. As I describe the circuit, I'll discuss some of the design tradeoffs that I made along the way, starting with the output stage.

The 6L6GCs are operated with a 500V plate supply, which is their maximum rating. Using the maximum plate-supply voltage obviously gives the most power output (assuming you don't exceed any other tube ratings), and I've found it also gives the lowest measured distortion. For push-pull-parallel Class AB<sub>1</sub> operation at 500V, a plate-to-plate load impedance in the range of 2.5k–3.2kΩ is appropriate, multiplying the suggested push-pull operating loads for the 6L6GC and 7027A in the RCA Tube Manual<sup>2</sup> by one-half.

The suggested screen voltage from the manual is in the 350–400V range, but here I have chosen to set it a bit on the low side, at 340V. Lower screen voltage yields lower screen dissipation, which in my experience results in a more stable operating point and longer tube life. Setting the screen voltage up to its 400V maximum will reduce distortion slightly and increase power output a few watts, so you can experiment here.

### OUTPUT TRANSFORMER

The Plitron PAT4004 was not my first selection for output transformer, although it has proven to be an excellent choice. I began constructing the prototype using a pair of Thordarson transformers purchased many years ago, but I was very disappointed in their high-frequency power bandwidth, so I looked through *Glass Audio* to find a source for better ones.

I was initially concerned about the PAT4004's power-handling capability, since its 70W rating was at the low end of my design target. At midband, however, I discovered the Plitron transformer can handle over 100W. I have one caveat about the PAT4004's low-frequency power bandwidth that I will discuss later. I did not use the ultralinear taps on the PAT4004 in this design.

I've used a relatively large (47Ω) unby-passed cathode resistor for each 6L6GC. In most circumstances this would not be done, because it reduces the gain of the tube and increases both the plate resistance and the required signal voltage swing at the grid. In this case, however, you are controlling the gain and output resistance of the final stage with a local feedback loop, and so can get away with using the large cathode resistors. These have the benefit of equalizing the dynamic currents through the paralleled tubes, so that matched output tubes are not required. This was important for me because I had a quantity of unmatched, new old stock (NOS) RCA 6L6GCs that I wished to use in the amplifier.

I set the quiescent current in each

**TABLE 1**  
**AMPLIFIER PARTS LIST (EACH CHANNEL)**

RESISTORS		CAPACITORS	
R1, R12–R15	100kΩ, ½W, 2%	C1	2μF, 400V, film
R2	10kΩ, ½W, 2%	C2, C3	0.1μF, 600V, film (don't be tempted to substitute a higher
R3, R26, R27, R36, R37	100kΩ, 1W, 2%		
R4	1.8kΩ, ½W, 2%		
R5	27Ω, ½W, 2%		
R6	27kΩ, 2W, 2%		
R7	no longer used		
R8	470kΩ, ½W, 2%		
R9	1MΩ, ½W, 5%		
R10, R11	50kΩ, 1W, 2%		
R16, R17	910Ω, ½W, 2%		
R18, R19	10kΩ, 2W, 2%		
R20, R21	500Ω, ¾W, 15-turn trimmer		
R22, R23, R28, R29	1kΩ, ½W, 5%		
R24, R25, R30, R31	47Ω, 2W, 2%		
R32, R35	100kΩ, 2W, 2%		
R38, R39, R42, R43	10kΩ, ¾W, 15-turn trimmer		
R40, R41, R44, R45	10kΩ, ½W, 5%		
R46	330Ω, 3W, 2% (three 1kΩ, 1W resistors in parallel)		
R47	5kΩ, ¾W, 15-turn trimmer		
TUBES		T1	
V1	5879 pentode (connected in the circuit as a triode with μ = 21. Could substitute 6J5, 6C4, half of a 6SN7GT/B, etc.)	Q1, Q2	MPF102, n-channel Si JFET
V2, V4, V5	12AU7 or 5814 dual triode (I don't recommend Chinese 12AU7. Could substitute 6SN7GT/B.)		
V3	6SN7GT/B (I prefer NOS.)		
V6–V9	6L6GC, 7581A, 7027A, KT-66, Svetlana 6L6GC, or Sovtek 5881. (6L6, 6L6G, 6L6GA, 6L6GB, 5881 other than Sovtek, and all Chinese 6L6 types are unsuitable because they have lower ratings.)		
	Plitron PAT4004, 2700Ω plate-to-plate primary, 5Ω secondary (ultralinear taps are not used. Don't substitute unless you're experienced; see text.)		

output tube to 50mA, equivalent to 2.35V across each of the 47Ω cathode resistors. The grid-bias voltage to obtain this value is approximately -28V, for a total grid-to-cathode bias of about -30V. The 50mA quiescent current gives a total plate-plus-screen dissipation of 25W, which is well within the 30W plate dissipation and 5W screen dissipation ratings of the 6L6GC. This conservative operation of the tube should result in long tube life. Higher quiescent currents will reduce distortion, as I discuss later in the article. The grid-bias voltage for each output tube is set independently with trimmer potentiometers R38-R39 and R42-R43.

### DRIVER STAGE

The driver stage is unusual, so it deserves some attention. The active gain element for the top side of the push-pull circuit is one section of a 6SN7 (V3A) with a very large (10kΩ) cathode resistor (R18) to accept feedback from the 6L6GC's plates via two 100kΩ resistors in series (R32 and R33). The unbypassed 10kΩ cathode resistor would ordinarily reduce the gain

too much, so I have provided a constant-current source load consisting of an FET (Q1) and the paralleled sections of a 12AU7 (V4).

A low-impedance output is taken from the common cathodes of the 12AU7 sections. This stage is a modified mu-follower, with the bias current set to 5mA by a small potentiometer (R20) in the source lead of Q1. If you break both the inner and outer feedback loops, you can measure a gain of approximately 105 (40.4dB) from the grids of the 6SN7 to the plates of the output tubes. With the inner feedback loop closed, this gain is 20 (26dB),

so there is approximately 14.4dB of negative feedback.

This local feedback loop around the output and driver stages not only helps to reduce the distortion of the 6L6GCs, but also reduces their output impedance, making their performance less sensitive to variations in speaker-load impedance. Also, the output transformer produces less distortion and has wider bandwidth when driven from a lower impedance source. Menno van der Veen discusses this effect briefly in a letter published in *Audio Electronics* (1/98).<sup>3</sup>

to page 20

**TABLE 2**  
**AMPLIFIER SPECIFICATIONS**

Power output:	70W per channel into 5Ω, nominal power rating. Actually delivers >90W continuous power into 5Ω at 1% THD, 50Hz-10kHz
Frequency response at 7W:	+0/-1dB from 9Hz-21kHz +/-3dB from 4Hz-46kHz
Power bandwidth at 70W:	+0/-3dB from 24Hz-46kHz
Total harmonic distortion:	0.15% at 70W and 1kHz. See Figs. 3-4
Intermodulation distortion:	0.4% at 70W, 60Hz, and 6kHz, mixed 4:1. See Fig. 5
Closed-loop gain:	22dB
Sensitivity:	1.5V RMS for 70W into 5Ω
Open-loop gain:	37dB

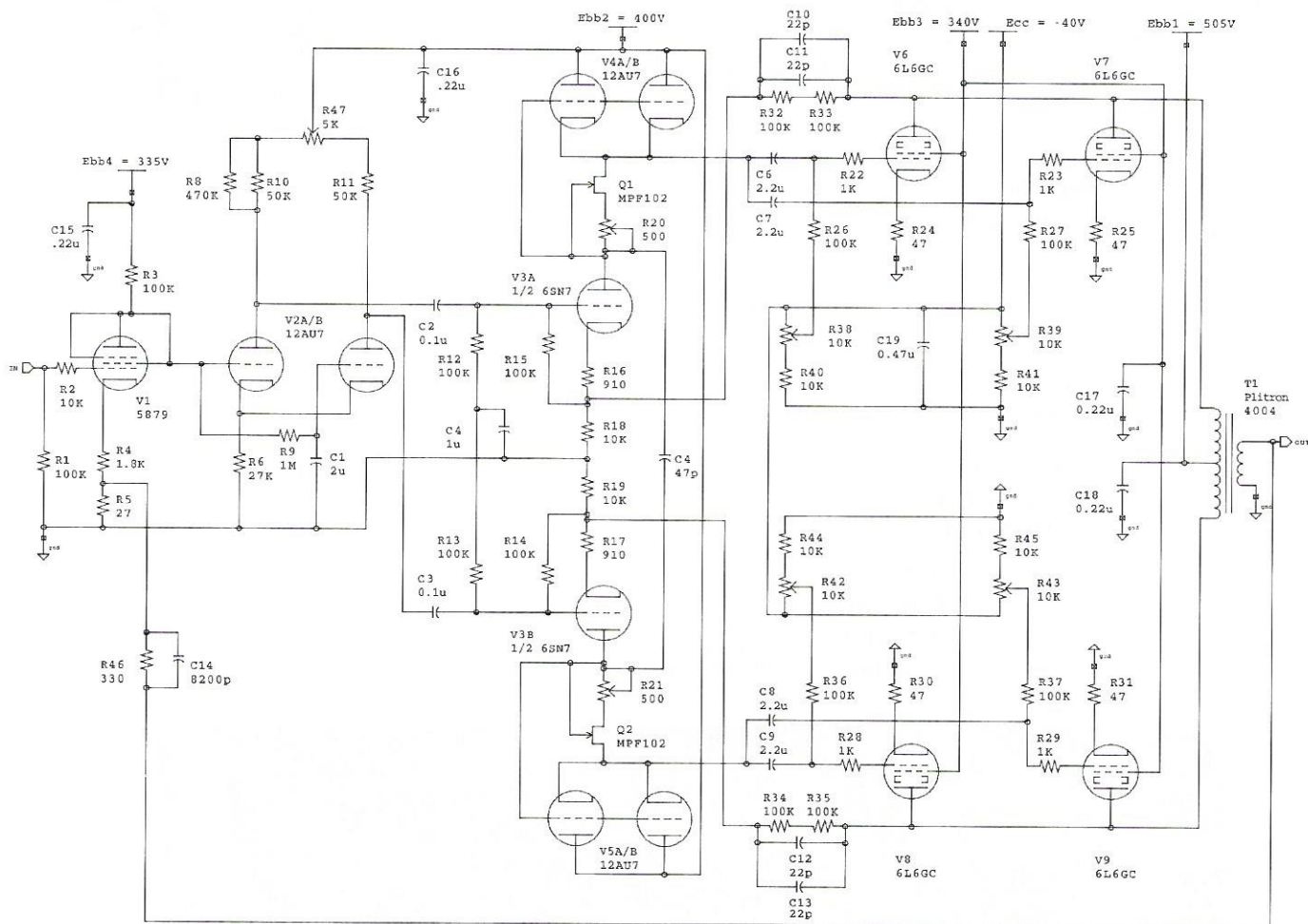


FIGURE 1: Amplifier schematic.

### INPUT STAGES

The input stages consist of a conventional voltage amplifier V1 and "long-tailed" phase splitter V2. I experimented with constant-current biasing of V2, as a replacement for the cathode resistor R6. This balanced the two out-of-phase outputs without the need for unequal plate-load resistors, but I found that I still needed an AC balance control (R47) in order to obtain minimum IM distortion for the amplifier as a whole. Therefore, I eliminated the constant-current source and reinstalled R6 to simplify the circuit.

A triode-connected 5879 pentode is used for the input-voltage amplifier. The 5879 is a low-noise, low-microphonics tube originally used primarily for microphone amplifiers. It produces very low distortion as a triode (it's pretty good as a pentode, too), and I've had good results with it. Note that both the screen and the suppressor are connected to the plate for triode operation. So connected, the 5879 has a  $\mu$  of 21.

You may have noticed that all the tubes used in the voltage amplifier and driver stages are medium- $\mu$  triodes. In the parts list, I've suggested several possible tube substitutions, since a wide variety of medium- $\mu$  triodes exist. For in-

stance, you could build the amplifier entirely with 6SN7 tubes if you wish. Note that I haven't built and tested all these combinations, so to be conservative, a beginner should stick to the schematic as drawn, but I can't think of a reason why the substitutions wouldn't work.

With the outer feedback loop open, the overall amplifier gain from input to speaker output is about 70, or 37dB. With the loop closed, the gain is about 22dB, so there is 15dB of negative feedback around the entire amplifier. In using negative feedback, you need to be concerned about stability. In this case, with nested feedback loops, stability considerations become a bit more complicated than usual, and the amplifier must be frequency-compensated by working from the inside feedback loop outward to the global loop.

### CONSERVATIVE DESIGN

I've chosen to be very conservative in my design, favoring stability over extremely wide bandwidth. Experienced readers can experiment with frequency compensation to suit their own preferences, but inexperienced builders should follow the schematic exactly as shown to avoid problems. It is important to note that the values of frequency-compensation com-

ponents depend very strongly on the choice of output transformer, so you should not substitute for the Plitron PAT4004 unless you are willing to compensate the amplifier yourself.

Capacitor C4 places a high-frequency dominant pole at roughly 13kHz within the inner feedback loop. Capacitors C10-C13 provide lead compensation for the inner feedback loop. This compensation decreases the closed loop gain of the driver and output stages at high frequencies, with a 3dB point at 15kHz. The location of this 3dB point is determined partly by the values of C10-C13 and R32-R35, and partly by the location of the dominant pole created by C4. This lead compensation of the inner feedback loop creates a 15kHz dominant pole for the outer feedback loop.

Finally, the outer feedback loop is lead-compensated by capacitor C14. Closed-loop gain decreases at high frequencies, with a 3dB point of 46kHz. The location of this 3dB point is determined partly by the parallel combination of C14 (8200pF) and R46 (330 $\Omega$ ), and partly by the location of the outer feedback loop dominant pole at 15kHz, as described earlier.

This frequency compensation gives the amplifier excellent high-frequency stability. You also need to be concerned

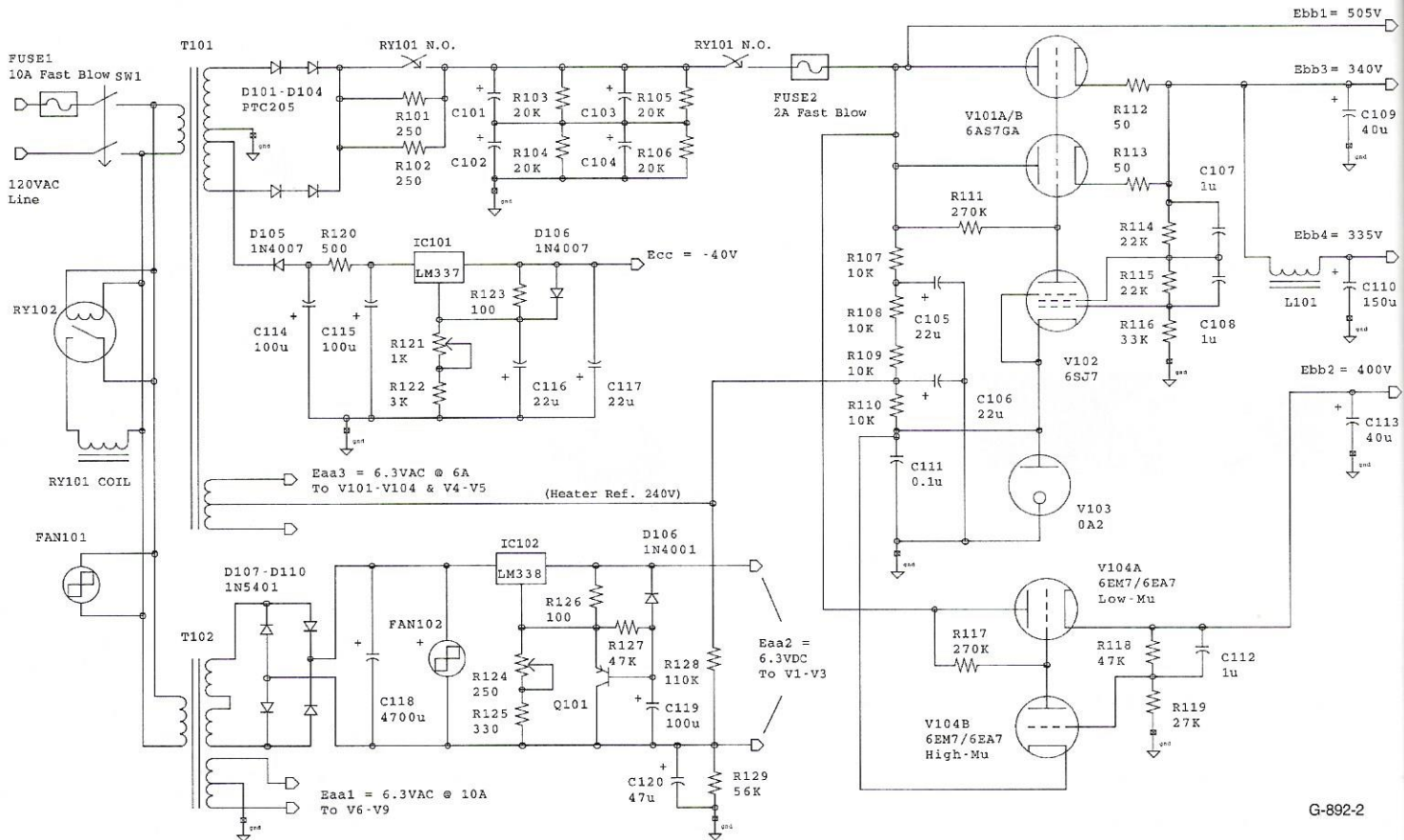


FIGURE 2: Power-supply schematic for two stereo channels.

**TABLE 3**  
**POWER-SUPPLY PARTS LIST (FOR TWO CHANNELS)**

**RESISTORS**

R101, R102	250Ω, 10W, wirewound
R103-R106	20kΩ, 10W, wirewound
R107-R110	5kΩ, 5W, wirewound
R111, R117	270kΩ, 1W, 5%
R112, R113	50Ω, 2W, 5%
R114, R115	22kΩ, 3W, 5%, metal oxide
R116	33kΩ, 3W, 5%, metal oxide
R118	47kΩ, 3W, 5%, metal oxide
R119	27kΩ, 3W, 5%, metal oxide
R120	500Ω, 1W, 5%
R121	1kΩ, ½W, trimmer
R122	3kΩ, ½W, 5%
R123, R126	100Ω, ½W, 5%
R124	250Ω, ½W, trimmer
R125	330Ω, ½W, 5%
R127	47kΩ, ½W, 5%
R128	110kΩ, 1W, 5%
R129	100Ω, ½W, 5%

**CAPACITORS**

C101-C104	2500μF, 300VW DC, computer grade electrolytic
C105, C106	22μF 450VW DC, electrolytic
C107, C108, C112	1μF, 250V, film
C109, C113	40μF, 450VW DC, electrolytic
C110	150μF, 450VW DC, electrolytic
C111	0.1μF, 600V, film
C114, C115	100μF, 100VW DC, electrolytic
C116	22μF, 1000VW DC, electrolytic
C118	4700μF, 25VW DC, electrolytic
C119	100μF, 16VW DC, electrolytic
C120	47μF, 100VW DC, electrolytic

**TUBES**

V101	6AS7GA or 6080, dual low-mu triode
V102	6SJ7GT, pentode
V103	0A2, 150V gas-filled regulator
V104	6EM7/6EA7, dual triode (the high-mu section is V104B, the low-mu section is V104A)

**DIODES**

D101-D104	PTC205, 1000PIV, 2.5A rectifier diode
D105, D106	1N4007
D107-D110	1N5401
D111	1N4001
Q101	2N2907 or equivalent PNP Si bipolar
IC101	LM337T, TO-220 adjustable regulator
IC102	LM338K, TO-3 adjustable regulator (mount on large heatsink or chassis)
L101	15H @ 75mA filter choke (if no power take-off is desired, may substitute a 2.2kΩ, 1W resistor; see text)
T101	400-0-55-400V @ 800mA (420-0-60-420V no load) 6.3V @ 6A
T102	6.3V @ 10-12A, 5V @ 3A, 5V @ 3A
RY101	10A DPDT relay with 120V AC coil
RY102	Amperite 115NO30 thermal-delay relay (could substitute any electronic or mechanical delay relay adjusted for 30 seconds turn-on delay)
FAN101	120V AC fan, 4½" diameter, mounted above T101
FAN102	12V DC fan to ventilate the underside of the power supply chassis; the sort used in PCs is suitable
SW1	10A DPST toggle

**Best Quality Available**  
Best Materials/Design • Longest Life • Cool Running

**LAB TESTED**

**TESLA**  
**E34L/EL34**



**GE**  
**6550A**



**EI**  
**6CA7**



**ARS ELECTRONICS**  
ELECTRONIC TUBE SPECIALISTS  
7110 DeCielis Place • P.O. Box 7323  
Van Nuys, California 91406

**(818) 997-6279**  
**FAX: (818) 997-6158**

**Audiophile Electron Tubes**

**MATCHED POWER TUBES**

P/N	EACH	PAIRS	QUARTET	P/N	EACH	PAIRS	QUARTET
2A3 CHINA	25.00	50.00	100.00	KT90/99	24.00	48.00	96.00
6BQ5/EL84 Philp/Syl	15.00	30.00	60.00	211	50.00	120.00	
6BQ5/EL84 Yugo/EI	11.00	22.00	44.00	300B CHINA	78.00	156.00	
6CA7/EL34 Yugo/EI	18.00	36.00	72.00	807 RCA USA	25.00	50.00	100.00
6L6 TESLA	18.00	36.00	72.00	845 CHINA	50.00	120.00	
6L6WGB Philp/Syl USA	19.00	38.00	76.00	5881 Philp/Syl USA	19.00	38.00	76.00
Mil-Spec				Mil-Spec			
E34L TESLA	14.00	28.00	56.00	5881/6L6WGC USSR	12.00	24.00	48.00
EL34 TESLA	14.00	28.00	56.00	6550A CHINA	19.00	38.00	76.00
KT88 CHINA	25.00	50.00	100.00	6550A GE USA	42.00	84.00	168.00
KT88 TESLA	39.00	78.00	156.00	6550WC USSR/SVT	25.00	50.00	100.00

**PRE-AMP TUBES**

5AR4 CHINA	15.00	LM-12AU7A EI	12.00	LOW NOISE
5U4GB USA	20.00	12AU7/6189W GE/SYL/RCA	8.50	
6AN8A	15.00	12AX7A CHINA	8.50	
6AU6A	6.50	LM-12AX7A CHINA	12.00	LOW NOISE
6CA4	15.00	12AX7A EI	8.50	
6CW4 RCA	20.00	LM-12AX7A EI	12.00	LOW NOISE
6DJ8 EI	8.50	12AZ7 USA	15.00	
LM-6DJ8 EI	12.00	12BH7A USA	20.00	
6FQ7 USA	20.00	12BH7A EI	15.00	
6FQ7/6CG7 EI	15.00	12BY7A SYL/GE	15.00	
6SL7GT FOREIGN	8.50	12FQ7 USA	15.00	
6SL7WGTA USA	12.00	12X4 USA	15.00	
6SN7GT FOREIGN	8.50	5751 GE/SYL	15.00	
6SN7GT USA	12.00	5965A USA	15.00	
6X4 USA	9.00	6267/EF86	12.00	
12AT7WC PHILP/SYL	8.50	6922/E88CC TESLA	12.00	
12AU7A TELEFUNKEN	25.00	LM-6922/E88CC TESLA	18.00	LOW NOISE
12AU7A EI	8.50	7199 USSR	15.00	




Ship By Fedex or UPS  
**NEW TUBES ARRIVING DAILY**  
Over 100,000 Tubes in Stock

**MIN. ORDER**  
\$35<sup>00</sup>


★ **WORLD WIDE SHIPPING** ★




Prices Subject to Change

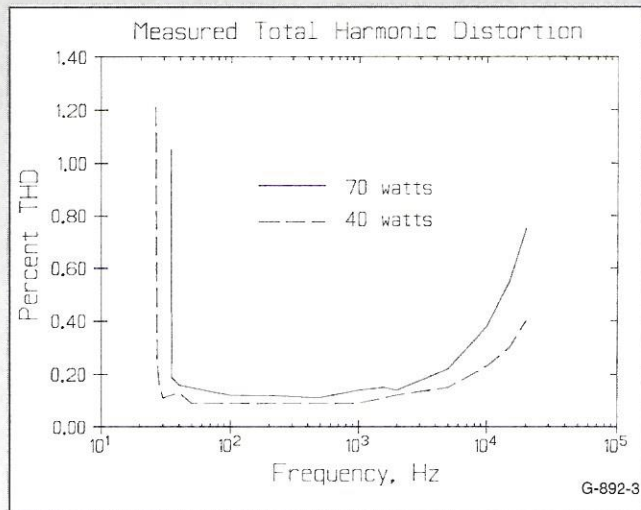

**FIGURE 3: Measured total harmonic distortion versus frequency at 70W and 40W into 5Ω. Meter residual is 0.08%.**

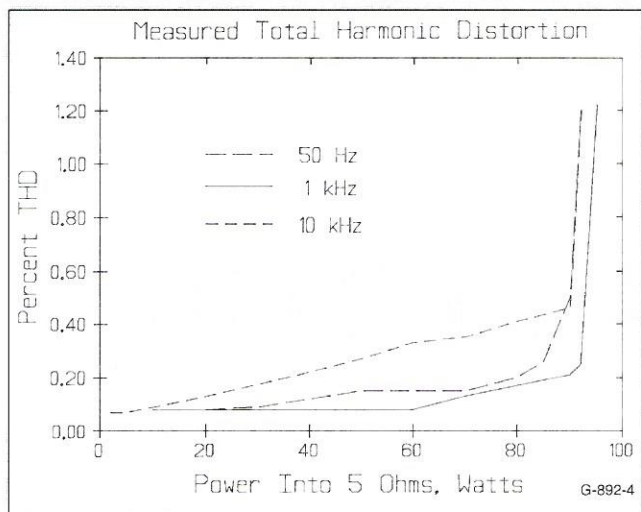

**FIGURE 4: Measured total harmonic distortion versus power into 5Ω at 50Hz, 1kHz, and 10kHz. Meter residual is 0.08%.**

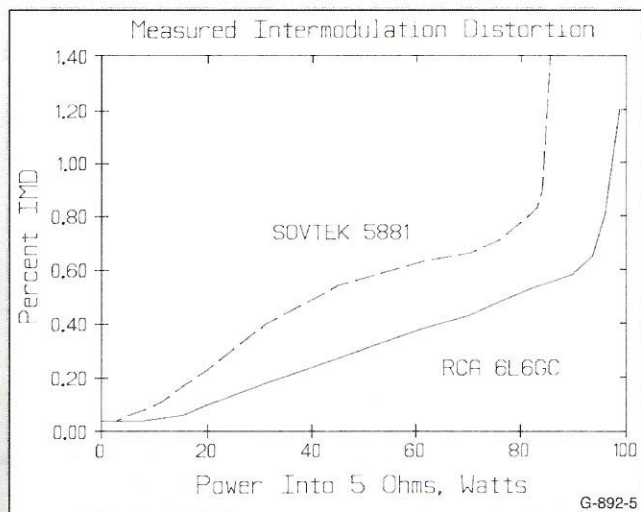

**FIGURE 5: Measured intermodulation distortion versus power into 5Ω, 60Hz and 6kHz mixed 4:1. Meter residual is 0.06%. Data is shown for the RCA 6L6GC and Sovtek 5881. The Sovteks produced consistently higher distortion and lower power output than other tubes I tried.**

about low-frequency stability, but that is much simpler. You establish a low-frequency dominant pole at about 11Hz by coupling capacitors C2 and C3. Any phase shift added by coupling capacitors C6–C9 or the output transformer T1 is at much lower frequencies. The resulting amplifier is stable with or without a secondary load on T1.

### POWER SUPPLY

I chose to design a single power supply for both stereo channels, but there is no reason why you couldn't follow a dual monoblock approach, as long as you provide the same supply voltages and currents. Referring to Fig. 2 (Table 3 is the power-supply parts list), plate supply Ebb1 provides 505V under idle conditions, which is 200mA per channel. Current drain increases to 400mA per channel at maximum signal. Plate supply Ebb1 is unregulated, but computer-grade capacitors C101–C104 have a net capacity of 2500μF, which provides a very large energy reservoir.

With such large capacitors, the turn-on surge needs to be controlled, which is the function of relays RY101 and RY102. At turn-on, C101–C104 initially charge through power resistors R101 and R102, providing a controlled ramp-up of the capacitor voltage. After 30 seconds, thermal-delay relay RY102 energizes the coil of RY101, which in turn shorts out resistors R101 and R102 and supplies high voltage to the 6L6GC plates and the rest of the power supply.

The balance of the high-voltage supplies are regulated. Screen-supply Ebb3 is 340V at 45mA maximum per channel. Supply Ebb4 is 335V at 2mA per channel for the 5879 input tube. Supply Ebb2 is 400V at 15mA per channel for the phase splitter and driver.

The voltage regulators are a conventional design. Gaseous regulator tube V103 (0A2) provides a 150V reference for the error amplifiers V102 (6SJ7) and V104B (the high-μ section of a 6EM7/6EA7). V104A (the low-μ section of the 6EM7/6EA7) serves as the pass tube for supply Ebb2 and dissipates 3W. V101 (6AS7GA) serves as a pass tube for the screen supply.

Using a 6AS7 might seem a bit of overkill here, since V101 dissipates no more than 15W under maximum signal conditions, and much less than that normally. However, I wished to use the 335V supply Ebb4 as a possible power take-off for my tuner, preamp, or CD player at some point in the future, so I designed the regulator to have excess capacity. Similar-

ly, decoupling choke L101 is grossly over-rated at 75mA, since it passes only 4mA, but it will serve for the future power take-off. If no power take-off is desired, you can replace choke L101 with a simple 2.2k $\Omega$ , 1W decoupling resistor for much less cost.

Transformer T101 has a 55V tap that I used for the bias supply. A half-wave rectifier and an RC filter produces -72V at the input to the regulator IC101. The regulator output Ecc is adjusted for -40V DC. The amplifier requires several heater supplies. A separate transformer T102 has a 6.3V AC @ 10-12A winding, which I used for the 6L6GC heaters.

The heaters of tubes V4 and V5 in the amplifier and tubes V101, V102, and V104 in the power supply run off a 6.3V AC @ 6A winding on T101, which is biased 240V above ground to reduce the heater-cathode potentials. A 6.3V DC heater supply is provided for tubes V1-V3. Transformer T102 has two 5V AC @ 3A windings, which I wired in series for this supply. The circuit is a standard slow-turn-on regulator using the LM338K, a rugged three-terminal regulator in the TO-3 package, allowing for good heatsinking.

#### COOLING CONCERNS

I purchased transformer T101 from a sur-

plus dealer several years ago, and I don't know of any current production product which is an exact duplicate. The T101 has a 400-0-55-400V secondary, rated at 800mA, so any transformer (or combination thereof) that provided this would be suitable. As an alternative, you could use two Hammond 278CX transformers (400-0-400V @ 465mA) in a dual-mono approach.

Transformer T101 proved not to be as conservatively rated as I had hoped, and in my prototype the temperature of T101 reached 60-65°C after several hours of operation, heating up the entire power-supply chassis. After prolonged high-power testing, it became even hotter. I considered this unacceptable, so I provided fan cooling for T101 and for the power-supply chassis. FAN101 is a 4"-diameter, 120V AC cooling fan mounted directly above T101. FAN102 is a small 12V DC fan (the sort used for cooling computers) that I used to ventilate the underside of the power-supply chassis. T101 and the supply chassis now barely rise above room temperature. If you wish to avoid fan cooling, I recommend a more conservatively rated power transformer.

In my setup, the power supply is mounted remotely from the amplifier,

connected to it via a 12' cable that runs from my listening room into the cellar, where the power supply sits on a shelf. This keeps the fan noise, transformer buzz, and power-supply heat dissipation out of the listening environment. The only caveat is that the heater supplies require heavy-gauge wiring to prevent excessive voltage drop; I used paralleled sections of 14-gauge stranded wire.


The overrated heater windings result in more than 6.3V AC at the transformer secondaries, so a drop of a few tenths of a volt in the cable is acceptable. With such a long cable, the DC power supplies need to be bypassed on the amplifier chassis; that is the function of C15-C19.

#### PERFORMANCE EVALUATIONS

Distortion measurements on the amplifier are summarized in *Figs. 3-5*. I measured harmonic distortion using the spectrum-analysis capability of a digital-storage-oscilloscope (DSO) card that I have for my lab computer. This DSO can resolve distortion down to about 0.08%, which is the noise floor in spectrum-analysis mode. Amplifier distortion is predominantly third harmonic, with a small amount of uncanceled second harmonic at low frequencies.
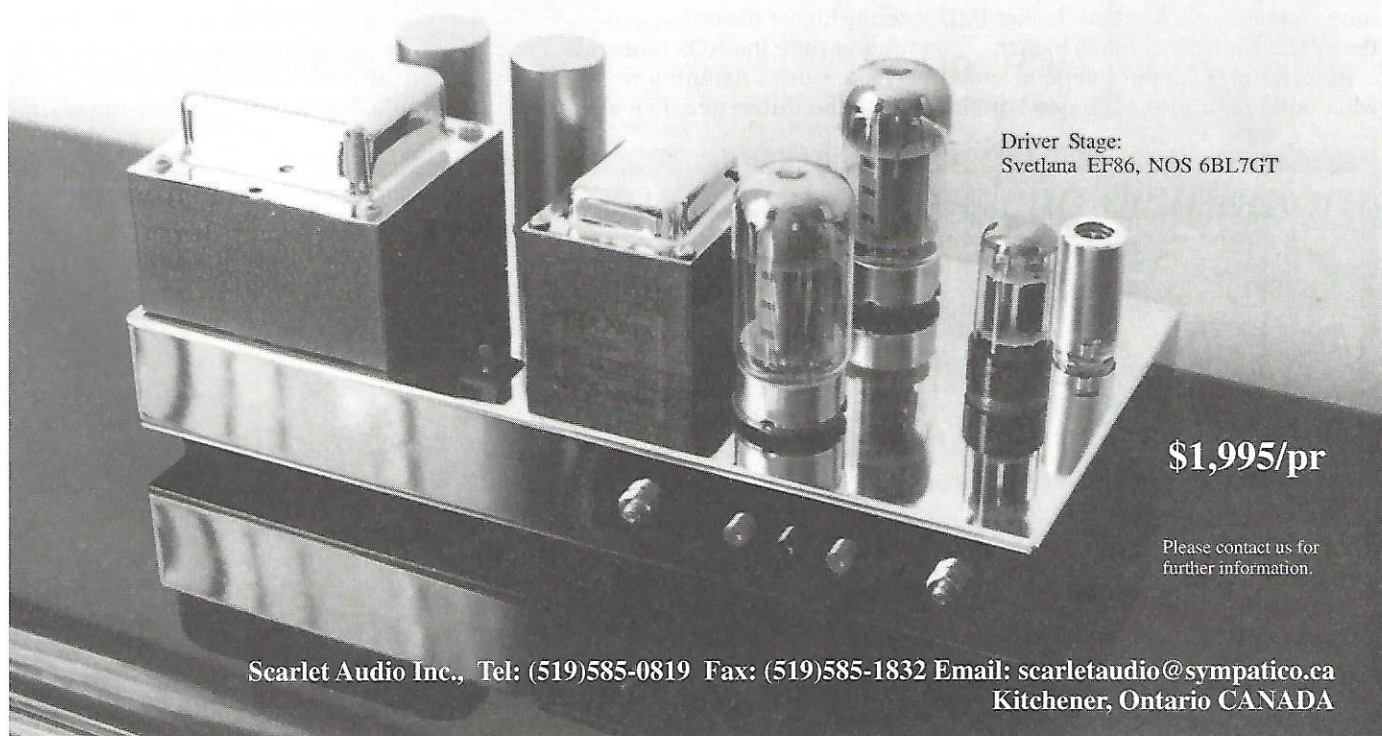
## SA-6550-M

Quick, clean, detailed and powerful monoblocks  
Triode connected Svetlana SV6550C's  
33W push-pull zero feedback design




Driver Stage:  
Svetlana EF86, NOS 6BL7GT


\$1,995/pr

Please contact us for  
further information.

Scarlet Audio Inc., Tel: (519)585-0819 Fax: (519)585-1832 Email: scarletaudio@sympatico.ca  
Kitchener, Ontario CANADA

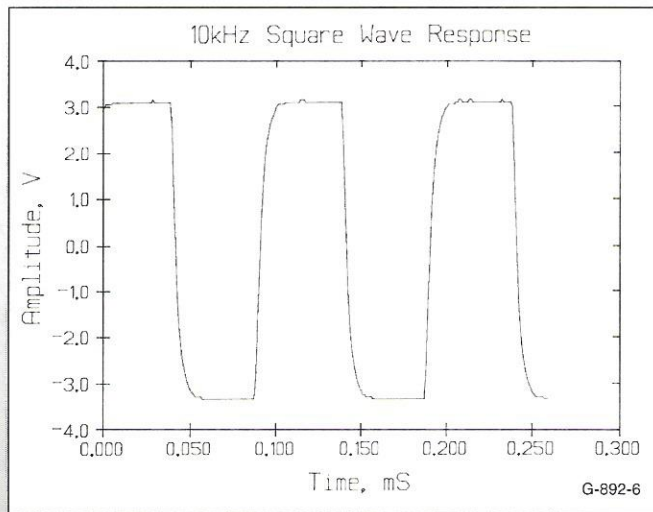

**FIGURE 6:** Square-wave response, 10kHz into 5Ω resistive load.

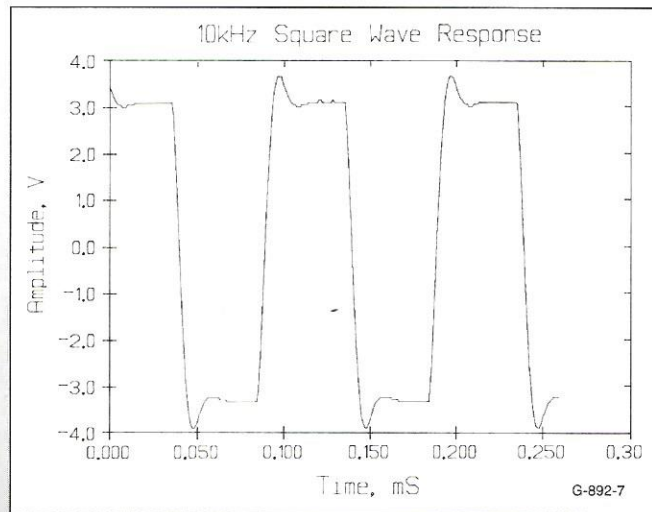

**FIGURE 7:** Square-wave response, 10kHz into 5Ω in parallel with 2.2μF, demonstrating stability into capacitive loads.

At 1kHz, distortion is at or below the noise floor of the DSO for power levels below about 50W. Distortion rises at high frequencies, as is common with most tube amplifiers. At 70W and 10kHz, harmonic distortion is 0.38%, and at 20kHz it reaches 0.75%. This rise in distortion at high frequencies is partly due to a reduction in negative feedback caused by falling loop gains, a byproduct of the frequency-compensation method used.

I measured intermodulation distortion (IMD) with a modified Heathkit IM-48, using 60Hz and 6kHz mixed 4:1. The meter residual in this case is about 0.06%. At 70W, the amplifier produces 0.4% IMD, a figure consistent with the THD measurements. In my experience, tube amplifiers usually have higher IMD than THD, sometimes much higher.

All distortion readings depend somewhat on the output-tube quiescent bias

current, decreasing as the bias current increases. The measurements in Figs. 3–5 were taken at 50mA per tube. Increasing the current to 60mA drops the THD at 70W and 20kHz from 0.75% to 0.62%. I experimented with these higher bias currents and decided I couldn't hear the difference, so I set the current back to 50mA to prolong tube life.


Distortion readings also depend somewhat on which individual tubes you use in the amplifier, suggesting that it is probably possible to select a set of tubes to give lower distortion. This is a small effect, however, and no brand of NOS tubes that I tried (RCA, GE, Raytheon) gave consistently lower distortion. The Sovtek 5881 gave consistently higher distortion and lower power output than the NOS tubes, as shown in Fig. 5, but in listening tests I couldn't hear the difference. I've also tried the

new Svetlana 6L6GCs, which work well and sound as good as the others, but I haven't yet made distortion measurements with them.


### SQUARE-WAVE PERFORMANCE

I also examined the amplifier's square-wave performance as a test of high-frequency stability. Figure 6 is a plot of the amplifier's 10kHz square-wave response into a 5Ω resistive load, showing fast rise time with no ringing or overshoot. Figure 7 shows the 10kHz square-wave response into 5Ω and 2.2μF. There is a small amount of overshoot (10%), followed by a half cycle of well-damped ringing, indicating good high-frequency stability.

Figure 8 is a plot of the amplifier being overdriven at 95W and 1kHz, showing symmetrical clipping. Figure 9 is a plot of the amplifier being overdriven at 70W and 33Hz, showing output-transformer

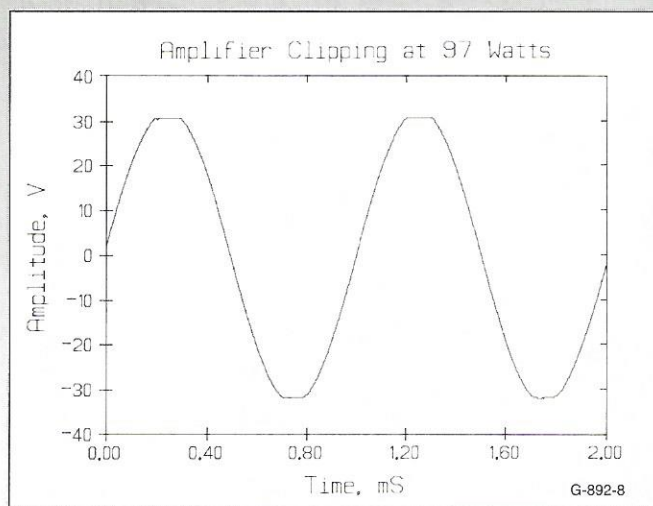


**FIGURE 8:** Amplifier clipping characteristic, 1kHz and 97W into 5Ω resistive load.

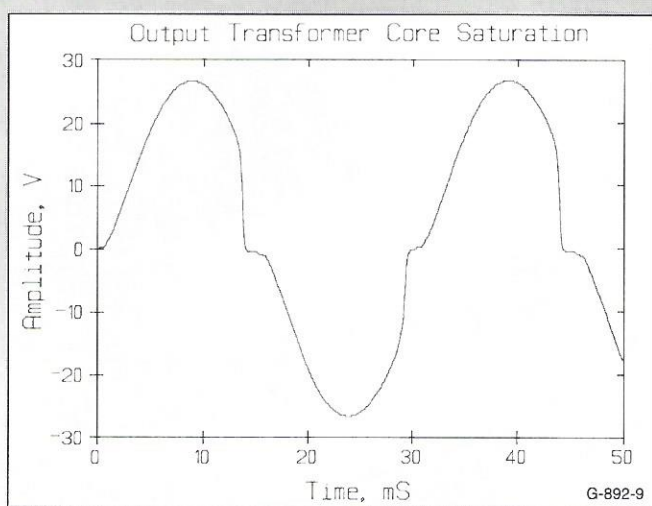

**FIGURE 9:** Output transformer core saturation at 70W and 33Hz into 5Ω resistive load. See text.



**PHOTO 2: Power-supply chassis.**

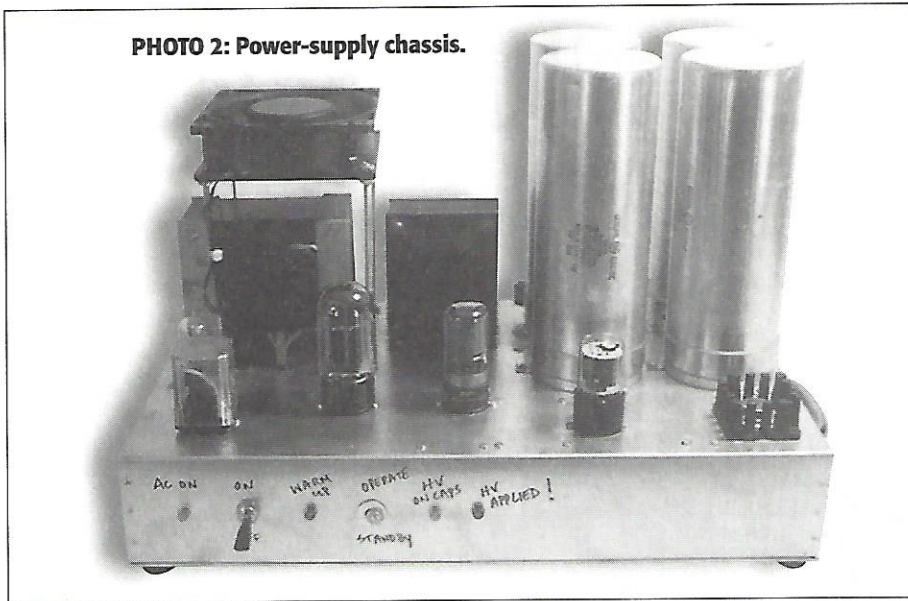

core saturation. The Plitron PAT4004 output transformers display the most abrupt onset of core saturation that I've ever seen. All transformers undergo core saturation at low frequencies, of course, but the PAT4004 goes from near-perfect performance to gross distortion within 1Hz! At 70W and 34Hz I measured THD of 0.18%, and at 33Hz I obtained the waveform shown in Fig. 9. At lower powers, the near-perfect performance extends to lower frequencies, as indicated in Fig. 3. This abrupt onset of core saturation may be a general characteristic of toroidal transformers.

I was at first concerned about what effect this core saturation would have on the amplifier's sound, since the gross distortion would be clearly audible. It turns out that the amplifier has excellent bass performance, as I discuss later in my listening comparisons. I suspect that most music has little power content below 30–40Hz, at least compared to the power in the upper bass or midrange. At any rate, I have been unable to detect core saturation on musical program material, either audibly or with my DSO.

To summarize the measurement results, I think the amplifier offers excellent performance. Although the distortion readings may seem high to those accustomed to the specifications of solid-state gear, the readings compare quite favorably to those of high-quality commercial tube amplifiers in the same power class, as reviewed recently in *Glass Audio*.<sup>4,5</sup> In making comparisons, note that some manufacturers (not those reviewed) advertise THD only at 1W and 1kHz, where it is low, rather than at higher powers or at the frequency extremes, where it is higher.

### CONSTRUCTION AND SETUP

The Cover Photo shows the completed amplifier. The two stereo channels are built side by side on a 17"×10"×3" aluminum chassis, and the power supply is built on a second identical chassis (Photo 2). I used a combination of point-to-point wiring and perforated board construction. The amplifier is sufficiently complicated that I recommend building it in sections and testing each section as you complete it. Perforated-board construction facilitates this by allowing you to test certain sections of the circuit outside the chassis on the bench. However, you could build the amplifier entirely with point-to-point wiring if you prefer.

The minimum test equipment required to build this amplifier is a digital multimeter (or VTVM) capable of accurate AC as well as DC measurements, and a sinusoidal signal generator. An oscillo-


scope is not absolutely required, but I highly recommend it because it simplifies checkout and troubleshooting.

I recommend building and testing the power supply first, beginning with the raw high-voltage supply. With a little planning, you can punch and drill the power-supply chassis before beginning any electronic assembly. You may need to modify the circuit slightly, depending on the transformer and filter capacitors you have available. The filter-capacitor bank should provide 1000–3000 $\mu$ F of capacitance at 600V DC, but you can obtain this with a variety of series or parallel connections.

Be aware that charged capacitance of this magnitude is dangerous and potentially lethal! With the bleeder resistors shown in the schematic, the capacitor bank can remain charged for 5–8 minutes after the power is switched off. Do not be tempted to discharge the capacitors by shorting across them, since the rapid release of energy will result in an enormous arc which may burn you or destroy components! You can test the power supply under load for brief periods using a 1250 $\Omega$ , 200W resistor, which will draw 400mA (I made such a resistor by wiring ten 125 $\Omega$ , 20W wirewounds in series). You should measure 505V  $\pm$ 20V with this load.

### BUILDING THE REGULATORS


Once the raw HV supply is working, you can build the HV regulators and check them for the correct output voltages. The low voltage regulated supplies Ecc and Eaa2 are each built on their own perforated boards. You should mount the IC102 (LM338K) on a heatsink, as shown on the right-hand side of Photo 2, isolat-

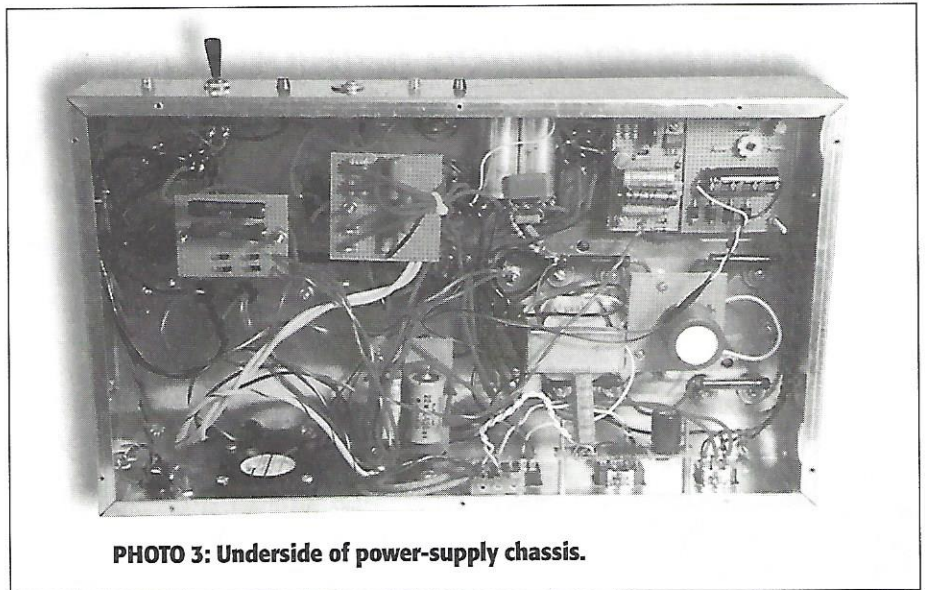

**PHOTO 3: Underside of power-supply chassis.**
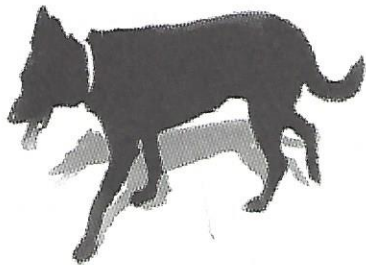
## Tippy Sez...

I'm goin' to  
**Bitco Electronics**  
Custom Built Pro Audio & Repair




Where I can get top notch  
Custom Pro and HiFi audio  
gear, built the way I want it!  
**(781)322-5560 ~Or~**  
**(888)429-9992**  
[www.tiac.net/users/bitco](http://www.tiac.net/users/bitco)

## SILVER SONIC™

Audio Cables

*Making the High End  
Affordable!*

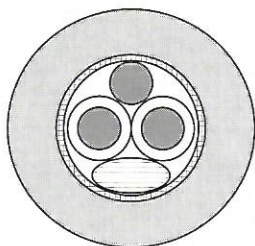"With tube amps and hybrids, the  
Silver Sonic competed with the best."  
*Bound for Sound*



Silver Sonic T-14 Speaker Cable  
Silver Sonic BL-1 Series II Interconnect  
Silver Sonic D-110 AES/EBU Digital  
Silver Sonic D-75 Digital Cable  
Hook up wire & Connectors

D.H. Labs, Inc.  
612 N. Orange Ave., Suite A-2  
Jupiter, FL 33458  
(561) 745-6406 (phone/fax)  
[www.dhlabscables.com](http://www.dhlabscables.com)

Reader Service #30

ing it from the chassis with a thermally  
conductive washer or gasket.

Install the fans last, since they are a  
nuisance to work around if they are spin-  
ning. *Photo 3* shows the installation of  
FAN102 on an edge under the chassis,  
oriented to bring air into the chassis. Ex-  
haust vents are shown on the right-hand  
side of *Photo 3*. As I mentioned, the  
power supply sits on a shelf in my cellar,  
where it can't be touched by accident. If  
it is in a room with children (or even  
adults), the exposed fans, hot tubes, and  
open vent holes represent a hazard, and  
you should install a screen cage.

Begin construction of the amplifier  
chassis by completing as much of the  
mechanical construction as possible. All  
grounds on the amplifier chassis are to a  
piece of 14-gauge solid wire connected to  
the chassis at a single point between the  
input jacks, as shown in *Photo 4*. The  
input jacks themselves are isolated from  
the chassis with an insulating washer,  
and the input grounds are connected to  
the grounded side of resistor R1 on the  
board containing tube V1.

### COMPONENT ASSEMBLY

I assembled tubes V1 and V2 and their  
associated components (including  
C2-C4 and R12-R13) on a 3" x 5" piece of  
perforated board. Once they're assem-  
bled, you can power up the circuit  
(please be extremely careful when work-  
ing with the HV applied!) and check for a  
plate voltage of about 120V on the 5879,  
a cathode voltage of about 125V on the  
12AU7, and plate voltages around 280V  
on the 12AU7. If these are obtained,  
apply a small test signal (100mV RMS,  
1kHz) to the input and check for a gain of  
50-60 to both outputs of the phase in-  
verter. You should adjust trimmer R47 at  
this point so the two outputs of the phase

inverter are equal in magnitude.

You can also assemble tubes V3, V4,  
V5, and their associated components (in-  
cluding R32-R35 and C10-C13) on a 3"  
by 5" piece of board. For testing purpos-  
es, you can temporarily connect the un-  
connected ends of R33 and R35 to Ebb2,  
since you cannot yet connect them to the  
6L6GC plates. When you power on the  
circuit, connect a voltmeter across R16  
and adjust R20 for 4.55V.

Similarly, adjust R21 for 4.55V across  
R17. These two adjustments set the driv-  
er-stage idle current to 5mA. Under this  
condition, the plates of the 6SN7 should  
idle at about 225V, and the cathodes at  
about 65-70V. If you cannot achieve the  
correct 5mA bias current by adjusting  
R20 or R21, and there is no wiring error,  
try substituting a different MPF102 JFET.  
I've noticed that the variability in these  
JFETs can be very wide, and you may  
have an out-of-spec transistor.

When the idle currents are set, you can  
apply a 100mV test signal to the grid of  
one of the 6SN7 sections through a DC  
blocking capacitor. You should measure a  
gain of 10-15 to the cathodes of the cor-  
responding 12AU7. Use a second DC  
blocking capacitor between the 12AU7  
cathodes and your VTVM or oscilloscope.  
When you have verified the correct gains,  
disconnect R33 and R35 from Ebb2 and  
set the board aside.

### WIRING

Finally, you can wire the output tubes and  
their associated circuitry, including the  
bias circuits, C6-C9, and the output trans-  
former. Also wire the two circuit boards  
(per channel) into the larger amplifier cir-  
cuit, connecting the inner feedback loops,  
but leaving the outer feedback loop tem-  
porarily open. Be careful to wire the am-  
plifier exactly according to the schematic

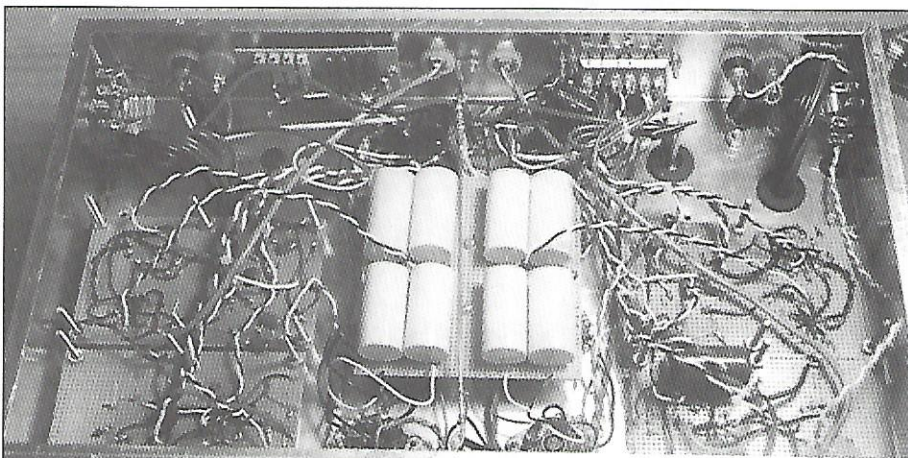


PHOTO 4: Underside of amplifier chassis.

in order to maintain correct phasing of the input and output. It is easy to invert the signal phase inadvertently when wiring the circuit boards or T1.

Apply power without inserting the output tubes and adjust R38-R39 and R42-R43 for -30V at the 6L6GC grids (pin 5 of the empty sockets). Then, with the power off, connect a 5Ω, 100W resistor to the speaker output, insert the tubes, and reapply power. If the amplifier oscillates with the outer feedback loop open, then the inner feedback loops must be out of phase or miswired. Adjust R38-R39 and

R42-R43 for 50mA through the corresponding 6L6GC, equivalent to 2.35V across each of the 47Ω cathode resistors. With the 5Ω load resistor connected to the speaker output, apply a 50mV test signal and check for a gain of about 70. If you have an oscilloscope, check that the output is in phase with the input.

Complete the wiring by connecting the outer feedback loop. If the amplifier oscillates, then there is probably a phase reversal, which you can correct by reversing the primary leads of T1. Recheck the settings of R38-R39 and R42-R43 after an

hour of operation. Also recheck the settings of R20-R21 and R47. If you have an oscilloscope, check the power output and frequency response. If you have distortion-measuring equipment, set R47 for minimum IM or THD at 70W.

## LISTENING COMPARISONS AND CONCLUSIONS

I've compared this amplifier to my Williamson 20/20, to my 20W Class A tube amp, and also to a 14W single-ended amp using paralleled 2A3 triodes. My comparisons were not rigorous A/B tests in which I rapidly switched between the various amplifiers. Instead, I installed each amplifier into my system and listened to it over a period of days or weeks, trying to form an overall impression of their strengths and weaknesses.

I don't have golden ears, and I've always found it difficult to reliably distinguish similar amplifiers. In this case, the most obvious distinction between the amplifiers was on the basis of power. The new 70W amp gives the impression of being able to produce virtually any volume level I would wish with the Magneplanars, without apparent clipping or compression. I believe it is superior to the 20/20 in this respect.

One of the common weaknesses of tube amps is in the bass region, where the sound is not as clear as that of solid-state amps. This new 70W amp does not share that weakness; low notes on organ recordings are as clean as I've heard through the Magneplanars, equaling or even surpassing the performance of the 20/20.

I must admit that at lower power levels there was very little to distinguish between the four amplifiers. I did have the impression that the single-ended amp was less clear than the other three, but in all fairness, a 14W amp is severely overstressed by the relatively inefficient Maggies.

I'm pleased with my 70W 6L6GC amp. After almost three years, I've found nothing to fault in its sound or reliability. I hope some of you will be equally pleased. ❖

PRICE VALIDITY TO END SEPT. 1999 - Ask About Any Type Not On This List

# CVC

# CHELMER VALVE COMPANY

## for High Quality Audio Tubes

Everybody in the tube business knows that the justly famous Brand names of yesteryear like BRIMAR, GEC, MULLARD, RCA & TELEFUNKEN Etc. Etc. are scarce and often very expensive.

Although we supply all major brands when available (and have many in stock) our policy is to offer a range of tubes, mostly of current manufacture, the best we can find from factories around the world, which we process specially to suit audio applications. The result - CVC PREMIUM BRAND.

Our special processing includes selection for LOW NOISE, HUM & MICROPHONY and controlled BURN - IN on all power tubes to improve STABILITY and select out tubes with weaknesses Etc.

### A selection of CVC PREMIUM Audio Tubes

PRE-AMP	POWER TUBES	POWER TUBES	POWER TUBES	SOCKETS ETC.				
ECC81	5.20	EL34G	7.70	6146B	10.50	B9A (Chassis or PCB)	1.60	
ECC82	5.20	EL34 (TESLA)	8.20	6336A	46.00	B9A (Ch. or PCB) Gold Plated	3.00	
ECC83	5.20	EL34/6CA7 (Large Dia.)	10.70	6550A	11.00	Octal (Ch. or PCB)	1.80	
ECC85	6.00	EL84/6BQ5	4.80	6550WA or WB	13.50	Octal (Ch. or PCB) Gold Plated	4.20	
ECC88	5.00	EL509/519	13.00	7581A	11.00	4 Pin (For 2A3, 300B Etc.)	3.30	
ECF82	5.00	E84L/7189A	6.50	807	9.00	4 Pin (For 2A3, 300B Etc.)/G/Plated	5.00	
ECL82	5.20	KT66	9.50	811A	11.00	4 Pin Jumbo (For 211 Etc.)	11.00	
ECL86	5.20	KT66R	22.00	812A	34.00	4 Pin Jumbo (For 211 Etc.)		
EF86	5.60	KT77	12.00	845	30.00	Gold Plated	15.00	
EB0F Gold Pin	10.00	KT88 (Standard)	12.50	<b>RECTIFIER TUBES</b>			5 Pin (For 807)	3.00
EB1CC Gold Pin	6.80	KT88 (Gold Special)	21.00				EZ80	4.20
EB2CC Gold Pin	8.00	KT88 (GL Type)	30.00	EZ81	4.70	9 Pin (For EL, PL509, Ch. or PCB)	5.00	
EB3CC Gold Pin	7.50	PL509/519	9.00	GZ32	12.00	Screening Can		
EB8CC Gold Pin	8.00	2A3 (4 or 8 Pin)	14.50	GZ33	10.00	(For ECC83 Etc.)	2.00	
6EU7	6.00	211	22.00	GZ34	6.70	Anode Connector		
6SL7GT	8.50	300B	50.00	GZ37	8.70	(For 807 Etc.)	1.50	
6SN7GT	4.60	6C33C-B	27.00	5U4G	5.50	Anode Connector		
6922	5.50	6L6GC	6.50	5V4GT	4.70	(For EL 509 Etc.)	1.70	
7025	6.50	6L6WGC/5881	8.00	5Y3GT	4.20	Retainer		
		6V6GT	5.00	5Z4GT	4.70	(For 6LWGC Etc.)	2.00	
		6080	11.50					

### ...and a few "Other Brands" (inc. Scarce types).

5R4GY FIVRE	7.00	6B4G SYLVANIA	27.00	6SN7GT BRIMAR	10.00	13E1 STC	110.00
5R4WGY CHATHAM USA	10.00	6BW6 BRIMAR	5.00	12AT7WA MULLARD	5.00	805 CETRON	50.00
5U4GB RCA or GE	12.00	6BX7 GT GE	8.50	12AY7 GE-SYLVANIA	7.75	5842A GEC	15.00
5Y3WGT SYLVANIA	5.00	6CG7/6FQ7 SYLVANIA	7.50	12AZ7 GE	7.50	6080W TUNGSOOL	12.50
6AS7G RCA or SIEMENS	12.00	6CL6 RCA or GE	5.00	12BH7A GE or RCA	13.00	6550A GE	23.00
6AU6WC SYLVANIA	3.50	6CW4 RCA	11.00	12BY7A GE	9.00	6146B GE	17.00
		6SL7GT STC	8.50	12E1 STC	12.50	ALL PRICES IN U.K. POUNDS £	

Please note carriage extra + VAT (EEC only) — When ordering state if matching required (add £1.00 per tube).  
Payment by CREDIT CARD (ACCESS, VISA, MASTERCARD) or BANKERS DRAFT, TRANSFER or CHEQUE (UK ONLY).  
FAX or POST your ORDER — We shall send PROFORMA INVOICE if necessary

Valve Amplifiers sound better still fitted with CVC PREMIUM Valves!

Chelmer Valve Company Ltd. • The Stables • Baddow Park, Great Baddow  
Chelmsford, Essex CM2 7SY, England

☎ 44 (0) 1245 265865 • Fax: 44 (0) 1245 490064

E-mail: sales@chelmervalue.com • Web Site: http://www.chelmervalue.com

## REFERENCES

1. R. Williamson, "The Twin-Twenty, Mark II," *The Audio Amateur*, 1/70, p. 4.
2. RCA Receiving Tube Manual, RC-30, 1975.
3. Menno van der Veen, "Letters," *Audio Electronics* 1/98, p. 41.
4. Charles Ochs, "Kit Report: Velleman 100W per Channel Stereo Valve Amp," *Glass Audio* 3/96, p. 65.
5. Charles Hansen, "Kit Report: The Assemblage ST-40," *Glass Audio* 4/98, p. 50.

Reader Service #40