\bigcirc		1
O THE CONTRACT OF THE CONTRACT.		
Did you know		
Electric eels can release powerful	circ	uit
electric charges of up to 650 volts!	Scri	be

First place your steel sheet under the drawing. Next, fill in the circles and follow the dotted lines with your Circuit Scribe conductive ink pen. Place your LED and power modules where indicated. Turn on the power and place your colored-in electric eel drawing on top and watch the lightning bolts light up!

LED

POWER



LED

LED,