







## **Installation Ideas**

Possible Power Bus Layout To Positive Common Positive (+) **▼**Bus (+) 🛛 🖉 **[(+)** Ø 0  $\oslash \oslash \oslash \oslash$ 0 To Switched To\_Negative Catch 🗷 Bus Diode Bus 0000 (-) 0 Ø 0 Ø -Always on - Switched Negative Negative

> Plasmatronics Pty Ltd 2/09/06 V1.0.0 JS © Attribution-NoDerivs 2.5 License http://creativecommons.org/

This diagram is for reference only. Wiring and fuses etc. must be installed as specified by the relevant Australian Standards.